
Basics Equations for Filters Synthesis


Giuseppe Macchiarella

Polytechnic of Milan, Italy

Electronic and Information Department



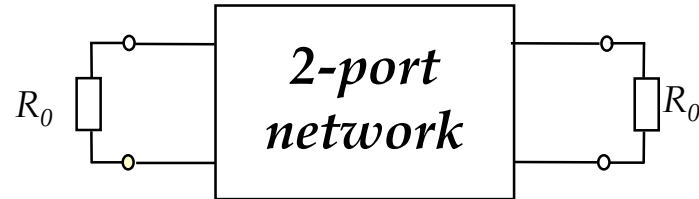Scattering parameters for lumped-elements filters



For linear, lumped-element networks the scattering parameters can be always represented as a polynomial ratio of the complex frequency p ($p = \sigma + j\omega$, with $\omega = 2\pi f$):

$$S_{11} = \frac{N_{11}(p)}{D(p)}, \quad S_{21} = S_{12} = \frac{N_{12}(p)}{D(p)}, \quad S_{22} = \frac{N_{22}(p)}{D(p)}$$

Roots of N_{11} (N_{22}) : reflection zeros

Roots of N_{21} : transmission zeros

Roots of D : poles (natural frequencies)

The above polynomials are called *characteristic polynomials*

Properties of lossless networks

For synthesis purposes the 2-port network representing a filter is assumed lossless (i.e. composed by lossless elements)

The scattering matrix of a lossless network is **unitary**:

$$\mathbf{S} \cdot \tilde{\mathbf{S}}^* = \mathbf{U}_2 \quad \longrightarrow \quad \begin{aligned} S_{11}(p) \cdot S_{11}(p)^* + S_{21}(p) \cdot S_{21}(p)^* &= 1 \\ S_{22}(p) \cdot S_{22}(p)^* + S_{12}(p) \cdot S_{12}(p)^* &= 1 \\ S_{11}(p) \cdot S_{21}(p)^* + S_{12}(p) \cdot S_{22}(p)^* &= 0 \end{aligned}$$

As a consequence, the following properties hold for the polynomials defining the scattering parameters (n is the filter order):

$$\begin{aligned} N_{11}(p) &= N(p), & N_{22}(p) &= (-1)^n N(p)^* \\ N(p) \cdot N(p)^* + N_{21}(p) \cdot N_{21}(p)^* &= D(p) \cdot D(p)^* \end{aligned}$$

The latter expression is known as *Feldtkeller equation*

Properties of characteristic polynomials

- ❑ The $*$ define the para-conjugate operator: $Q(p)^* = Q^*(-p)$.
The roots of $Q(p)^*$ are given by $-zQ^*$ (with zQ roots of Q)
- ❑ The roots of $D(p)$ are real or complex conjugate pairs.
The real part must be negative (strict *Hurwitz* polynomial)
- ❑ The roots of $N(p)$ can be everywhere in the complex plane (if complex they occur as conjugate pairs). If they are on the imaginary axis $N_{22}(p) = N(p)$
- ❑ The roots of $N_{12}(p)$ can be on the imaginary axis (conjugate pair) or on the real axis (pairs with opposite values) or as a complex quad in the p plane
- ❑ The coefficients of all the polynomials are **real numbers**.
Note that $Q(p)^* = Q(-p)$ in this case.

Steps of the synthesis process

- ❑ Assignment of selectivity specifications (Attenuation mask)
- ❑ Selection of a suitable *approximating function* and evaluation of its parameters in order to satisfy the specifications
- ❑ Evaluation of the characteristic polynomials from the approximating function
- ❑ Synthesis of the network from the polynomials

Simplify synthesis by frequency transformations

- ❑ In order to simplify the design process, the synthesis can be performed in a **normalized low-pass domain**, analytically defined by *frequency transformations*.
- ❑ By selecting a suitable frequency transformation, the synthesis can be carried out in the normalized domain

Low-pass \leftrightarrow Band-pass transformation

Let $s = \sigma + j\Omega$ be the normalized low-pass domain where the filter passband is defined $\Omega_B = -1 \leftrightarrow +1$.

The following equation relates the normalized domain with a pass-band domain suitably defined:

$$s = \frac{f_0}{B} \left(\frac{p}{f_0} + \frac{f_0}{p} \right)$$

f_0 and B are the frequency parameters defining the transformation:


$$f_0 = \sqrt{f_{p1} \cdot f_{p2}}, \quad B = f_{p2} - f_{p1}$$

The order of characteristic polynomials in the normalized domain is half of the order in the bandpass domain

Properties of the transformation (imaginary axis)


For $s=j\Omega$ and $p=j2\pi f$ it has
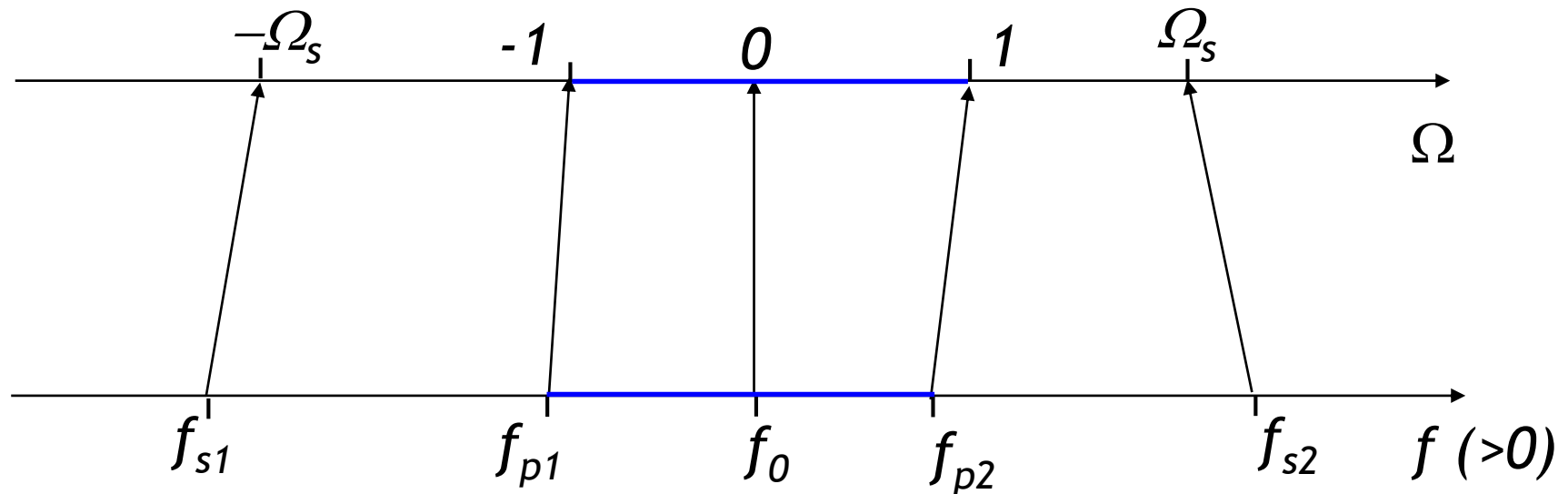
$$\Omega = \frac{f_0}{B} \left(\frac{f}{f_0} - \frac{f_0}{f} \right)$$



$$f_{p1} \cdot f_{p2} = f_{s1} \cdot f_{s2} = f_0^2$$

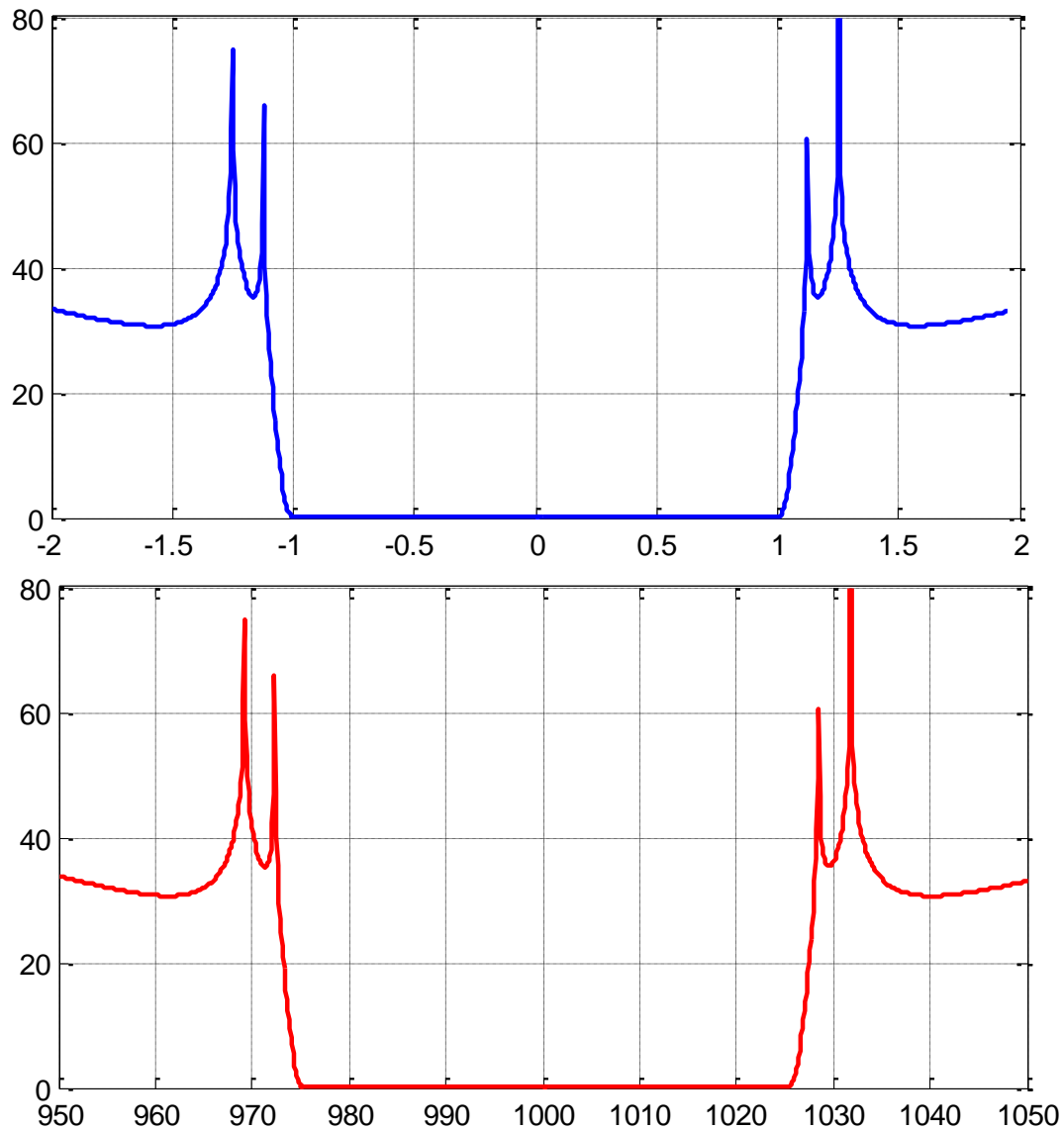
Conservation of response: $A(j\Omega)=A(j\omega)$



$B=50$ MHz
 $f_0=1000$ MHz


Circuit property of the transformation: Conservation of Z and Y

Low pass

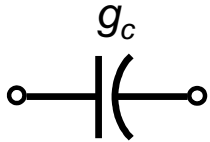


$$Y = s \cdot g_c$$
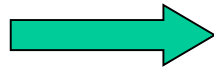
$$s = \frac{f_0}{B} \left(\frac{p}{f_0} + \frac{f_0}{p} \right)$$




$$Z = s \cdot g_L$$

Band pass

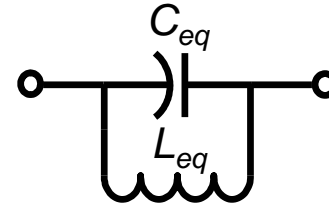

$$Y = p \cdot C_{eq} + \frac{1}{p \cdot L_{eq}} = \frac{f_0}{B} \left(\frac{p}{\omega_0} + \frac{\omega_0}{p} \right) \cdot g_c$$
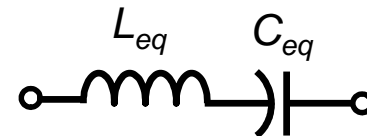
$$C_{eq} = \frac{g_c}{2\pi B}, \quad L_{eq} = \frac{1}{\omega_0^2 \cdot C_{eq}}$$




$$Z = p \cdot L_{eq} + \frac{1}{p \cdot C_{eq}} = \frac{f_0}{B} \left(\frac{p}{\omega_0} + \frac{\omega_0}{p} \right) \cdot g_L$$


$$L_{eq} = \frac{g_L}{2\pi B}, \quad C_{eq} = \frac{1}{\omega_0^2 \cdot L_{eq}}$$

Synthesis in the transformed frequency domain


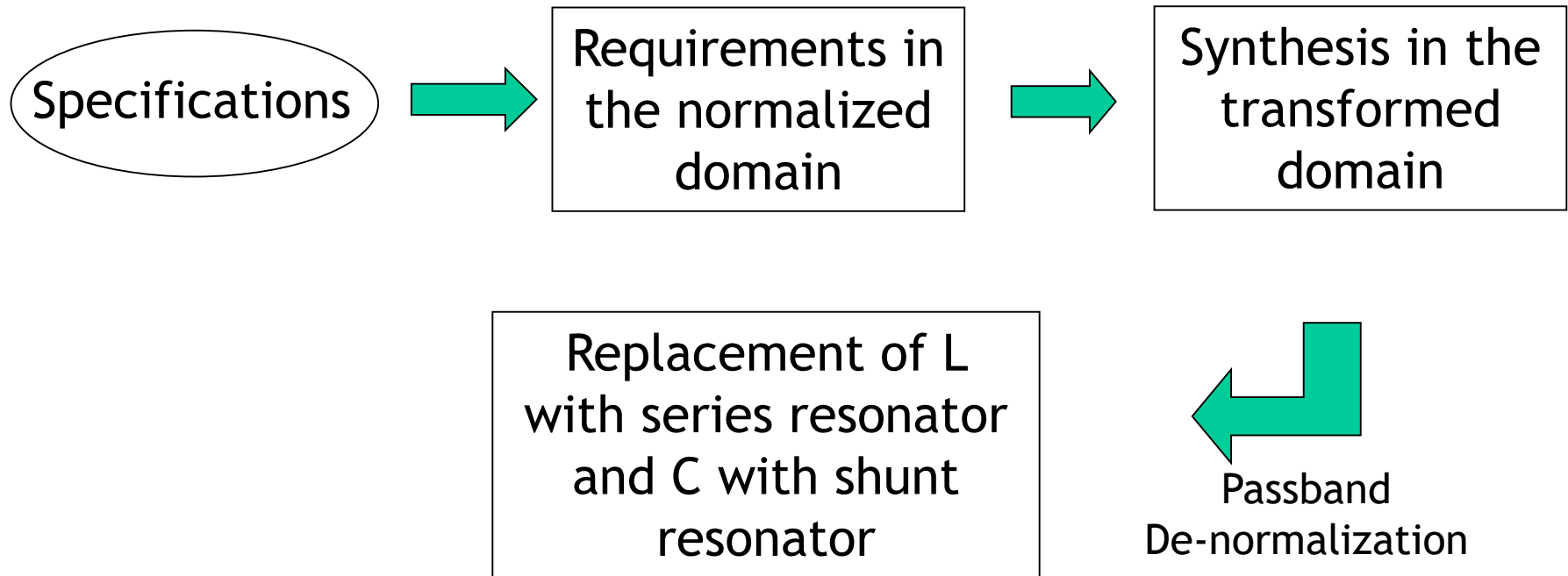
The synthesized network is then *de-normalized* to the band-pass frequency domain exploiting the *circuit transformation* seen before:



Specifications in the low-pass domain

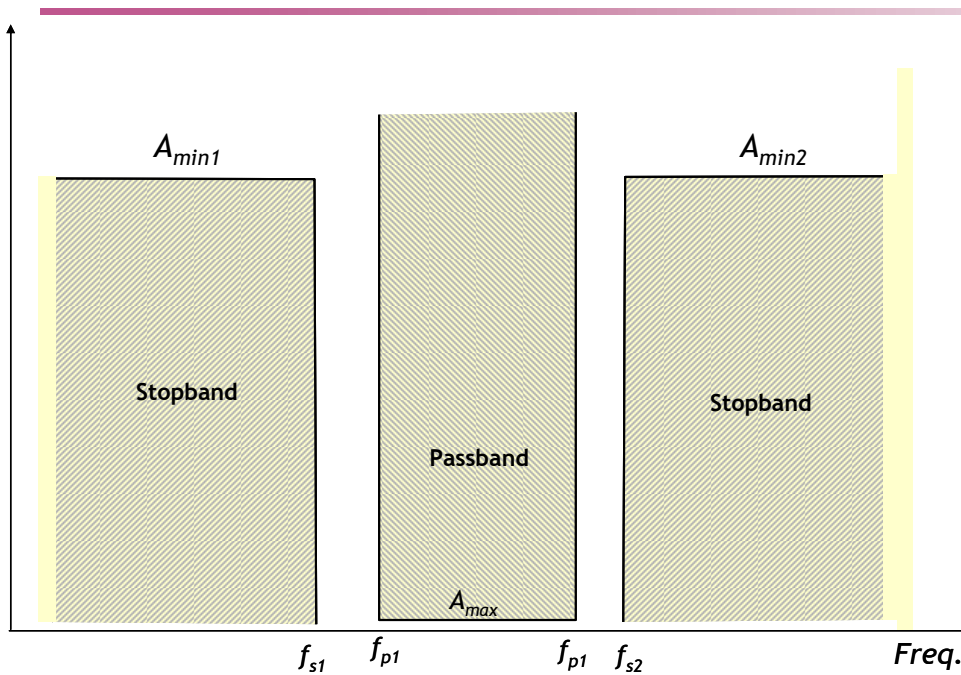

$$f_{s,1} \cdot f_{s,2} = f_0^2$$

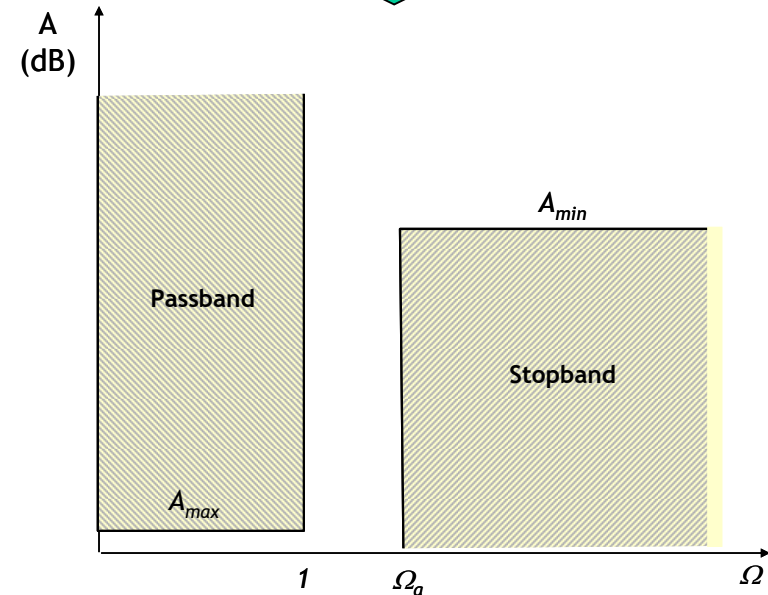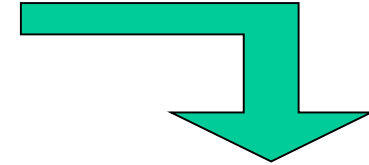

$$\Omega_a = \begin{cases} \frac{f_0}{B} \left(\frac{f_{s,1}}{f_0} - \frac{f_0}{f_{s,1}} \right), & A_{min} = A_{min1} \\ \frac{f_0}{B} \left(\frac{f_{s,1}}{f_0} - \frac{f_0}{f_{s,1}} \right), & A_{min} = A_{min2} \end{cases}$$

Approximation of the ideal Lowpass response

General expression for attenuation in the normalized domain:

$$A(\Omega) = 1 + \varepsilon'^2 C_n^2(\Omega) = \frac{1}{|S_{21}|^2} = \frac{|S_{21}|^2 + |S_{11}|^2}{|S_{21}|^2} = 1 + \left| \frac{S_{11}}{S_{21}} \right|^2 \Rightarrow$$

$$C_n^2(\Omega) = \frac{1}{\varepsilon'^2} \left| \frac{S_{11}}{S_{21}} \right|^2$$

C_n is called *Characteristic Function* and defines the approximation of ideal filter response

Properties:

$$-1 < C_n < 1 \quad \text{for } -1 < \Omega < 1$$

$$|C_n| = 1 \quad \text{for } \Omega = \pm 1$$

$$A(\pm 1) = 1 + \varepsilon'^2$$

Parameters ε' and n

Evaluation of ε' :

$$A_{\max} = \frac{1}{|S_{21,\min}|^2} = \frac{1}{1 - |S_{11,\max}|^2} = 1 + \varepsilon'^2 \Rightarrow \varepsilon'^2 = \frac{|S_{11}|_{\max}^2}{1 - |S_{11}|_{\max}^2} = \frac{10^{-\frac{RL}{10}}}{1 - 10^{-\frac{RL}{10}}}$$

RL is the Return Loss defined as: $RL = -20 \cdot \log(|S_{11}|_{\max})$

The parameter n represents the *order* of the characteristic function and corresponds to the number of resonators in the de-normalized network. n is derived from:

$$A(\Omega_s) = 1 + \varepsilon'^2 C_n^2(\Omega_s) \geq A_{\min} \Rightarrow C_n^2(\Omega_s) \geq \frac{A_{\min} - 1}{\varepsilon'^2}$$

In general there are two pairs $(A_{\min 1}, \Omega_{s1})$ and $(A_{\min 2}, \Omega_{s2})$ to be considered (the pair determining the largest n must be selected)

The characteristic function in s domain

Being $s=j\Omega$, it has:

analytic continuation

$$C_n^2(\Omega) = C_n(j\Omega) \cdot C_n(-j\Omega) \Rightarrow C_n^2(s) = C_n(s) \cdot C_n(-s) = C_n(s) \cdot C_n^*(s)$$

$C_n(s)$ is an *analytic function* which can be in general expressed as the ratio of two monic polynomials:

$$C_n(s) = \frac{1}{\varepsilon'} \frac{S_{11}(s)}{S_{21}(s)} = \frac{1}{\varepsilon'} \frac{F(s)}{P(s)/\varepsilon}$$

The roots of $F(s)$ are the *reflection zeros* ($A=1$). The roots of $P(s)$ are the complex frequencies at which the attenuation becomes infinity (*transmission zeros*).

If $P(s)=1$ it has an *all-pole* characteristic function (Attenuation is infinite only for $s=\infty$)

Characteristic polynomials in s domain

From the last expression of $C_n(s)$ the definition of the scattering parameters in s domain can be derived (all polynomials are monic):

$$S_{11}(s) = \frac{F(s)}{E(s)}, \quad S_{21} = \frac{P(s)/\varepsilon}{E(s)}$$

Note that once $F(s)$ and $P(s)$ are known, $E(s)$ is obtained by applying the unitary condition of S matrix:

$$\frac{1}{\varepsilon^2} P(s) \cdot P(-s) + [F(s) \cdot F(-s)] = E(s) \cdot E(-s)$$

$E(s)$ is found from the roots with negative real part of right-hand side (Hurwitz polynomial)

All-pole characteristic functions (P=cost)

□ Butterworth function:

$$C_n(\Omega) = \Omega^n$$

Main property: maximum flatness for $\Omega=0$, monotonic for $|\Omega|>0$

□ Chebyshev function:


$$\cos\left(n \cdot \cos^{-1}(\Omega)\right) \quad |\Omega| \leq 1$$

$$C_n(\Omega) =$$

$$\cosh\left(n \cdot \cosh^{-1}(\Omega)\right) \quad |\Omega| > 1$$

Main property: oscillates between ± 1 for $|\Omega|<1$ (n peaks), increases monotonically for $|\Omega|>1$

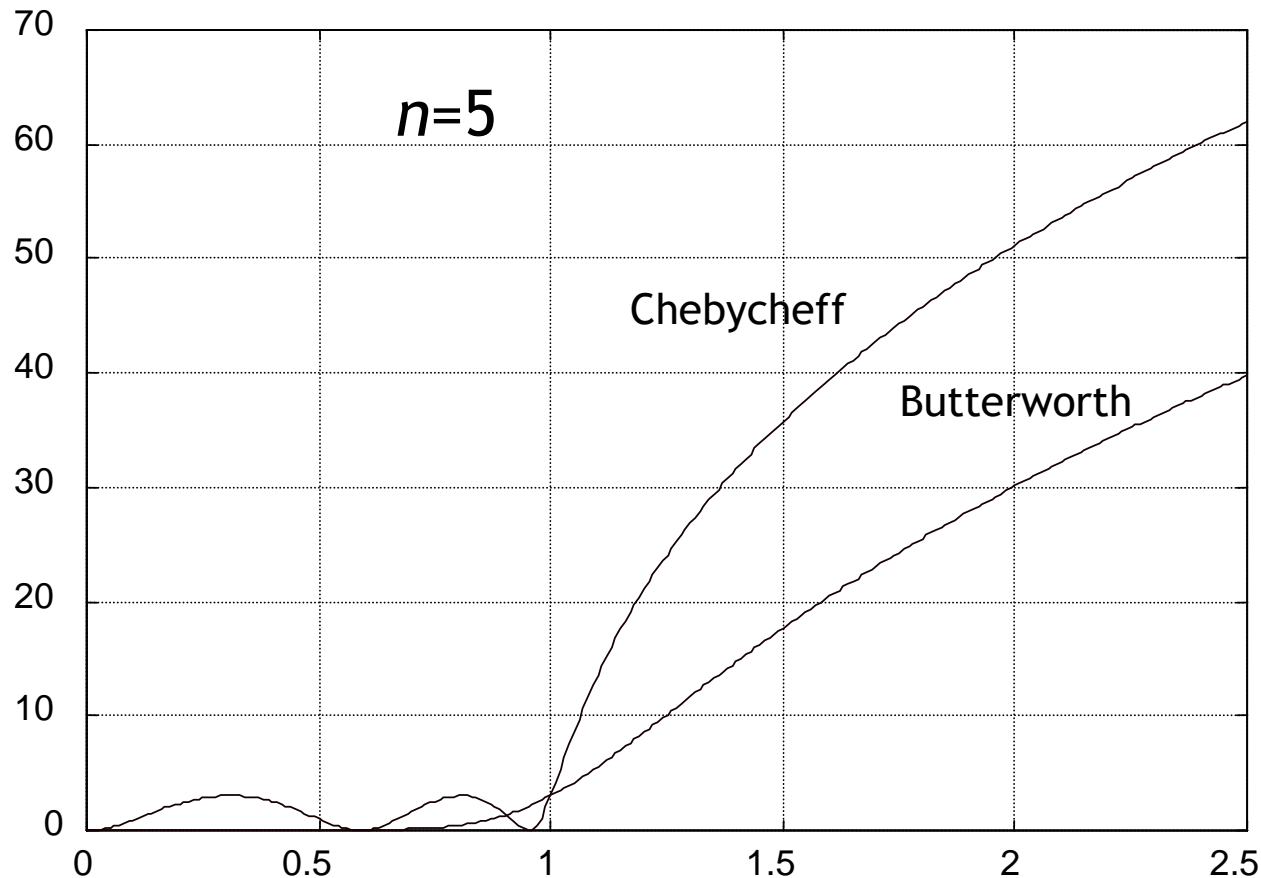Comparison between Butterworth and Chebicheff



Attenuation of Chebycheff function is $6(n-1)$ dB larger than Butterworth function for $|\Omega| \gg 1$

Evaluation of ε and n

□ Assigned parameters:

- Passband Return Loss in dB (RL)
- Filter bandwidth (B) and center frequency (f_0)
- Minimum attenuation (dB) in stopband ($A_{\min 1}$ at Ω_{S1} or $A_{\min 2}$ at Ω_{S2})


$$\text{Evaluation of } \varepsilon' = \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \quad \text{with } \Gamma_m = 10^{-(RL/20)}$$

$$n \geq \max \left\{ \left(\frac{A_{\min 1} + RL}{20 \log(\Omega_{S1})} \right), \left(\frac{A_{\min 2} + RL}{20 \log(\Omega_{S2})} \right) \right\} \quad \text{Butterworth characteristic}$$


$$n \geq \max \left\{ \left(\frac{A_{\min 1} + RL + 6}{20 \log(\Omega_{S1}) + 6} \right), \left(\frac{A_{\min 2} + RL + 6}{20 \log(\Omega_{S2}) + 6} \right) \right\} \quad \text{Chebycheff characteristic}$$

Normalized low-pass prototype (all-pole)

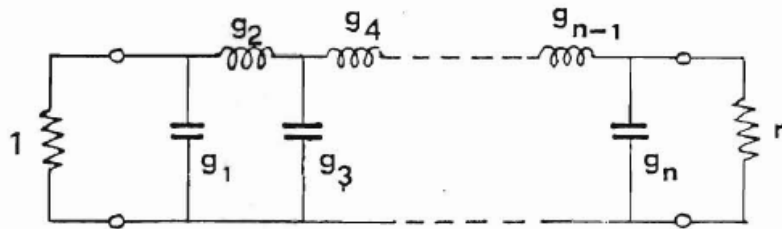
- Ladder network synthesized in the normalized domain assuming unitary reference load (generator side):



Lowpass

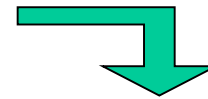

Bandpass

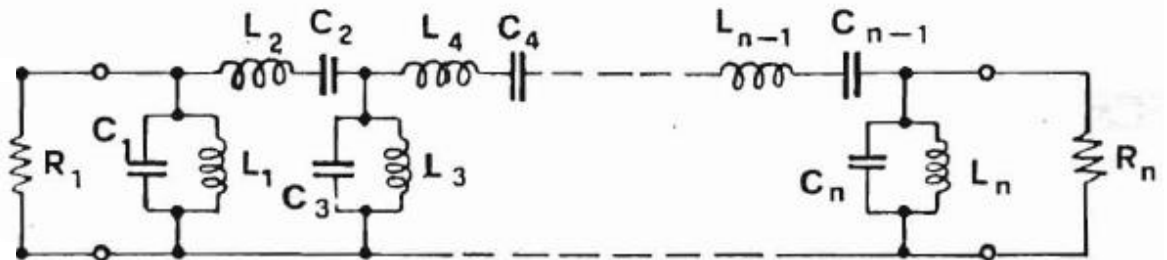

Bandpass de-normalization:

$g_1, g_3, \dots \rightarrow$ shunt resonators with $C_k = g_k / (R_1 \cdot 2\pi B)$

$g_2, g_4, \dots \rightarrow$ series resonators with $L_k = R_1 \cdot g_k / (2\pi B)$

Synthesis of lowpass prototype

□ Butterworth characteristic


$$r_n = 1, \quad g_q = 2a_q \sqrt[n]{\varepsilon'}, \quad a_q = \sin\left(\frac{(2q-1)\pi}{2n}\right)$$

□ Chebycheff characteristic

$$r_n = 1 \quad (n \text{ odd}), \quad r_n = \left[\sqrt{1 + \varepsilon'^2} - \varepsilon' \right]^2 \quad (n \text{ even})$$


$$g_1 = \frac{2a_1}{\gamma}, \quad g_q = \frac{4a_{q-1} \cdot a_q}{b_{q-1} \cdot g_{q-1}}, \quad a_q = \sin\left(\frac{(2q-1)\pi}{2n}\right)$$
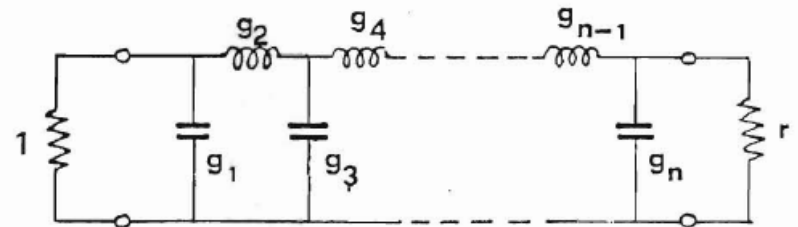
$$\gamma = \sinh\left(\frac{1}{2n} \ln\left(\frac{\sqrt{1 + \varepsilon'^2} + 1}{\sqrt{1 + \varepsilon'^2} - 1}\right)\right), \quad b_q = \gamma^2 + \sin^2\left(\frac{q\pi}{n}\right)$$



De-normalized (bandpass) network with only series or shunt resonators

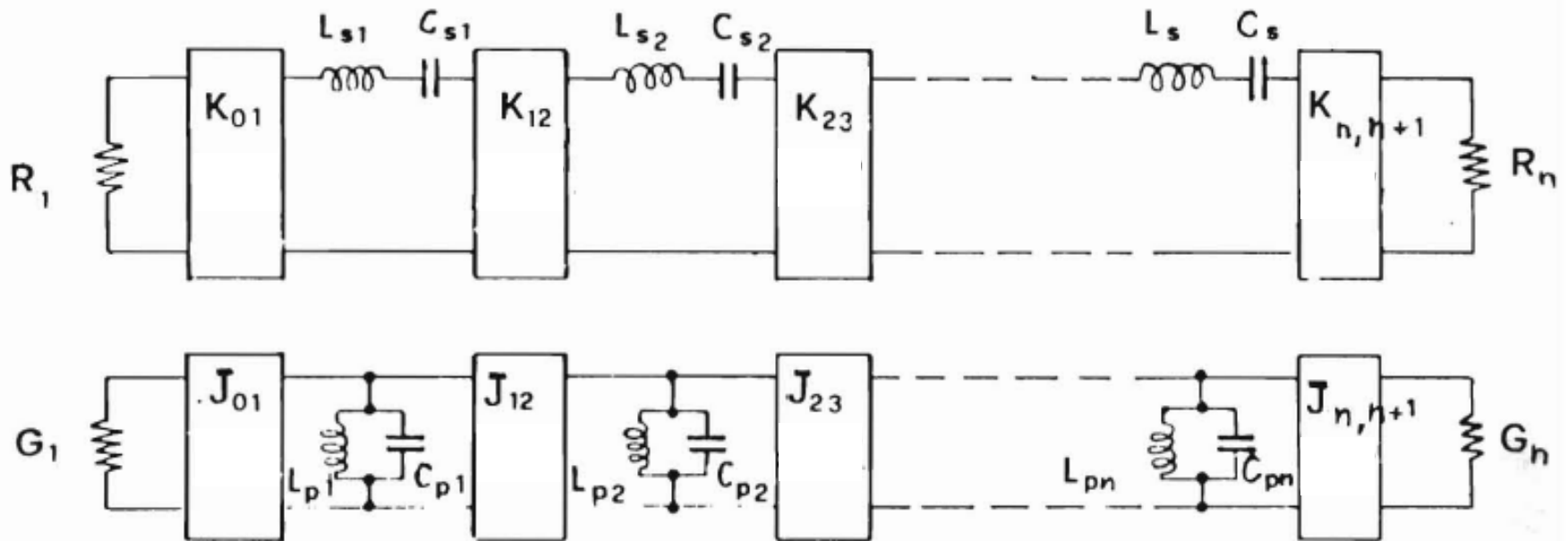For microwave frequencies implementation is requested to have only one type of resonator (series or shunt). This is obtained with the introduction of impedance (admittance) inverters



General design equation

Introduction of inverter determines additional degrees of freedom which allows the arbitrary assignments of some parameters (inverters or resonators parameter).
The condition to be satisfied are expressed by the following equations:

Series Network

$$K_{01} = \sqrt{\frac{B}{f_0} \frac{\omega_0 L_{s,1}}{g_1} R_1}$$

$$K_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{\omega_0 L_{s,q} \cdot \omega_0 L_{s,q+1}}{g_q \cdot g_{q+1}}}$$

Shunt Network

$$J_{01} = \sqrt{\frac{B}{f_0} \frac{\omega_0 C_{s,1}}{g_1} G_1}$$

$$J_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{\omega_0 C_{s,q} \cdot \omega_0 C_{s,q+1}}{g_q \cdot g_{q+1}}}$$

The bandpass network is assumed symmetric respect the central inverter (n even) or resonator (n odd)

Universal coupling parameters

Coupling coefficient:

$$k_{q,q+1} = \frac{K_{q,q+1}}{\sqrt{\omega_0 L_{s,q} \cdot \omega_0 L_{s,q+1}}} = \frac{J_{q,q+1}}{\sqrt{\omega_0 C_{s,q} \cdot \omega_0 C_{s,q+1}}} = \frac{B}{f_0} \sqrt{\frac{1}{g_q \cdot g_{q+1}}}$$


External Q:

$$Q_E = \frac{\omega_0 L_{s,1}}{K_{01}^2 / R_1} = \frac{\omega_0 C_{s,1}}{J_{01}^2 / G_1} = \frac{g_1}{B / f_0}$$

$\omega_0 L_{s,k}$ = Equivalent reactance of series resonators

$\omega_0 C_{s,k}$ = Equivalent susceptance of shunt resonators

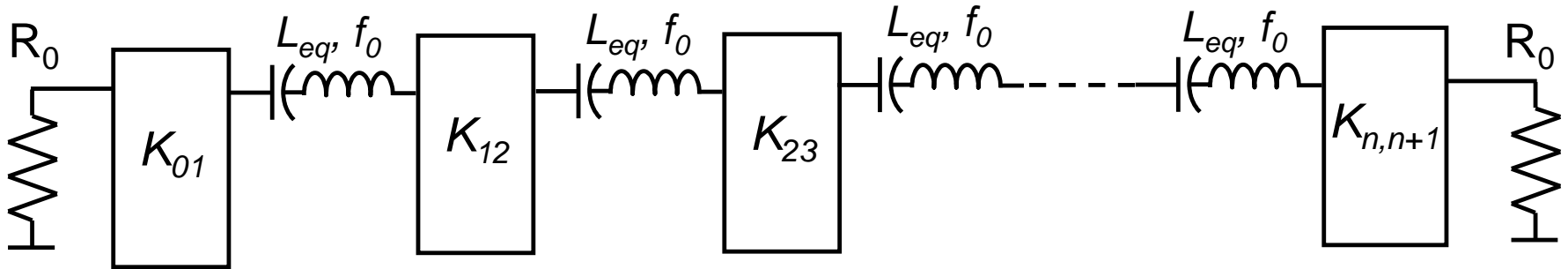In-line filters with all-equal resonators






From the general design equations:

$$K_{q,q+1} = k_{q,q+1} \cdot (\omega_0 L_{eq}) \quad K_{01} = K_{n,n+1} = \sqrt{\frac{\omega_0 L_{eq}}{Q_E} R_1}$$

with:

$$k_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{1}{g_q \cdot g_{q+1}}} \quad Q_E = \frac{g_1}{B/f_0}$$

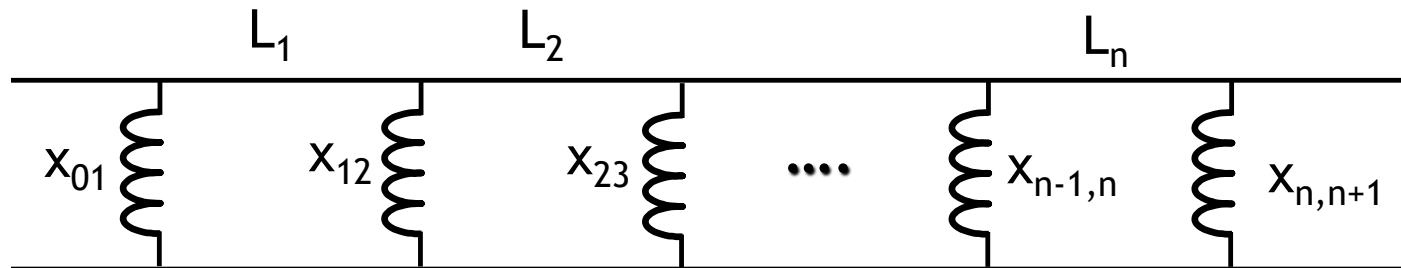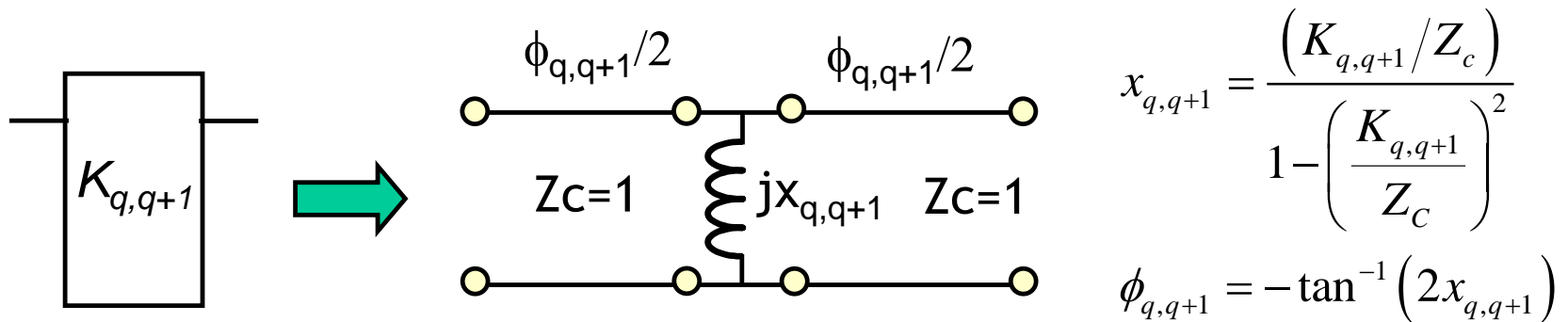
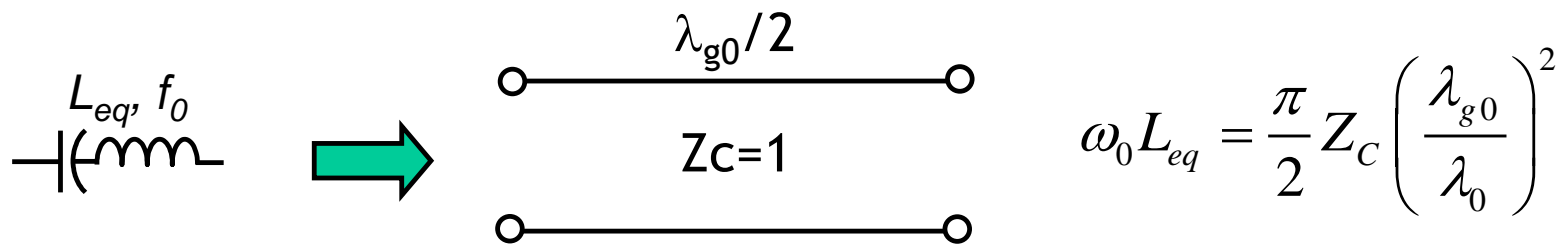
$\lambda_{g0}/2$ waveguide resonators coupled with inductive reactances



$$L_q = \frac{1}{\beta_{g0}} \left[\pi + \frac{\phi_{q-1,q} + \phi_{q,q+1}}{2} \right]$$

Inductive reactances in rectangular waveguide

□ Iris with finite thickness

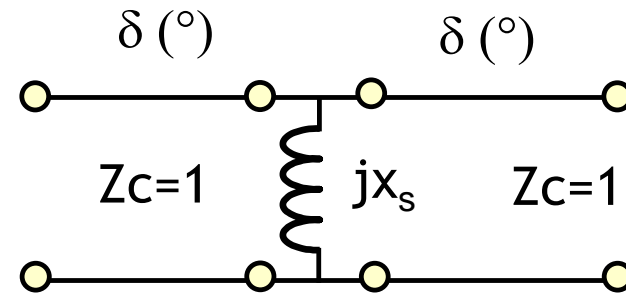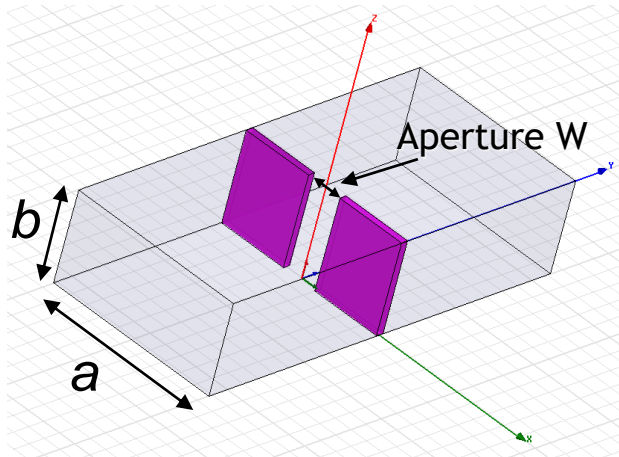


Equivalent circuit (reference sections: symmetry axis)

$$j \frac{X}{Z_c} = -\frac{1}{2} \frac{S_{12}}{S_{11}}, \quad \exp(-j2\delta) = (S_{12} - S_{11})$$


S_{11} , S_{12} : scattering parameters (computed numerically with EM simulators)

Evaluation of iris equivalent parameters

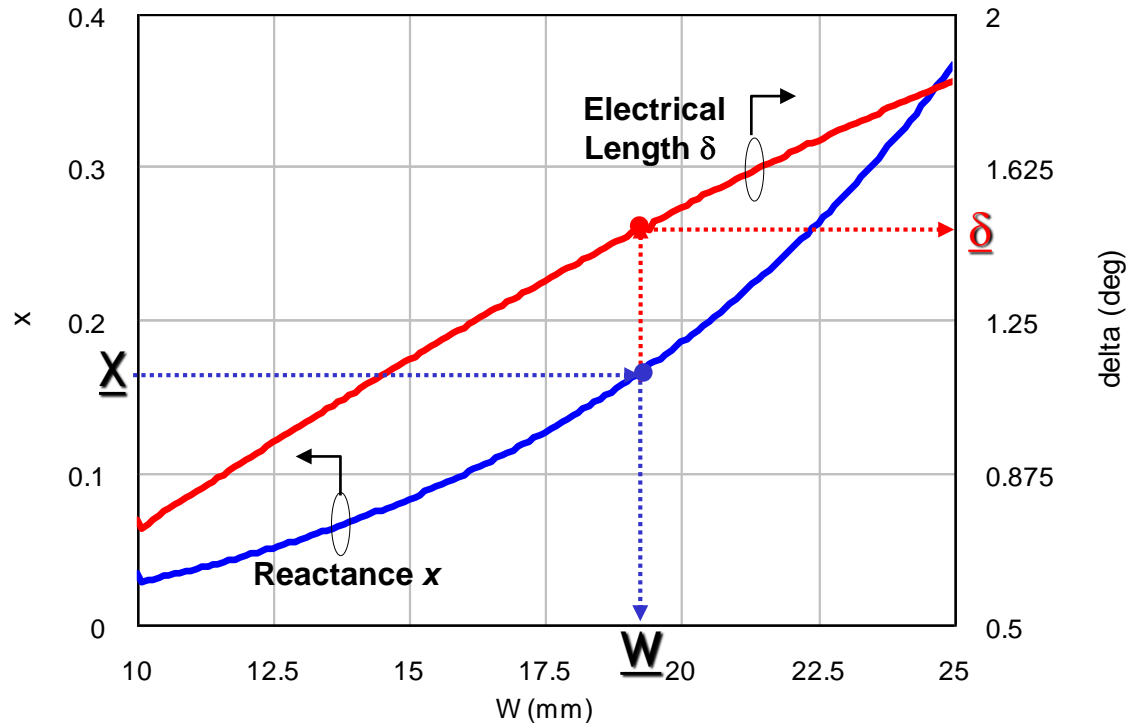

- With the previous formulas, the curves of x and δ vs. W are drawn (see the graph above).
- For the required value \underline{x} the aperture \underline{W} is first obtained through the blue curve. The corresponding electrical length $\underline{\delta}$ is derived from the red curve

Filter dimensioning

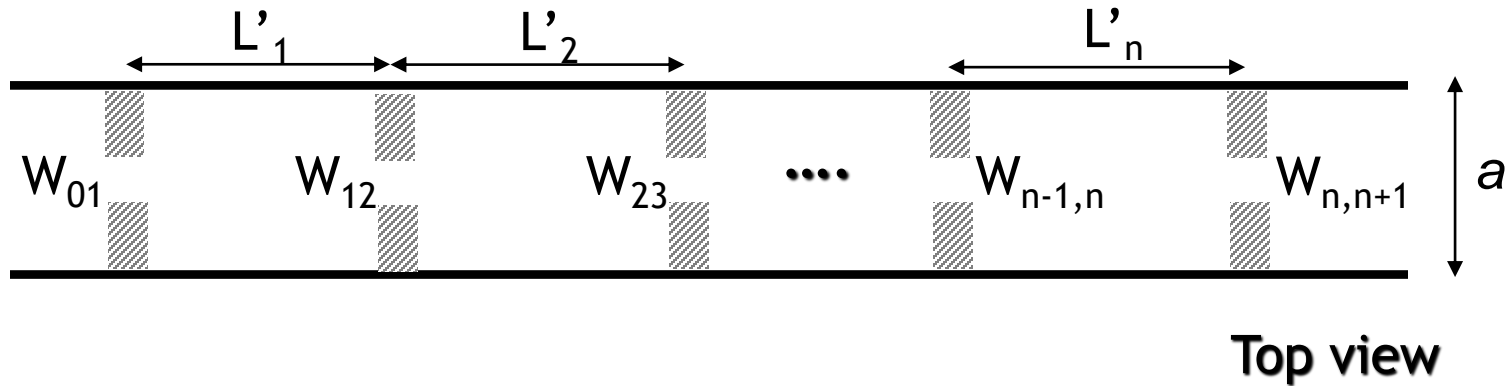

The apertures $W_{i,i+1}$ are evaluated as explained in the previous slide from the $K_{i,i+1}$.

The separation of the iris are obtained from the lengths L_q corrected with the irises parameters $\delta_{q,q+1}$:

$$L'_q = L_q - \frac{1}{\beta_{g0}} \left(\delta_{q-1,q} + \delta_{q,q+1} \right)$$

Example of design

Specifications:

$f_0=4$ GHz, $B=40$ MHz

Return Loss in passband ≥ 26 dB

$A_{s1} \geq 45$ dB for $f > 4.05$ GHz

$A_{s2} \geq 60$ dB for $f > 3.9$ GHz

Chebyshev characteristic

Being f_{s1} and f_{s2} not geometrically symmetric, the requested order n of the filter is obtained by selecting the larger between the following ones:

$$n_1 \geq \frac{A_{s1} + RL + 6}{20 \log(\Omega_{s1}) + 6} = 5.54$$

$$n_2 \geq \frac{A_{s2} + RL + 6}{20 \log(\Omega_{s2}) + 6} = 4.58$$

$$\mathbf{n=6}$$

Step 1: Evaluation of equivalent circuit param.

Selected waveguide: $a=50\text{mm}$, $b=25\text{mm}$

Waveguide parameters:

Cutoff frequency: $f_c=v/2a=3\text{ GHz}$

$$\lambda_{g_0} = \frac{\lambda_0}{\sqrt{1-(f_c/f_0)^2}} = 113.3\text{mm}, \quad \left(\frac{\lambda_{g_0}}{\lambda_0}\right)^2 = 2.286$$


Prototype normalized coefficients:

$$g_q=\{0.7919, 1.3649, 1.7002, 1.5379, 1.5089, 0.7163\}$$

Coupling reactances and resonator lengths:

$$x_{q,q+1}=\{0.223, 0.0345, 0.0235, 0.022, 0.0235, 0.0345, 0.223\}$$
$$L_q=\{52.21, 55.56, 55.78, 55.78, 55.56, 52.21\}$$

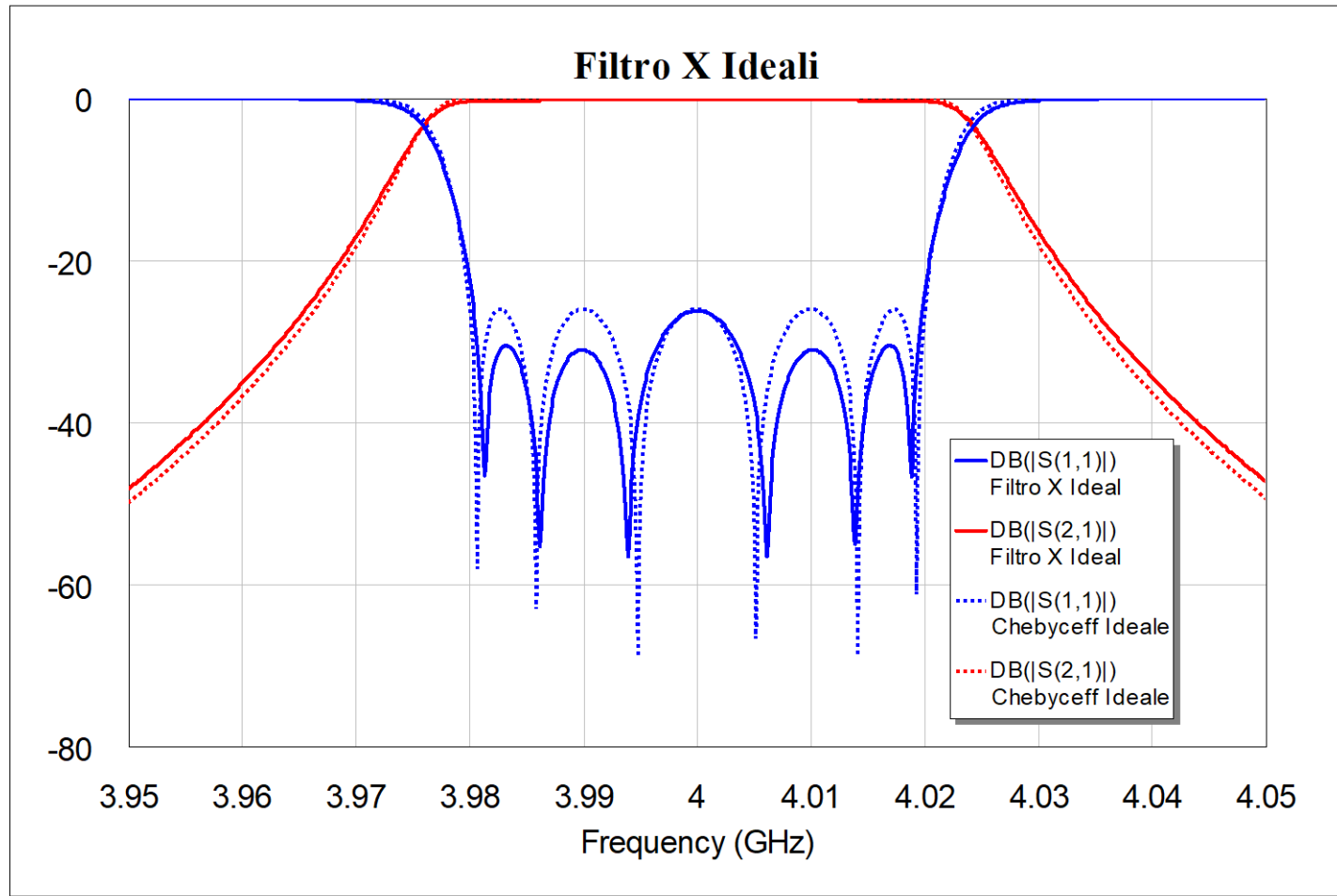Filter response (ideal inductive reactance)



The reactances are assumed constant with f


Step 2: Irises dimensioning

$$W_{q,q+1} = \{21.31, 10.85, 9.419, 9.213, 9.419, 10.85, 21.31\} \text{ mm}$$

$$\delta_{q,q+1} = \{0.507, 0.2536, 0.2145, 0.209, 0.2145, 0.2536, 0.507\} \text{ mm}$$


Corrected lengths of resonators:
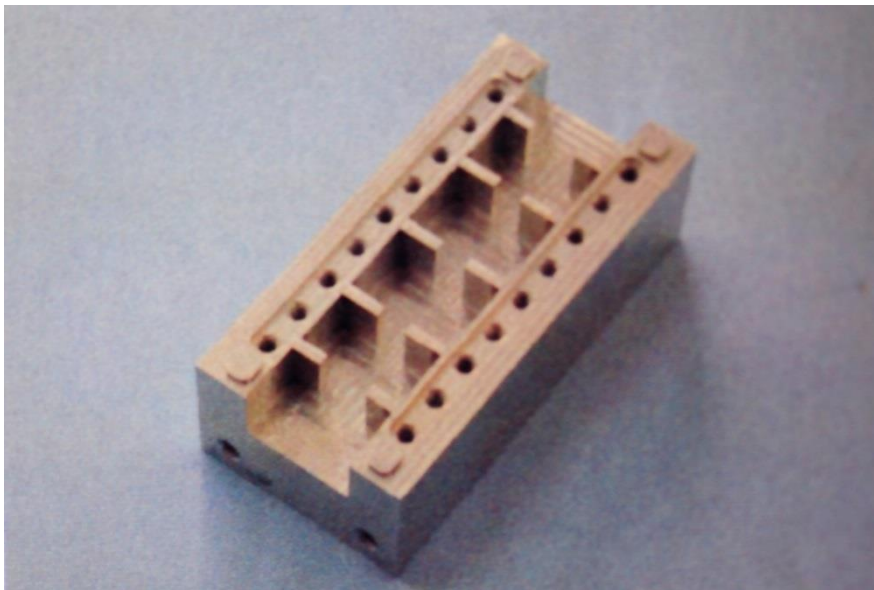
$$L'_q = \{51.45, 55.09, 55.36, 55.36, 55.09, 51.45\} \text{ mm}$$




Example of
fabricated device (4
resonators sample)





Computed filter response (Mode Matching)

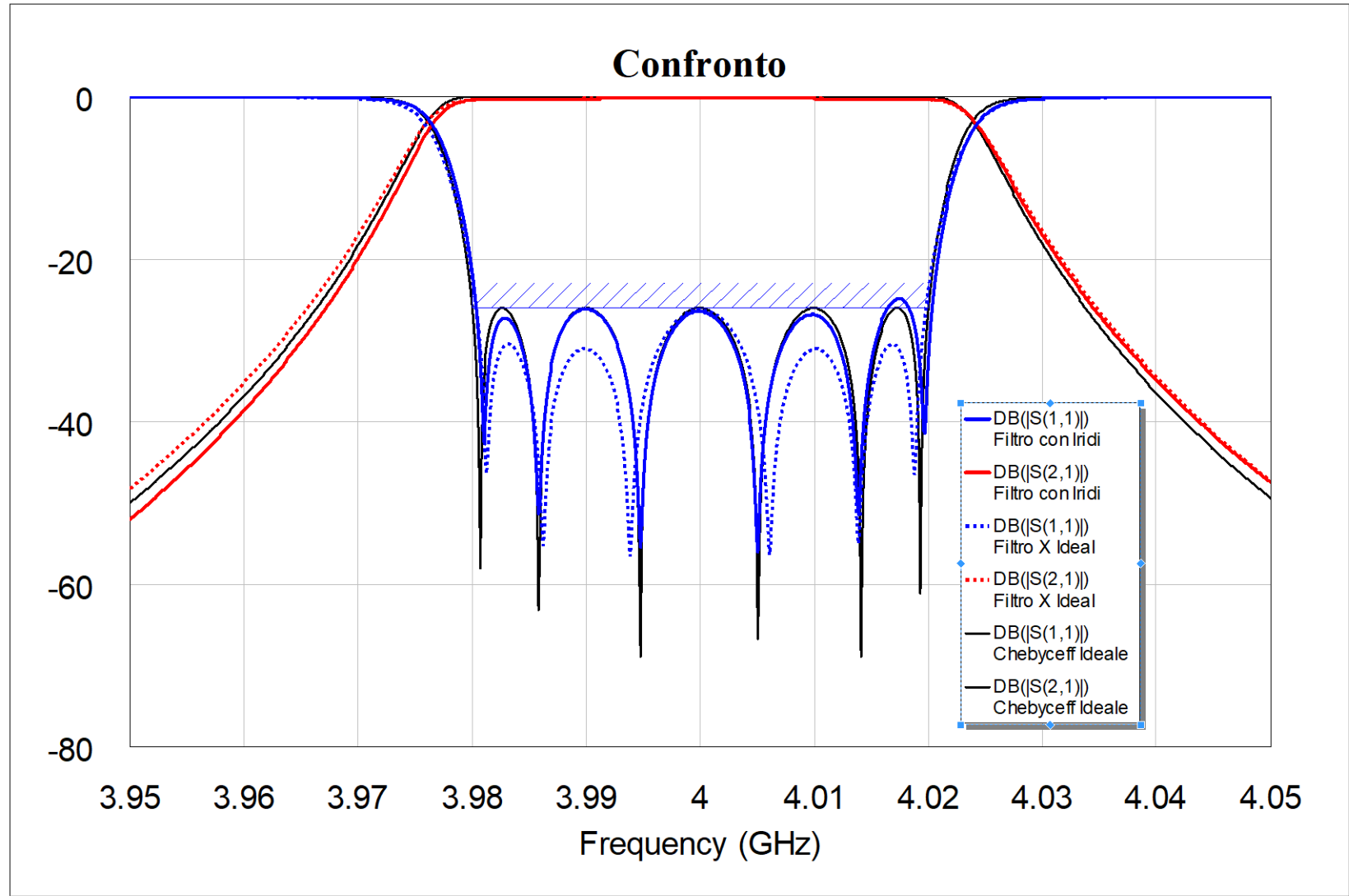


Broad frequency range response

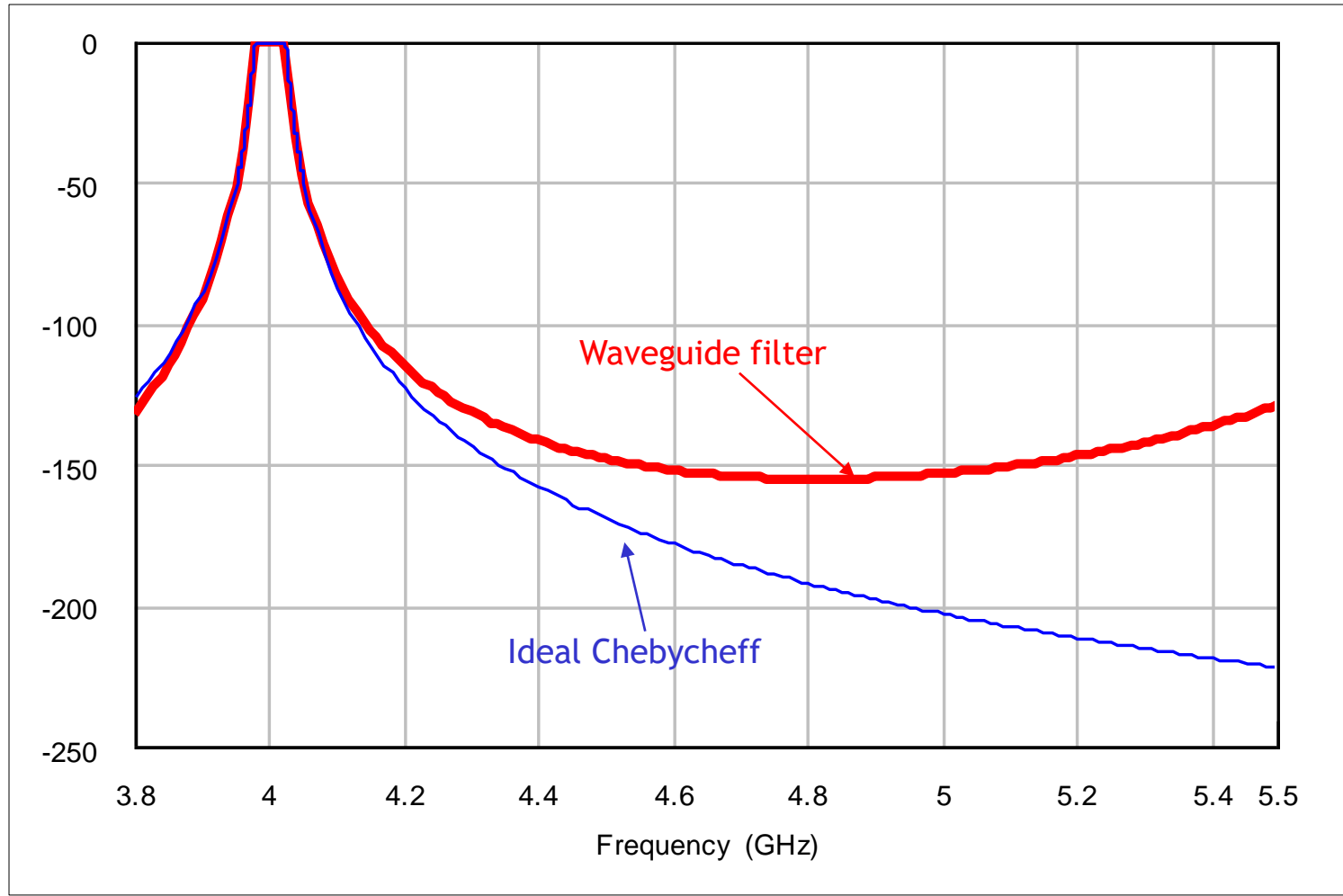

Effect of filter bandwidth on accuracy

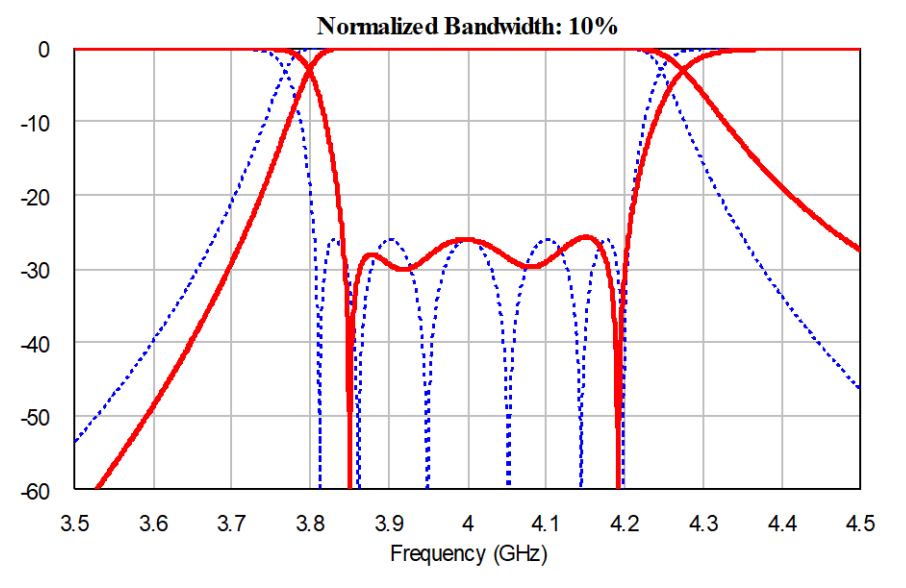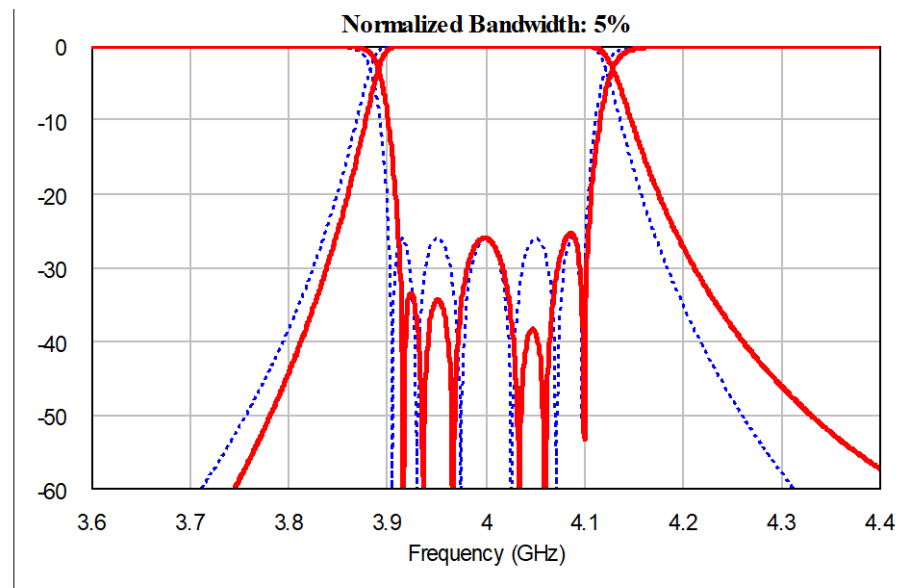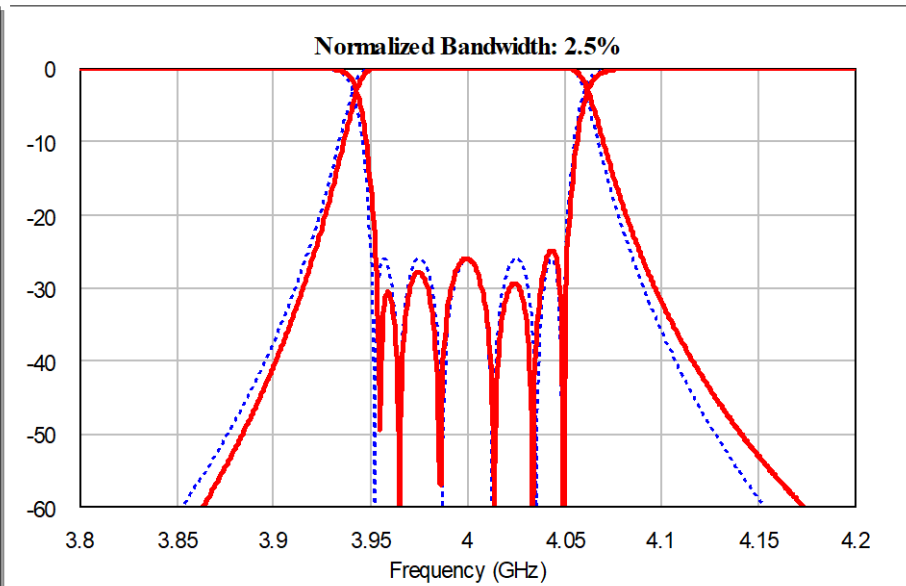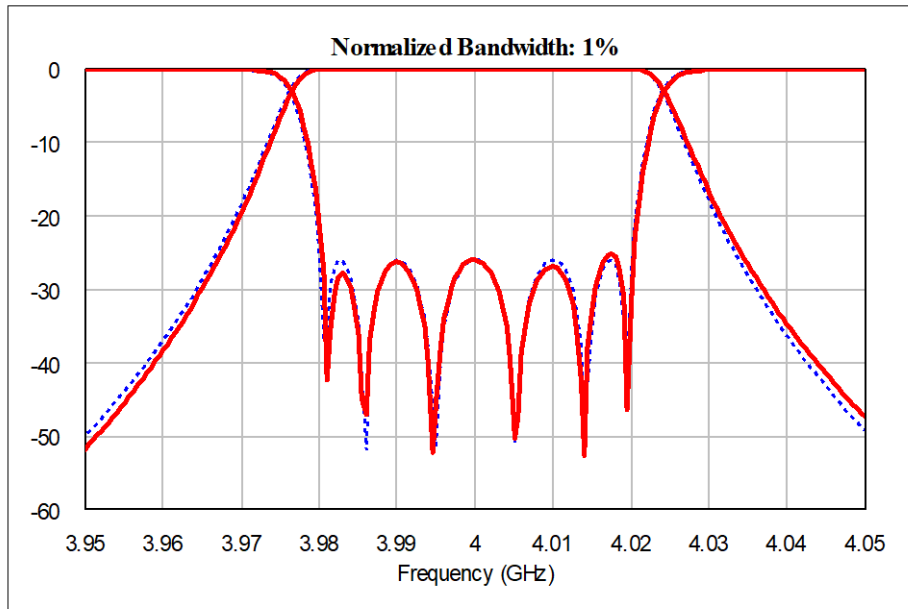

Multi-port simulation of the filter

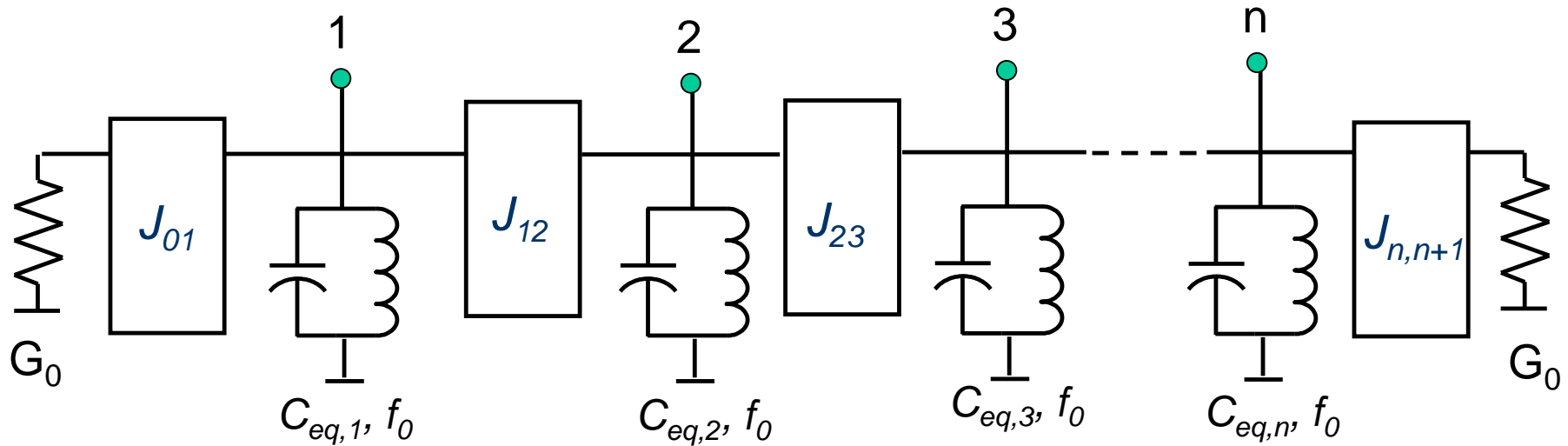

Extraction of matrix Y (EM simulation):

$$y_{i,i} = jB_{ris,i}, \quad y_{i,i+1} = jJ_{i,i+1}$$

$$B_{ris,i}(\omega) = \omega_0 C_{eq,i} \left(\frac{f}{f_0} - \frac{f_0}{f} \right) \Rightarrow \omega_0 C_{eq,i} = B_{eq,i} = \frac{1}{2} \omega_0 \left. \frac{\partial \text{Im}(y_{i,i}(\omega))}{\partial \omega} \right|_{\omega=\omega_0}$$

$$J_{i,i+1} = \text{Im}(y_{i,i+1}(\omega_0))$$

Extraction of Universal Parameters from Y matrix

$f_{0,i}$ is the frequency where $B_{i,i}=0$


$$Q_{ext,1} = \frac{B_{eq,1}}{J_{01}^2} G_0 = \frac{\left[\frac{1}{2} \omega_0 \frac{\partial \operatorname{Im}(y_{11}(\omega))}{\partial \omega} \right]_{\omega=\omega_0}}{\operatorname{Re}[y_{11}(\omega_0)]},$$

$$k_{i,i+1} = \frac{J_{i,i+1}}{\sqrt{B_{eq,i} \cdot B_{eq,j}}} = \frac{\operatorname{Im}(y_{i,i+1}(\omega_0))}{\frac{1}{2} \omega_0 \sqrt{\frac{\partial \operatorname{Im}(y_{i,i}(\omega_0))}{\partial \omega} \frac{\partial \operatorname{Im}(y_{j,j}(\omega_0))}{\partial \omega}}}$$

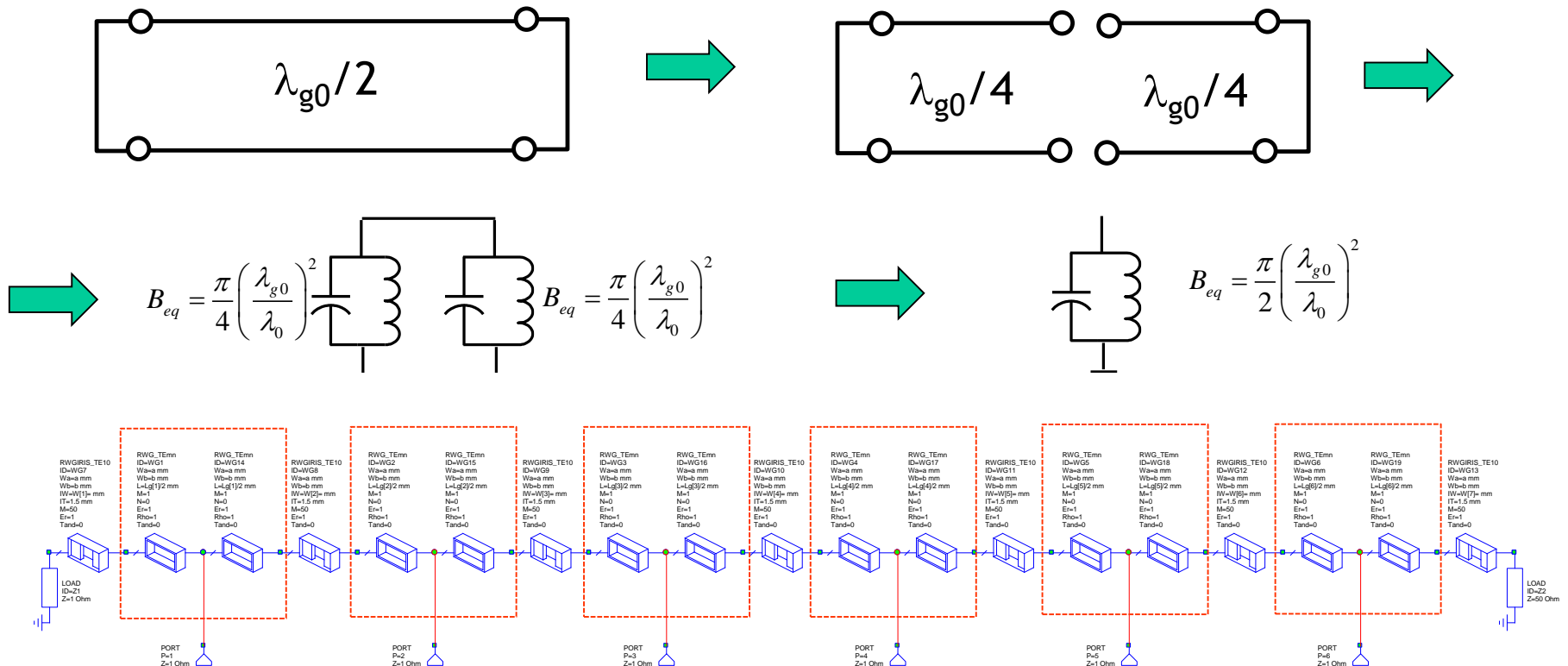
Example: waveguide filter seen before

Note


A short-circuited waveguide resonator of length $\lambda_{g0}/2$ observed at the center shows a shunt resonance:



Extracted $B_{i,i}$

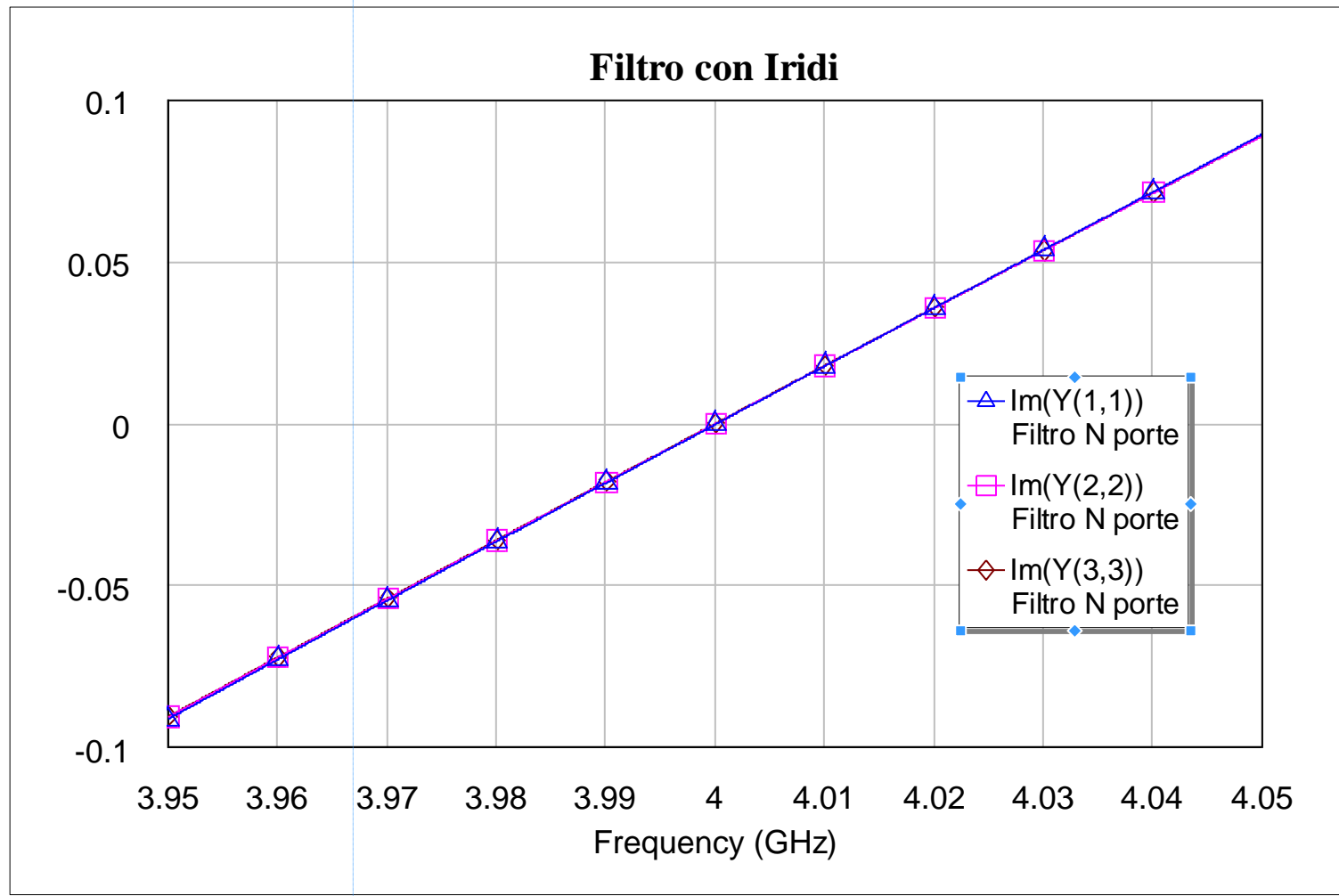

Extracted $J_{i,i+1}$

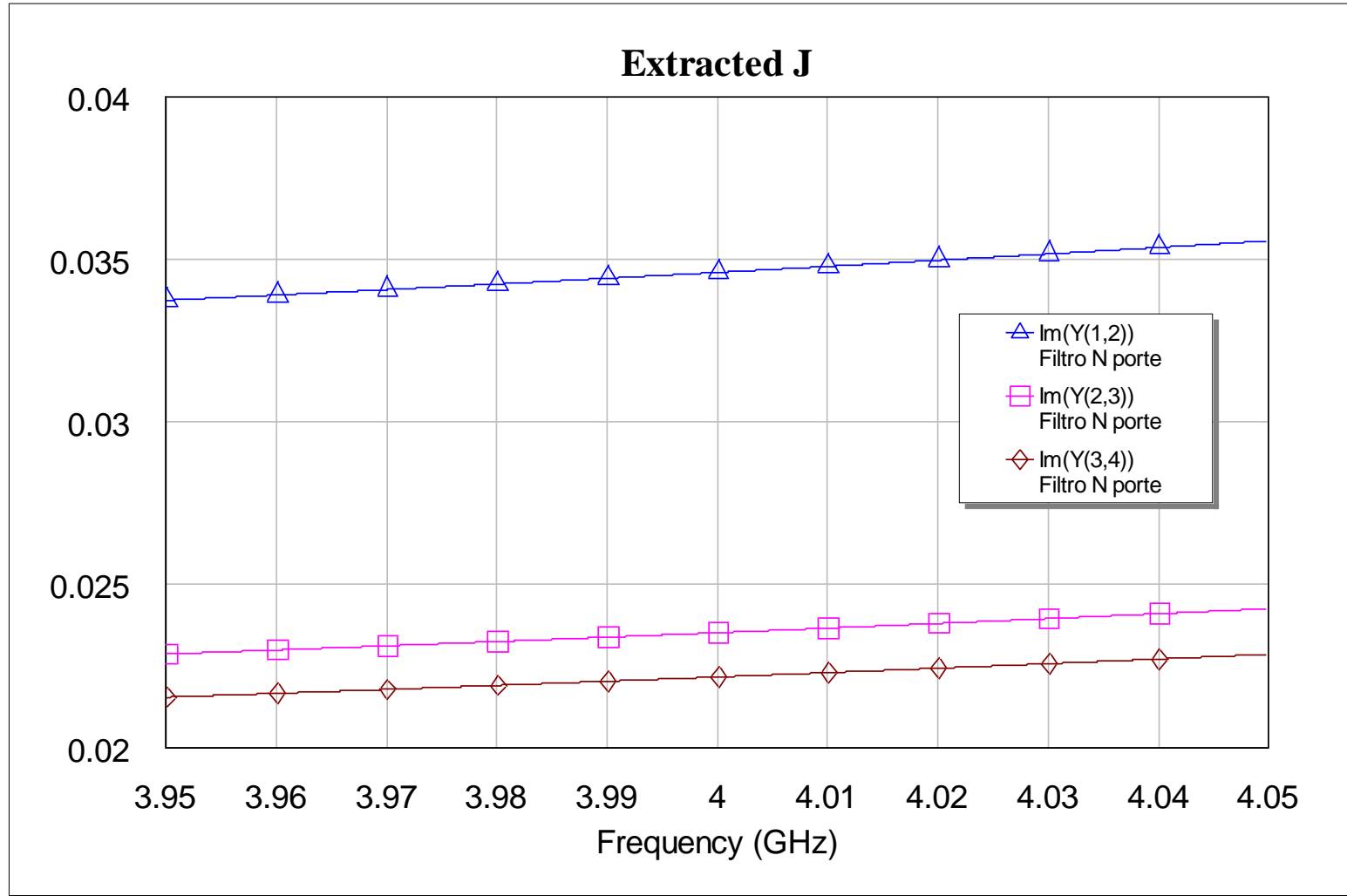

Computed Universal Parameters

Y11 = Filtro N porte:Y(1,1)
 Y22 = Filtro N porte:Y(2,2)
 Y33 = Filtro N porte:Y(3,3)
 Y12 = Filtro N porte:Y(1,2)
 Y23 = Filtro N porte:Y(2,3)
 Y34 = Filtro N porte:Y(3,4)

F=_FREQ*1e-6

B11=imag(Y11)
 B22=imag(Y22)
 B33=imag(Y33)

J12=imag(Y12)
 J23=imag(Y23)
 J34=imag(Y34)

I1=find_index(B11,0)
 I2=find_index(B22,0)
 I3=find_index(B33,0)

F[I1]: 4000
 F[I2]: 4000
 F[I3]: 4000

I0=find_index(F,4000)

Beq1=0.5*der(B11,F)
 Beq1=Beq1[I1]*F[I1]

Beq1: 3.611

Beq2=0.5*der(B22,F)
 Beq2=Beq2[I2]*F[I2]

Beq2: 3.59

Beq3=0.5*der(B33,F)
 Beq3=Beq3[I3]*F[I3]

Beq3: 3.588

Qext=Beq1/real(Y11[I1])

1/Qext: 0.01271

Synthesized:

k01= 0.01263

k12=J12[I0]/sqrt(Beq1*Beq2)

k12: 0.00961

k12=0.0096189

k23=J23[I0]/sqrt(Beq3*Beq2)

k23: 0.006554

k23=0.0065646

k34=J34[I0]/sqrt(Beq3*Beq3)

k34: 0.006176

k34=0.0061843