

---

# ***Lesson 1:*** ***Introduction on Filters and*** ***Backgrounds on Distributed*** ***Circuits***


***Giuseppe Macchiarella***  
Polytechnic of Milan, Italy  
Electronic and Information Department

---



# Representation of a physical structure


---

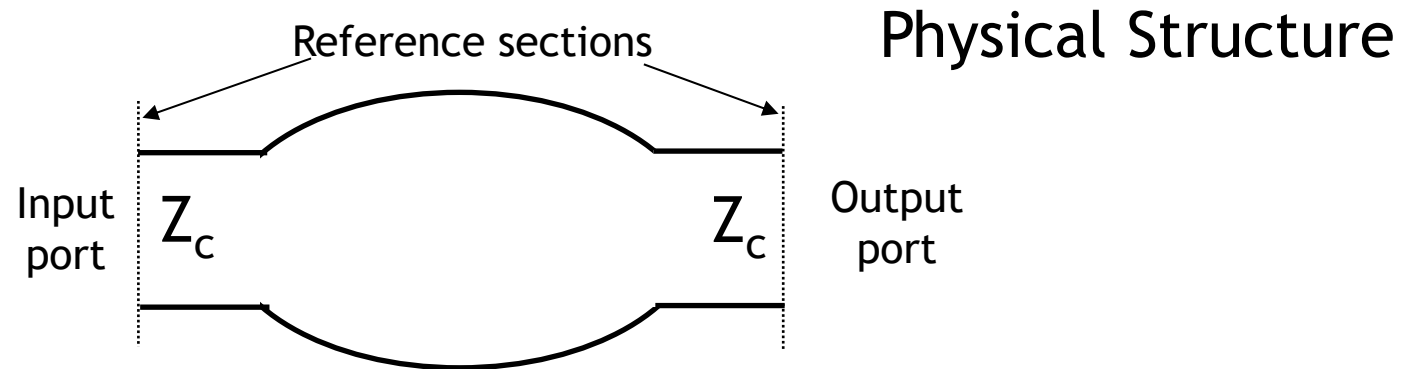

Given a physical structure, the Scattering Parameters ( $S$  matrix) allow a representation of its behavior in terms of the waves propagating on the transmission lines that connect the structure with the external world. Each line is characterized by its characteristic impedance ( $Z_c$ ), the phase velocity ( $v$ ) and a reference section (defined *port*) at which the structure is observed. The physical structure must be linear to allow the  $S$  parameters characterization.

# Power Wave definition


---

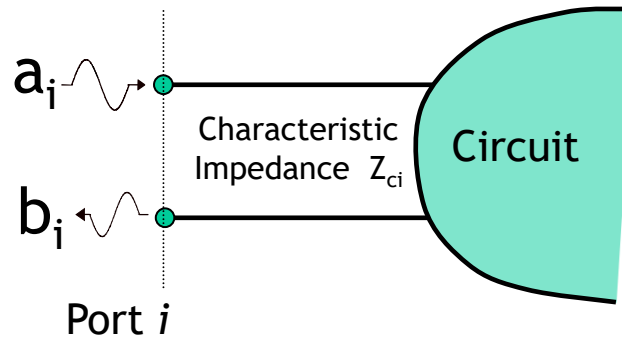

$(1/2) |a_i|^2$ : Incident power wave = Available power from a source with impedance  $Z_{ci}$

$(1/2) |b_i|^2$ : Reflected power wave = Difference between the available power and the power absorbed by the port (i.e. flowing into the port)

# Definition of conventional $V$ and $I$

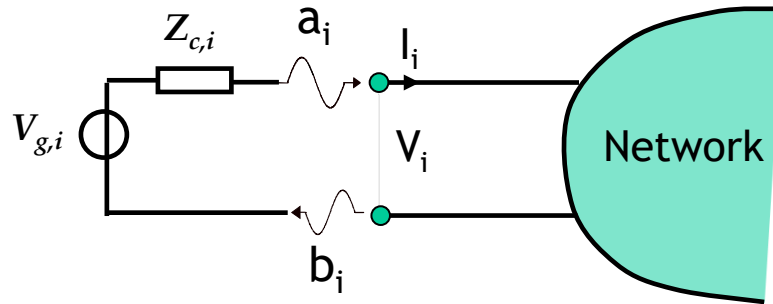

$$V_{g,i} = Z_{c,i}I_i + V_i$$


$$P_{IN,i} = \frac{1}{2} \operatorname{Re}\{V_i \cdot I_i^*\}$$

$$P_{av,i} = \frac{|V_{g,i}|^2}{8 \cdot \operatorname{Re}\{Z_{c,i}\}} = \frac{|V_i + Z_{c,i} \cdot I_i|^2}{8 \cdot \operatorname{Re}\{Z_{c,i}\}} = \frac{1}{2} |a_i|^2 \Rightarrow a_i = \frac{V_i + Z_{c,i} \cdot I_i}{2\sqrt{\operatorname{Re}\{Z_{c,i}\}}} = I_i \frac{Z_i + Z_{c,i}}{2\sqrt{\operatorname{Re}\{Z_{c,i}\}}}$$

$$P_{IN,i} = \frac{1}{2} \operatorname{Re}\{V_i \cdot I_i^*\} = \frac{1}{2} (|a_i|^2 - |b_i|^2) \Rightarrow b_i = \frac{V_i - Z_{c,i}^* \cdot I_i}{2\sqrt{\operatorname{Re}\{Z_{c,i}\}}} = I_i \frac{Z_i - Z_{c,i}^*}{2\sqrt{\operatorname{Re}\{Z_{c,i}\}}}$$

$$\left( a_i = \frac{I_i + Y_{c,i} \cdot V_i}{2\sqrt{\operatorname{Re}\{Y_{c,i}\}}}, \quad b_i = \frac{-I_i + Y_{c,i}^* \cdot V_i}{2\sqrt{\operatorname{Re}\{Y_{c,i}\}}} \right)$$

# Power and Voltages waves

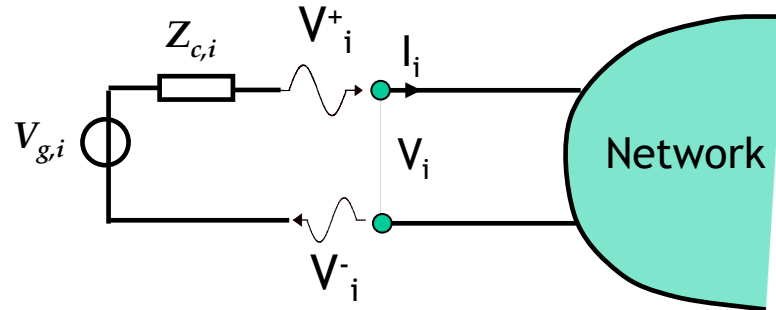

$$V_i = V_i^+ + V_i^-, \quad I_i = I_i^+ + I_i^-$$

$$V_i^+ = Z_{c,i} I_i^+, \quad V_i^- = -Z_{c,i} I_i^-$$

Power waves:

$$a_i = \frac{V_i + Z_{c,i} \cdot I_i}{2\sqrt{\text{Re}\{Z_{c,i}\}}}, \quad b_i = \frac{V_i - Z_{c,i}^* \cdot I_i}{2\sqrt{\text{Re}\{Z_{c,i}\}}}$$

Voltage waves:

$$V_i^+ = \frac{V_i + Z_{c,i} \cdot I_i}{2}, \quad V_i^- = \frac{V_i - Z_{c,i} \cdot I_i}{2}$$

Absence of reflected wave:

Conjugate matching


$$Z_i = Z_{c,i}^*$$

Matching

$$Z_i = Z_{c,i}$$

Coincide for  $Z_{c,i}$  real

# Generalized Scattering Matrix

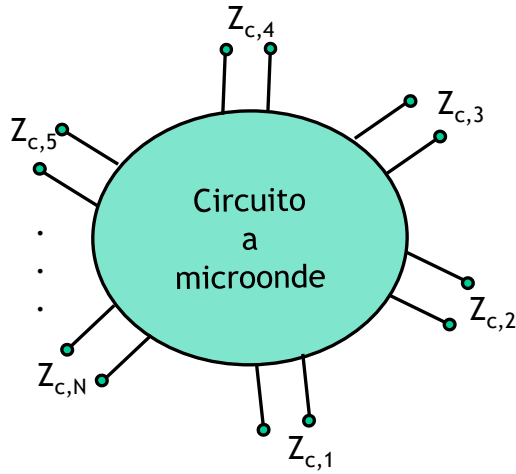

For a linear circuit, incident and reflected waves are linearly related:

$$b_1 = s_{11}a_1 + s_{12}a_2 + \dots + s_{1N}a_N$$

$$b_2 = s_{21}a_1 + s_{22}a_2 + \dots + s_{2N}a_N$$

.....

$$b_N = s_{N1}a_1 + s_{N2}a_2 + \dots + s_{NN}a_N$$

In matrix form:

$$\underline{\mathbf{b}} = \underline{\mathbf{S}} \cdot \underline{\mathbf{a}}$$

$$\underline{\mathbf{S}} = \begin{pmatrix} s_{11} & \dots & s_{1N} \\ \vdots & \ddots & \vdots \\ s_{N1} & \dots & s_{NN} \end{pmatrix}$$

# Meaning of S parameters

---

$$S_{ii} = \left. \frac{b_i}{a_i} \right|_{a_{k \neq i} = 0}$$



Reflection coefficient at port  $i$  when the other ports are connected to their reference impedances  $Z_{c_j}$  (*matched*)


$$S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_{k \neq j} = 0}$$



Transmission coefficient from port  $j$  to port  $i$  with the other ports matched. Note that  $|s_{ij}|^2$  represents the transducer power gain between the two ports

# S matrix of 2-port passive network

---

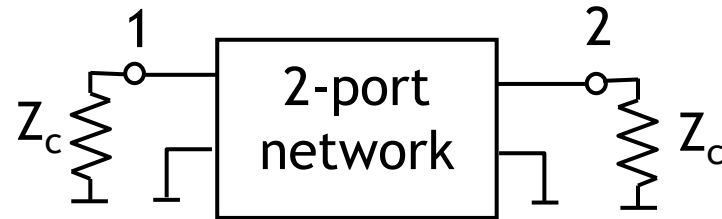

Equivalent  
Representation

$S_{11}$ ,  $S_{22}$  = Reflection at the ports

$S_{21}$ ,  $S_{12}$  = Transmission between the ports

Passive structures imply:  $|S_{i,j}| < 1$

Moreover, for reciprocal structures:  $S_{12} = S_{21}$

Lossless structures implies:  $|S_{11}|^2 + |S_{12}|^2 = 1$

In filters application transmission parameters are replaced by their inverse ( $> 1$ ). In decibel it has:

$$\text{Attenuation (dB)} = -20 \log_{10}(|S_{21}|)$$



# A very general definition of RF Filters

---

“A RF filter is a 2-port junction exhibiting a selective frequency behavior in the transmission from the input port to the output port”


**Passband(s):** Frequency band(s) which is transferred from input to output without attenuation (ideally)

**Stopband(s):** Frequency band(s) where the transmission is blocked. In general, the signal rejection is obtained by reflection


# Basic Classification

Filter are classified according to the number and location of passbands and stopbands. The most basic classification considers 4 filters classes:

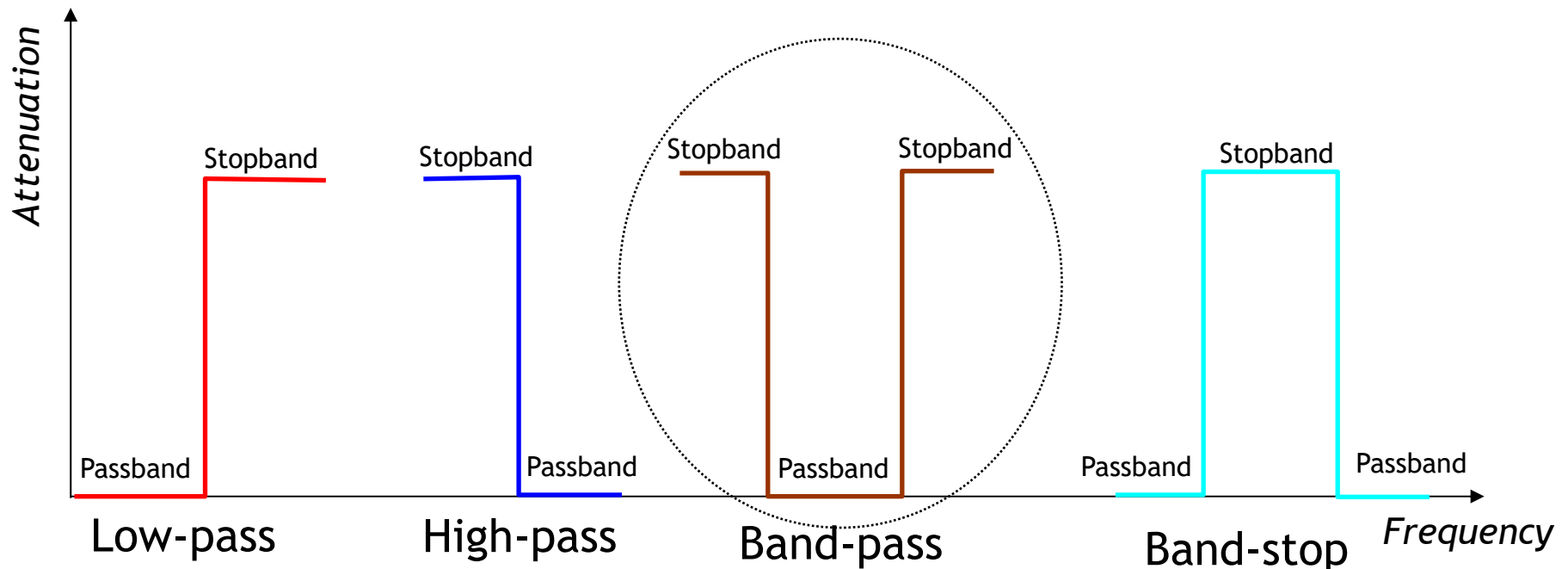**Low-pass, High-pass, Band-pass, Band-stop**


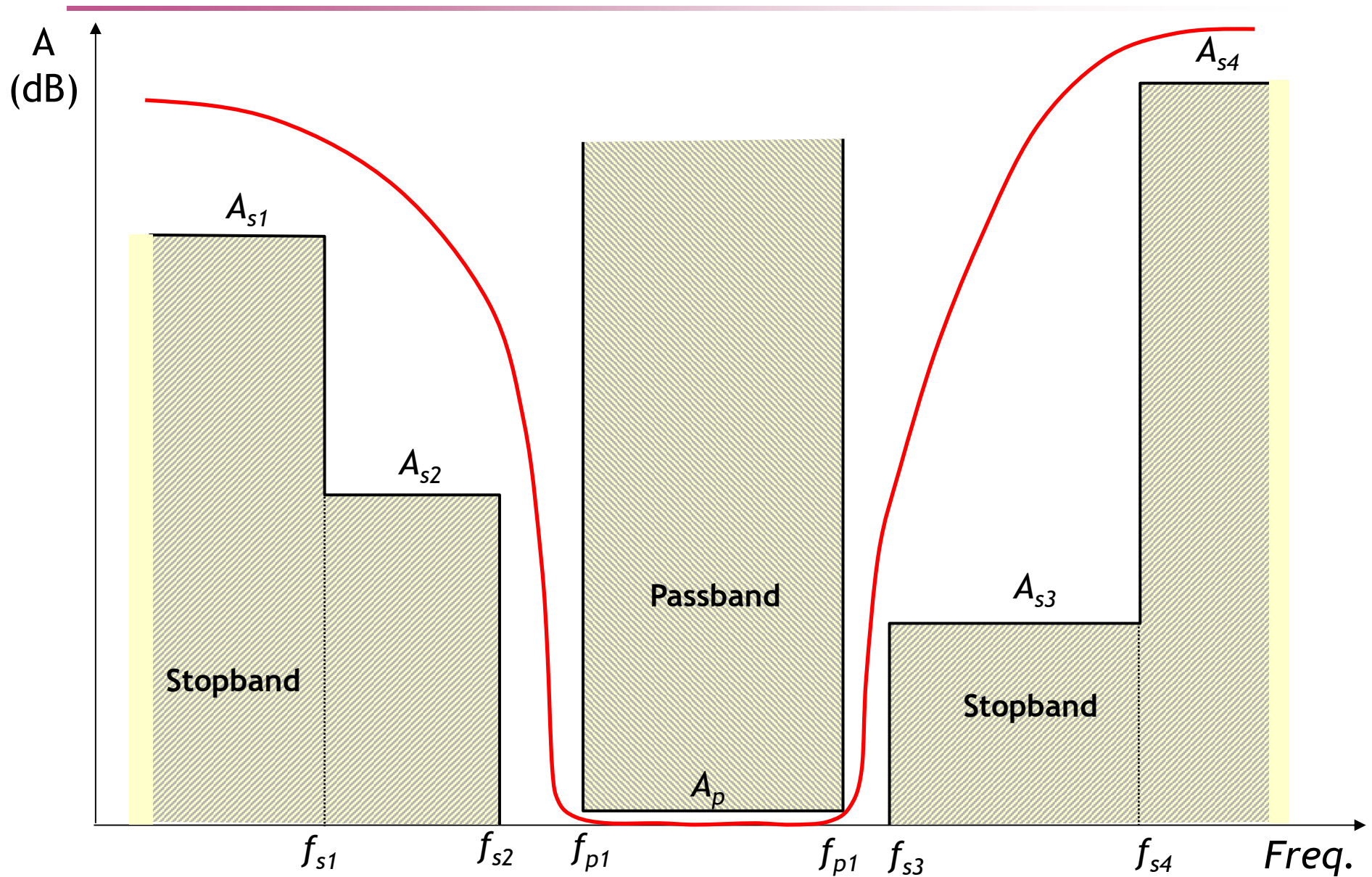
# Specification of filter requirements: the Attenuation Mask



# Attenuation and matching

---


Ideally, a filter is a lossless network. In this case the attenuation in the passband is produced only by the not perfect match at input/output ports.

In the real world the filter components introduce **dissipation**, which becomes the main contribution to passband attenuation.

Passband Losses affect very few (in general) the port matching

**In addition to the attenuation mask (which refer to overall attenuation) must be then specified also the matching requirements at the ports**
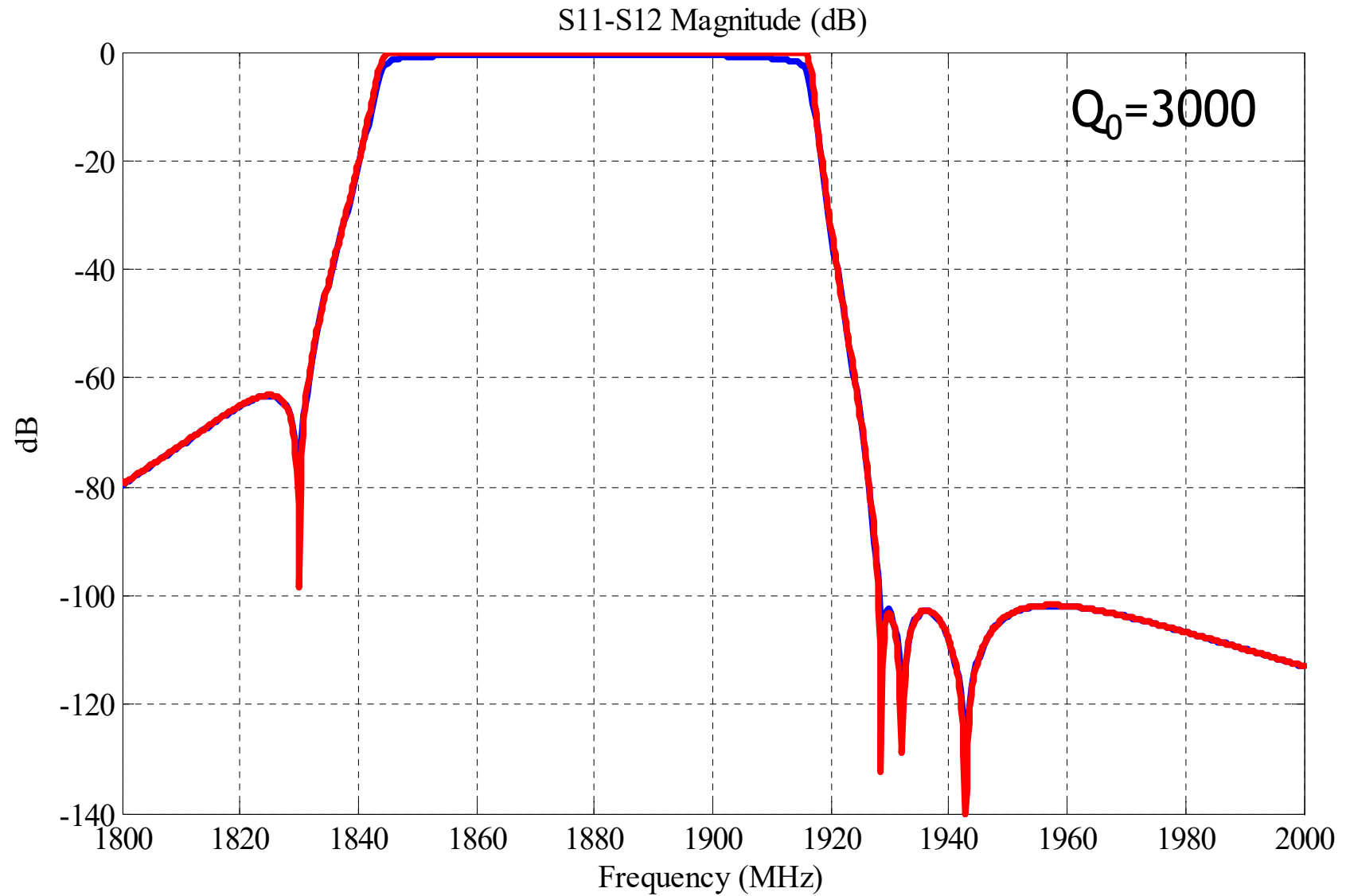
# Effect produced by losses on attenuation shape



## Requirements on transmission phase

---

- ❑ To have a distortion-less two port, the phase of transmission parameter should be linear in the passband
- ❑ Often, the requirement is given on the *group delay*, which is defined as the derivative of transmission phase with respect the radian frequency. The group delay should be ideally constant in the passband
- ❑ Phase linearity is generally assessed a posteriori, after the attenuation requirements are satisfied.
- ❑ If the requirements on phase linearity is not verified, a *phase equalizer* may be required.
- ❑ In alternative, complex transmission zeros can be introduced in the response for phase equalization

# Approaches to the design of microwave filters

---

- ❑ Image parameters methods (old technique based on attenuation produced by basic blocks, which are suitably interconnected).
- ❑ Synthesis of networks composed by commensurate transmission line sections and stubs (suited for broadband filters; poses strong bounds on the configuration of the filter structure)
- ❑ Equivalent Synthesis method, based on the equivalence between the real (distributed components) structure and a lumped component filter network (suitable for narrow and moderate bandwidth passband filters. The most used technique today)

# Advantages of the Equivalent Synthesis Method

---

- ❑ Precise control of the curve representing the filter response
- ❑ The synthesis is developed in the lumped-element world, where well established, analytical and numerical procedures are available
- ❑ The results of the synthesis can be expressed by means of universal parameters which maintain the same meaning both for lumped-element circuit and distributed microwave networks
- ❑ A first-order dimensioning of the physical structure can be easily performed using these universal parameters




---

*Recalls on Microwave Circuits  
for Filter Design*

# General physical structure of a microwave filter

---

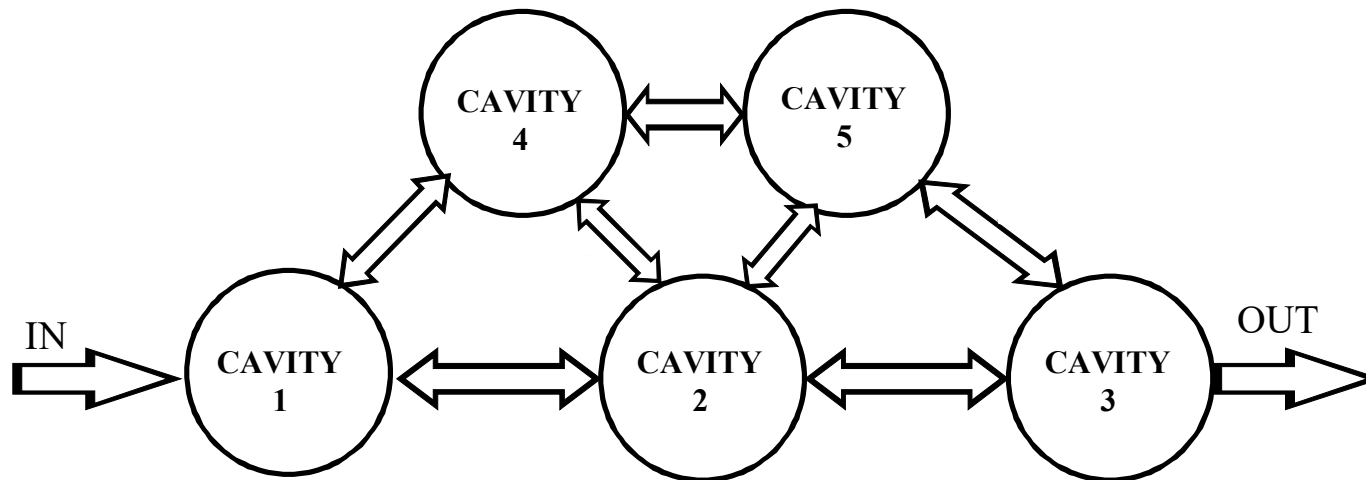



Basic components:

- Cavities (resonating on a specific mode)
- Coupling structures (represented as  $\longleftrightarrow$  )

Not always cavities and couplings can be identified separately

# Basic equivalent circuit of the cavity

---

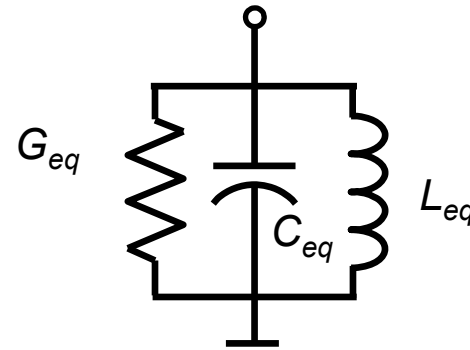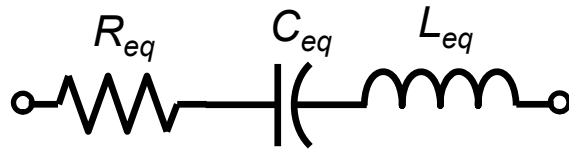


Series or parallel resonator

## Characteristic parameters:

- Mode Resonant frequency ( $f_0$ )
- Equivalent slope parameter ( $L_{eq}$ ,  $C_{eq}$ )
- Loss parameter ( $R_{eq}$ ,  $G_{eq}$ )
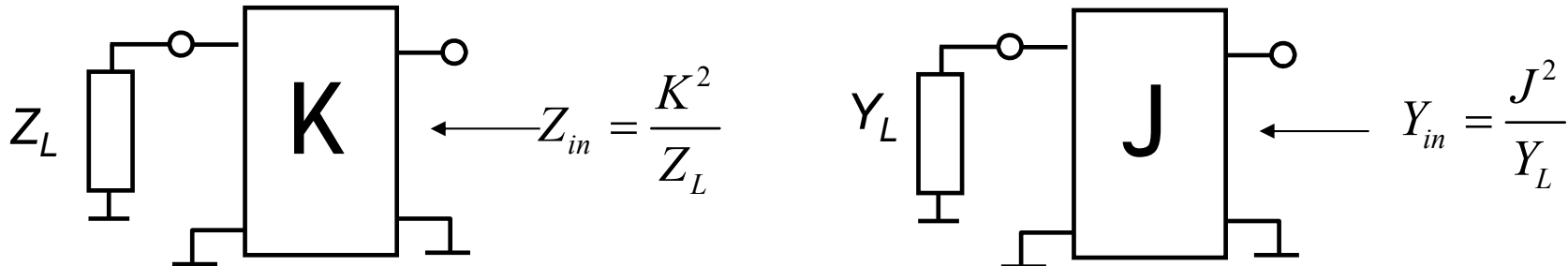
# Basic equivalent circuit of the coupling

Couplings are generally modeled with impedance or admittance inverters



The inverter has two basic functions:

- Operate as impedance transformer
- Change the nature of the load

**The inverter is an ideal component that can only be approximated by real elements in a limited frequency band**

# S parameters of the Impedance Inverter


---

$$S_{11} = S_{22} = \frac{\frac{K^2}{Z_0} - Z_0}{\frac{K^2}{Z_0} + Z_0} = \frac{K^2 - Z_0^2}{K^2 + Z_0^2} \quad \text{Real (positive or negative)}$$
$$\phi_{11} - \phi_{12} = \pm \frac{\pi}{2} \quad \Rightarrow \quad \phi_{12} = \pm \frac{\pi}{2}$$


The impedance inverter is a symmetrical and reciprocal 2-port network. It behaves as an ideal  $\pi/2$  phase shifter.

Imposing the lossless condition and the K value it is not sufficient to identify univocally the network (the  $\pm$  sign of  $\phi_{12}$  remains undetermined)

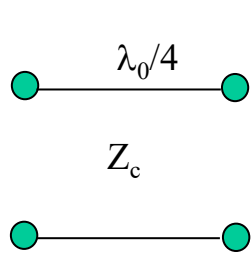
# Equivalent circuit for the impedance inverter




$$K = Z_c$$

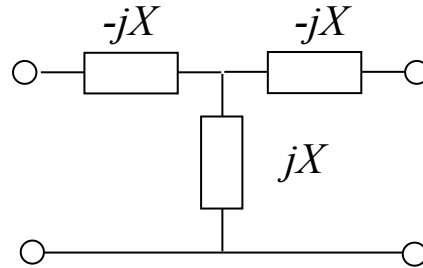

$$K = X$$

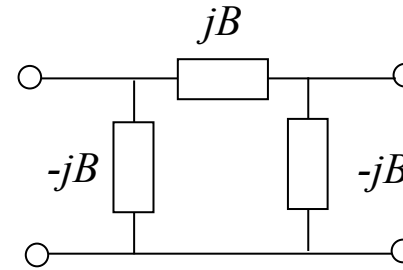


$$J = 1/K = B$$

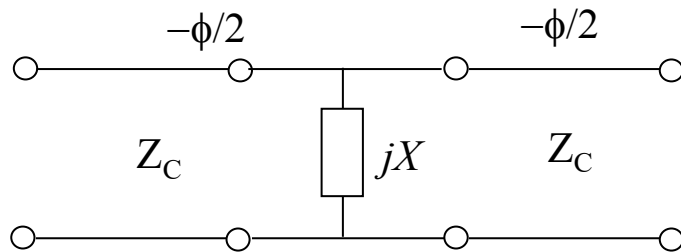

$$K = |Z_c \tan(\phi/2)|$$

$$\frac{\phi}{2} = \frac{1}{2} \tan^{-1} \left( \frac{2X}{Z_c} \right)$$
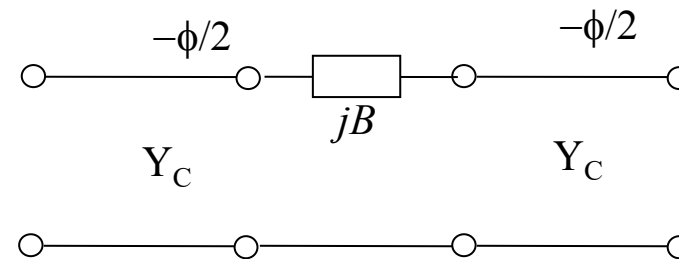
$$\frac{X}{Z_c} = \frac{K/Z_c}{1 - (K/Z_c)^2}$$




$$J = |Y_c \tan(\phi/2)|$$

$$\frac{\phi}{2} = \frac{1}{2} \tan^{-1} \left( \frac{2B}{Y_c} \right)$$

$$\frac{B}{Y_c} = \frac{J/Y_c}{1 - (J/Y_c)^2}$$

# Modeling of a microwave junction with a lumped equivalent circuit (1-port)

---

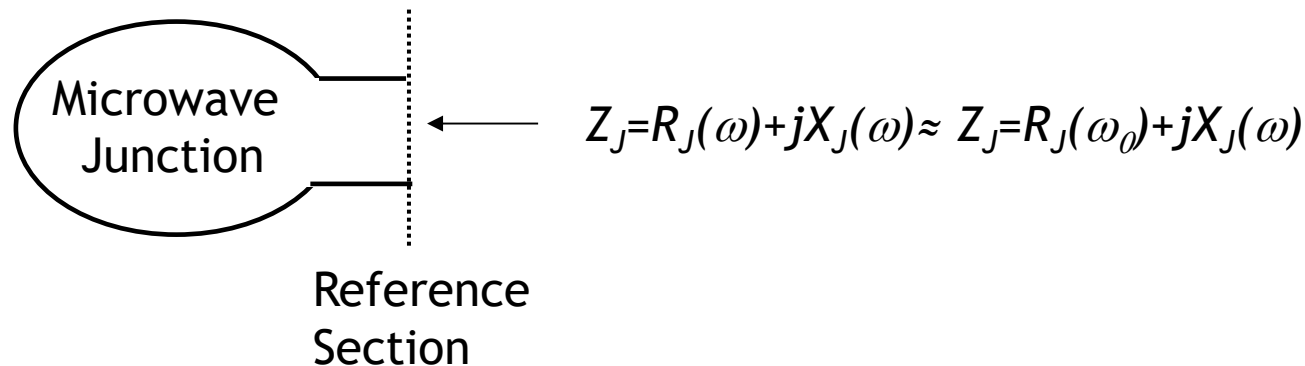


**Goal:** model of the junction in a defined frequency range  $B$  around  $f_0$  ( $B \ll f_0$ )

The model is represented by an equivalent lumped-element impedance  $Z_{eq} = R_{eq} + jX_{eq}$  obtained by imposing:

- Constant real part:  $R_{eq} = R_J(\omega_0)$
- Same value at  $\omega_0$  of the imaginary part:  $X_{eq}(\omega_0) = X_J(\omega_0)$
- Same value of derivative at  $\omega_0$ :  $\partial X_{eq}(\omega_0) / \partial \omega = \partial X_J(\omega_0) / \partial \omega$
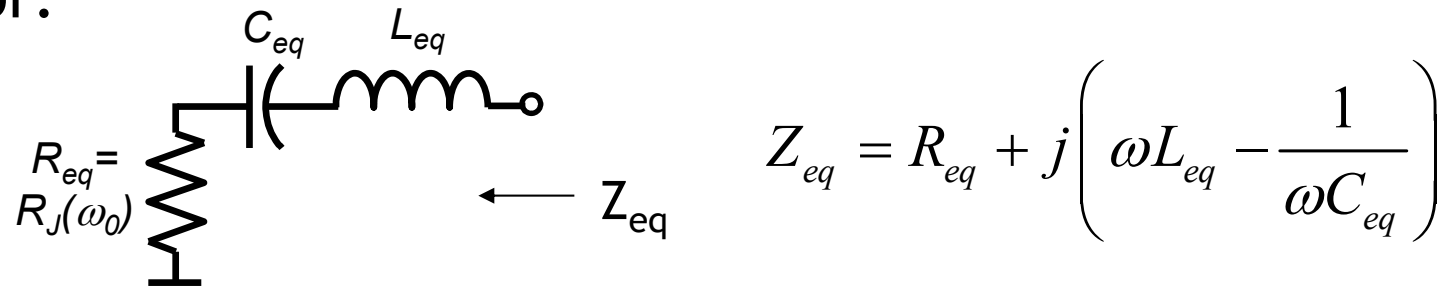
# Equivalent impedance $Z_{eq}$

The most elementary network exhibiting  $Z_{eq}$  is a series resonator:



Imposing the previous conditions:


$$X_{eq}(\omega_0) = \omega_0 L_{eq} - \frac{1}{\omega_0 C_{eq}} = X_J(\omega_0)$$

$$\left. \frac{\partial X_{eq}(\omega)}{\partial \omega} \right|_{\omega=\omega_0} = L_{eq} + \frac{1}{\omega_0^2 C_{eq}} = \left. \frac{\partial X_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0}$$

$$L_{eq} = \frac{1}{2} \left[ \left. \frac{\partial X_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0} + \frac{X_J(\omega_0)}{\omega_0} \right], \quad \frac{1}{\omega_0^2 C_{eq}} = \frac{1}{2} \left[ \left. \frac{\partial X_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0} - \frac{X_J(\omega_0)}{\omega_0} \right]$$


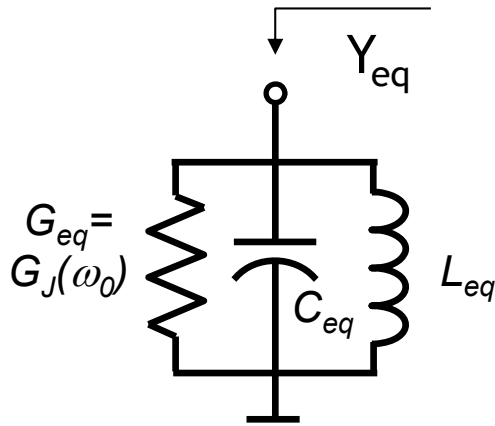
# Equations for the Equivalent Admittance



$$Y_{eq} = G_{eq} + j \left( \omega C_{eq} - \frac{1}{\omega L_{eq}} \right)$$

Imposing the previous conditions:


$$B_{eq}(\omega_0) = \omega_0 C_{eq} - \frac{1}{\omega_0 L_{eq}} = B_J(\omega_0)$$

$$\left. \frac{\partial B_{eq}(\omega)}{\partial \omega} \right|_{\omega=\omega_0} = C_{eq} + \frac{1}{\omega_0^2 L_{eq}} = \left. \frac{\partial B_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0}$$

$$C_{eq} = \frac{1}{2} \left[ \left. \frac{\partial B_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0} + \frac{B_J(\omega_0)}{\omega_0} \right], \quad \frac{1}{\omega_0^2 L_{eq}} = \frac{1}{2} \left[ \left. \frac{\partial B_J(\omega)}{\partial \omega} \right|_{\omega=\omega_0} - \frac{B_J(\omega_0)}{\omega_0} \right]$$
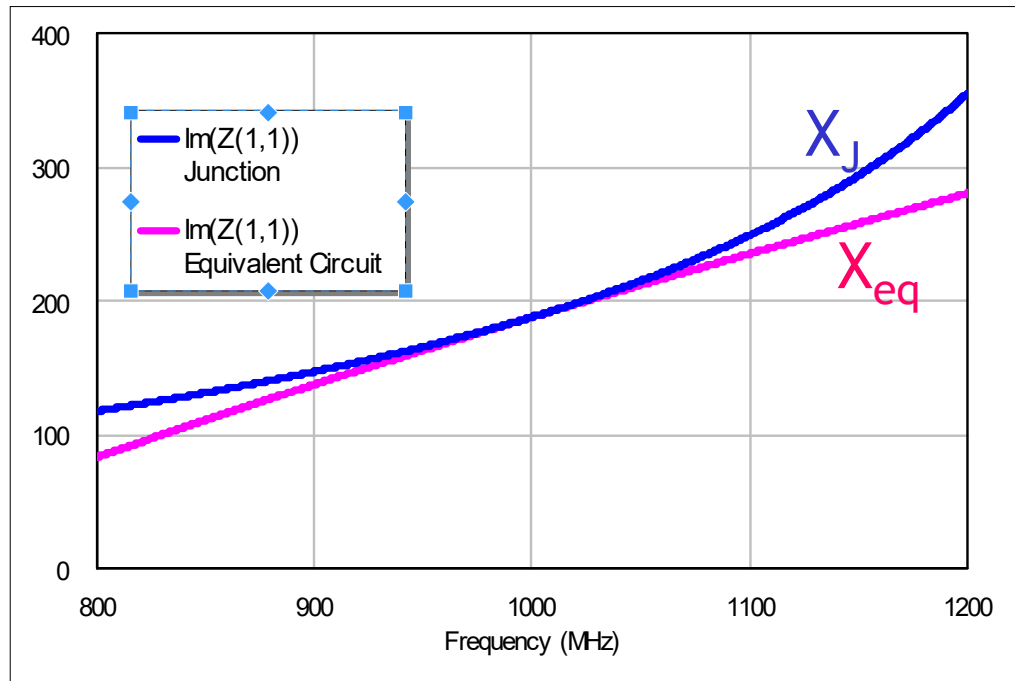
## Remark on the equivalent network

- The equivalence between the microwave junction and the lumped-element equivalent circuit is exact only at  $f_0$
- The deviation between  $Z_J$  ( $Y_J$ ) and  $Z_{eq}$  ( $Y_{eq}$ ) becomes larger and larger with the increase of  $B$



$$f_0 = 1000 \text{ MHz}$$
$$X(f_0) = 188.4 \Omega$$

## Special case: Resonant Junction (Cavity)

---


In case of resonant junctions ( $X_J(\omega_0)=0$ ,  $B_J(\omega_0)=0$ ), the previous equations become:

$$L_{eq} = \frac{1}{2} \frac{\partial X_J(\omega)}{\partial \omega} \Big|_{\omega=\omega_0} \quad C_{eq} = \frac{1}{\omega_0^2 L_{eq}}$$
$$C_{eq} = \frac{1}{2} \frac{\partial B_J(\omega)}{\partial \omega} \Big|_{\omega=\omega_0} \quad L_{eq} = \frac{1}{\omega_0^2 C_{eq}}$$


These equations define an equivalent circuit for a large class of **cavity resonators**.

The type of resonator depends on the **resonant mode** and on the **reference section**
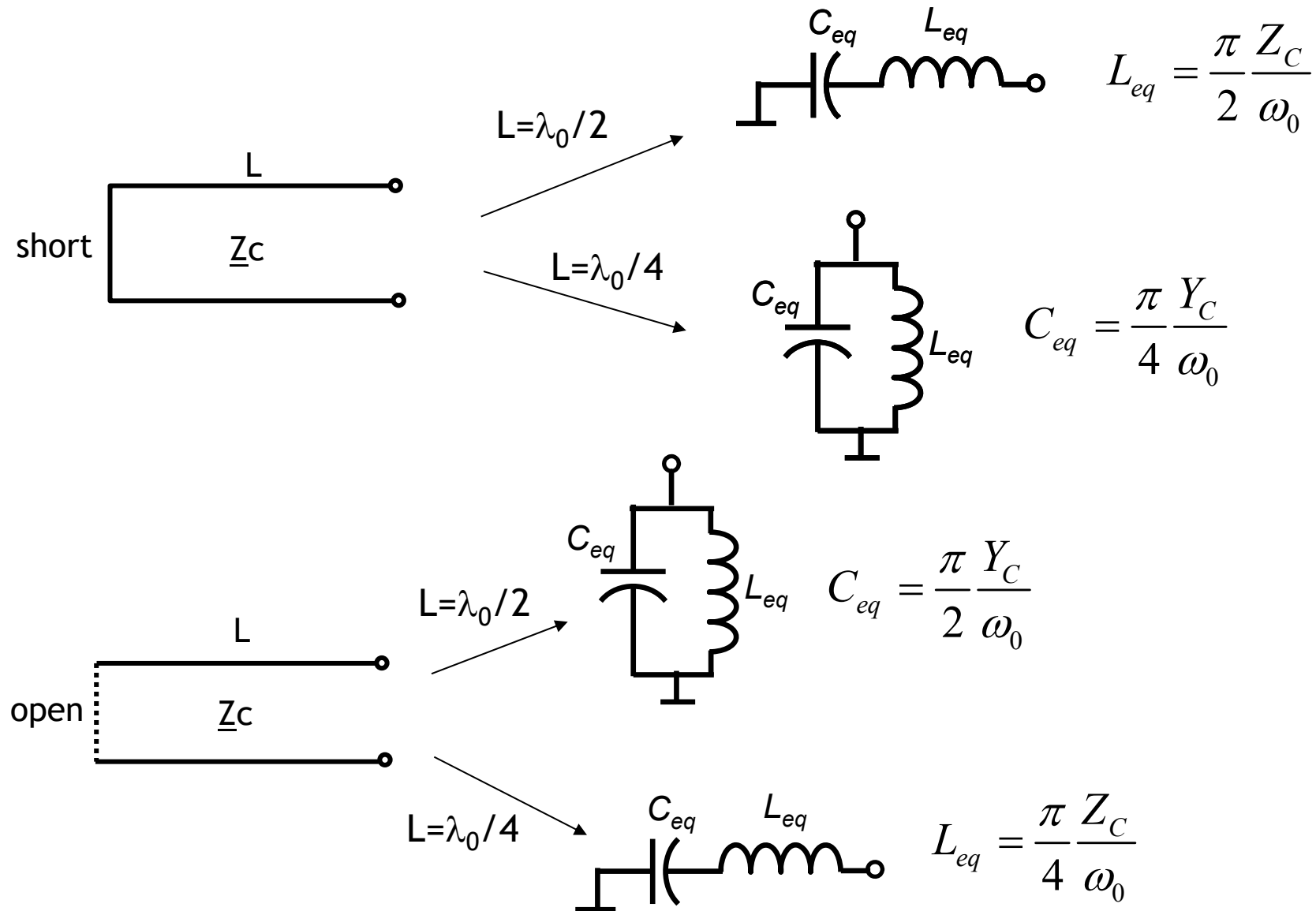
# Example: TEM cavity realized with short-circuited/ open-circuited transmission line



# Capacity-loaded coaxial resonator

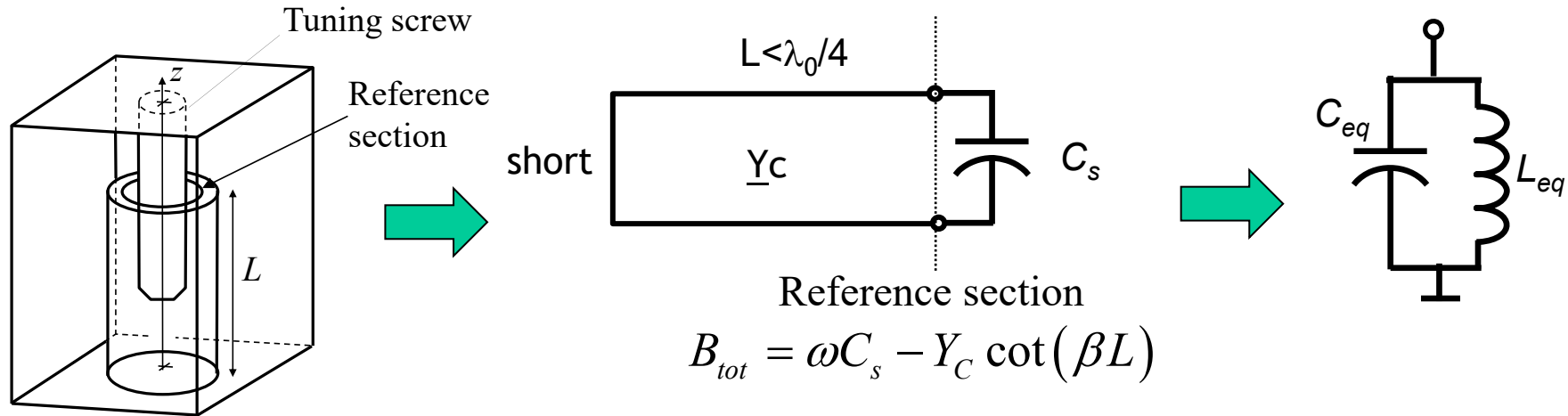

$$B_{tot} = \omega C_s - Y_C \cot(\beta L)$$


Resonance condition:

$$B_{tot}(\omega_0) = 0 \Rightarrow \omega_0 C_s = Y_C \cot(\beta_0 L)$$


Equivalent capacitance:

$$\begin{aligned} \omega_0 C_{eq} &= \frac{1}{2} \left. \frac{\partial B_{tot}(\omega)}{\partial \omega} \right|_{\omega=\omega_0} = \frac{1}{2} Y_C \left[ \cot(\beta_0 L) + \frac{\beta_0 L}{\sin^2(\beta_0 L)} \right] = \\ &= \frac{1}{2} Y_C \cot(\beta_0 L) \left[ 1 + \frac{2\beta_0 L}{\sin(2\beta_0 L)} \right] \Rightarrow \stackrel{L=\lambda_0/8}{\omega_0 C_{eq}} = \frac{Y_C}{2} \left[ 1 + \frac{\pi}{2} \right] \end{aligned}$$

## Losses in the cavity: the unloaded Q

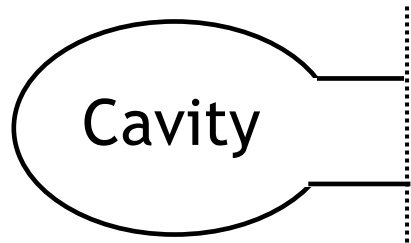
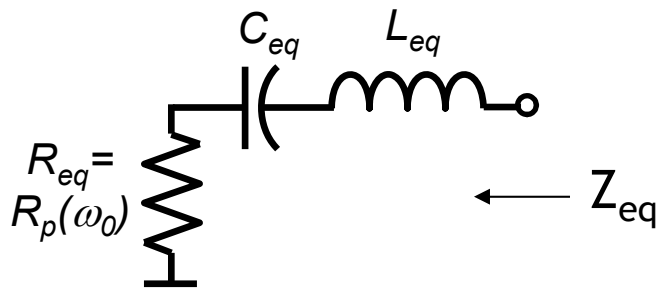
$$Q_0 = \omega_0 \frac{\text{Energy stored in the junction}}{\text{Power dissipated in the junction}}$$




$$Q_0 = \frac{\omega_0 L_{eq}}{R_p} \quad R_p = R_J + R_\epsilon$$

$R_J$  is the sum of two terms:  $R_p$ , due to the finite conductivity of metallic walls and  $R_\epsilon$  due to medium dissipation (dielectric losses). It has then:


$$\frac{1}{Q_0} = \frac{1}{Q_{0J}} + \frac{1}{Q_{0\epsilon}}$$

# Modeling of a cavity coupled to loads

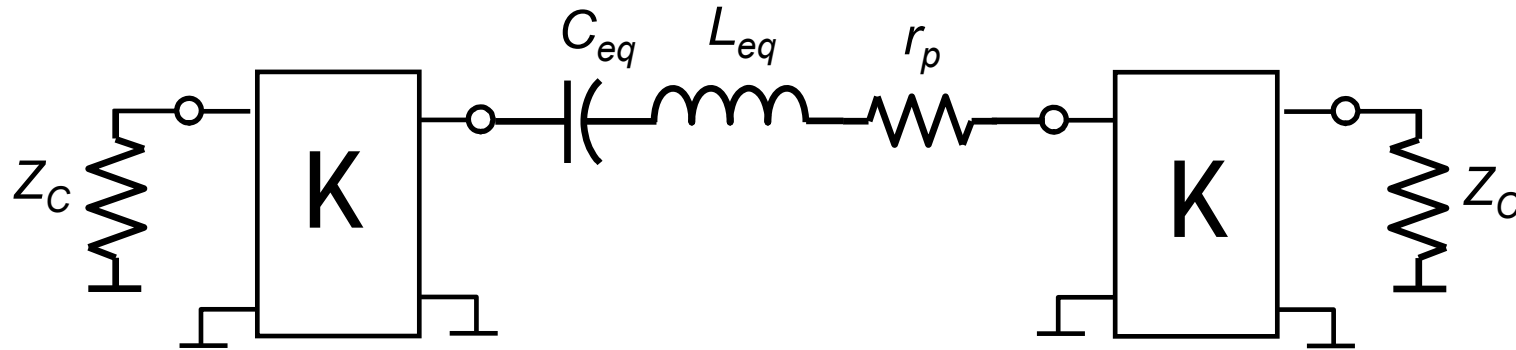

$$Q_L = \frac{\omega_0 L_{eq}}{2K^2/Z_C} = \frac{f_0}{B_{3dB}} \quad (\text{for } r_p \ll K^2/Z_C)$$

$$Q_0 = \frac{\omega_0 L_{eq}}{r_p}$$

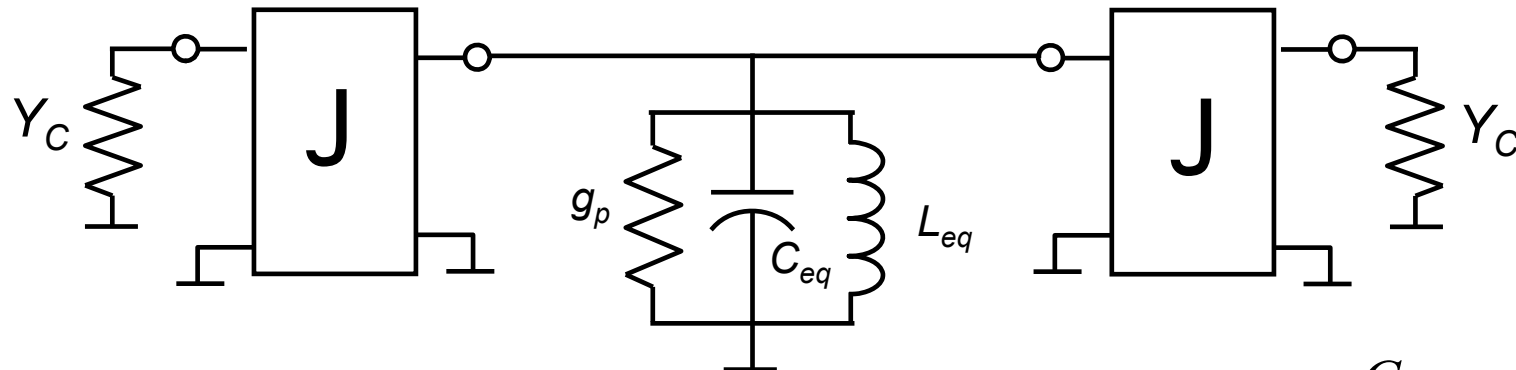

$$Q_L = \frac{\omega_0 C_{eq}}{J^2/Y_C} = \frac{f_0}{B_{3dB}} \quad (\text{for } g_p \ll J^2/Y_C)$$

$$Q_0 = \frac{\omega_0 C_{eq}}{g_p}$$

# Parameters of loaded cavities

---

## The loaded Q (QL): determines

- The 3 dB bandwidth ( $B_{3dB}=f_0/Q_L$ ). For a given cavity ( $L_{eq}$  or  $C_{eq}$ ), a value for K (J) can be evaluated for obtaining the desired  $B_{3dB}$ :


$$K = \sqrt{\frac{Z_C \cdot \omega_0 L_{eq}}{2Q_L}}, \quad J = \sqrt{\frac{Y_C \cdot \omega_0 C_{eq}}{2Q_L}}$$

- The matching band at the input (output) port. For small losses, it can be shown that the bandwidth  $B_\Gamma$  for a given value  $\Gamma$  of the input reflection coefficient is related to  $B_{3dB}$  as follows:

$$B_\Gamma \simeq |\Gamma| \cdot B_{3dB}$$



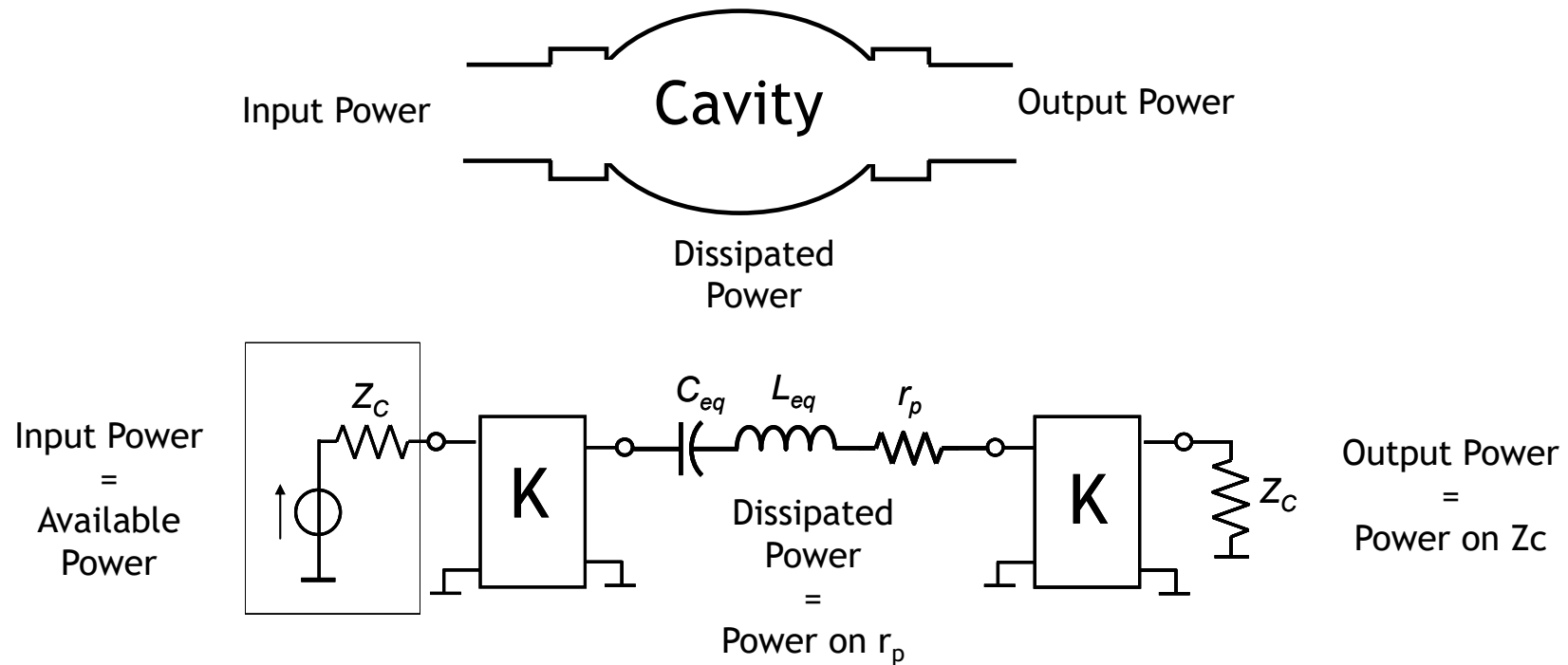
# Power transmitted to load (transducer attenuation)



$$A_{dB} = 20 \log \left( 1 + \frac{Q_L}{Q_0} \right)$$

# Coupling of two cavities: equivalent circuit

---

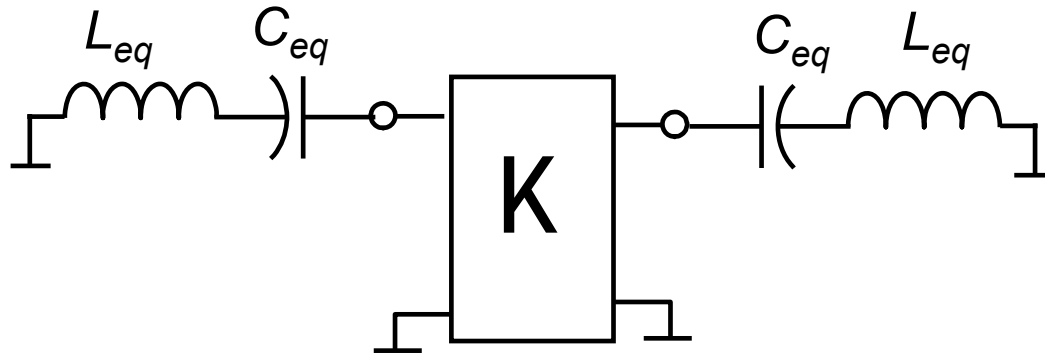



Characteristic parameter: the **coupling coefficient**

$$k = \frac{K}{\omega_0 L_{eq}} \quad \left( = \frac{J}{\omega_0 C_{eq}} \text{ for shunt resonators} \right)$$


$k$  determines the coupling bandwidth of the two resonators (the larger is  $k$  the larger is the bandwidth)
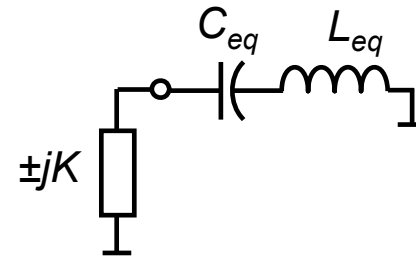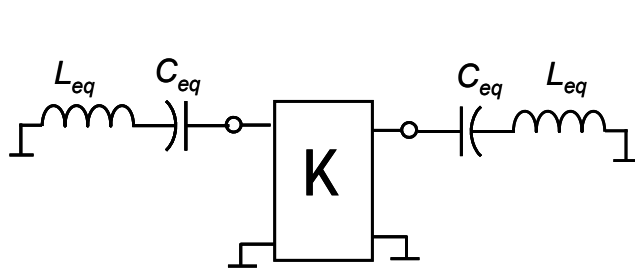
# Evaluation of $k$ from resonances

- Even and odd resonances of two coupled resonators:



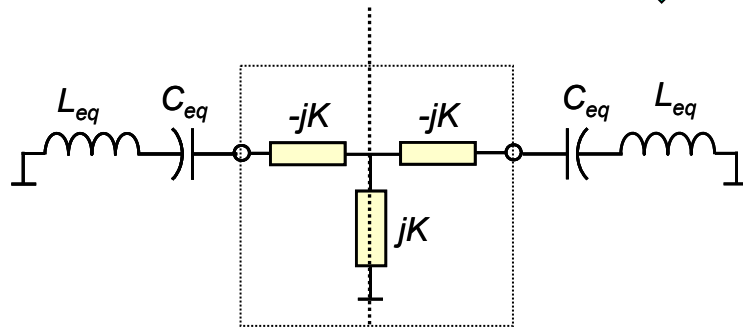Short  $\rightarrow$   $-jK$   
Open  $\rightarrow$   $+jK$




Short/Open

$$f_o = f_0 \left[ \sqrt{\left[ \left( \frac{K}{2\omega_0 L_{eq}} \right)^2 + 1 \right]} - \frac{K}{2\omega_0 L_{eq}} \right] \quad \text{Odd Resonance } (-jK)$$


$$f_e = f_0 \left[ \sqrt{\left[ \left( \frac{K}{2\omega_0 L_{eq}} \right)^2 + 1 \right]} + \frac{K}{2\omega_0 L_{eq}} \right] \quad \text{Even Resonance } (+jK)$$

$$f_0 = \sqrt{f_e \cdot f_o}, \quad k = \frac{f_e - f_o}{f_0}$$

# Practical evaluation of $k$

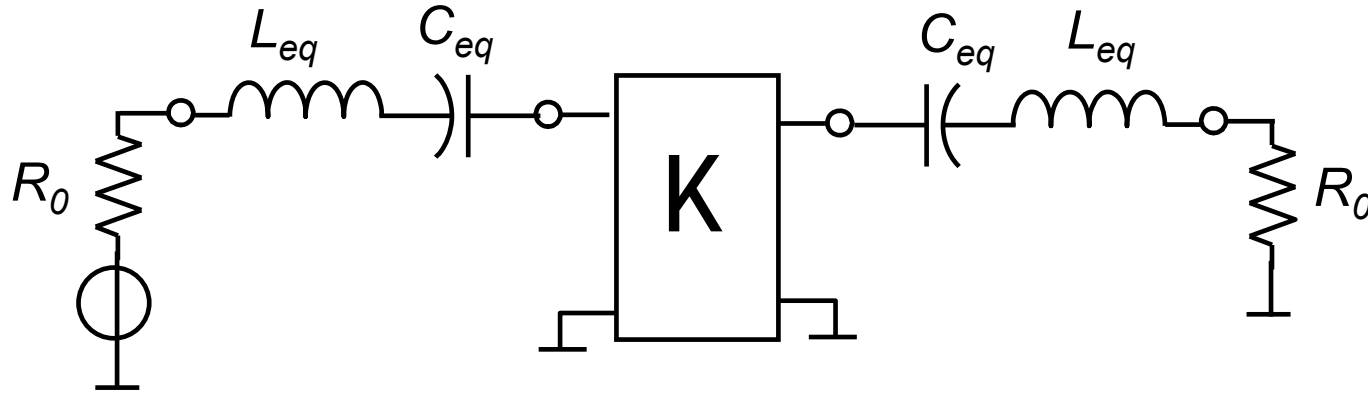

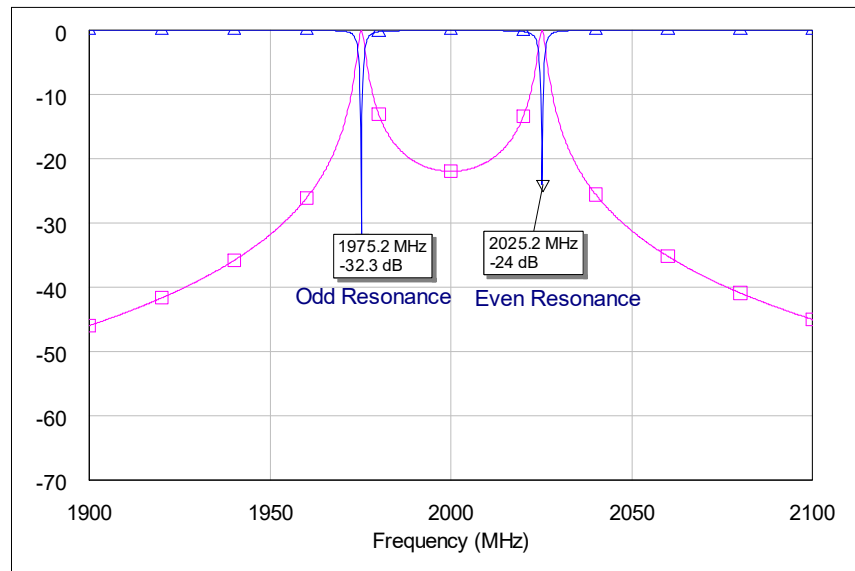$\omega_0 L_{eq} \gg R_0 \Rightarrow$  Input/output coupling  $\approx 0$



$$X_{eq} = 10, R_0 = 0.01$$


$$f_e = 2025.2 \text{ MHz}$$

$$f_o = 1975.2$$




$$f_0 = \sqrt{f_e \cdot f_o} = 2000 \text{ MHz}$$

$$k = \frac{f_e - f_o}{f_0} = 0.025$$

# Coupled cavities: example 1

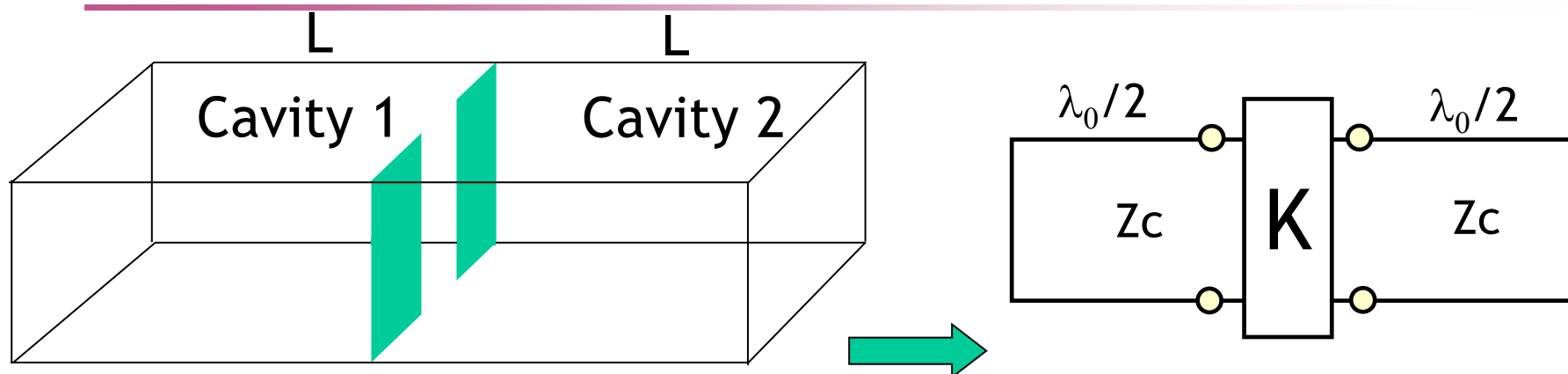


Inductive  
Iris ( $X_L$ )

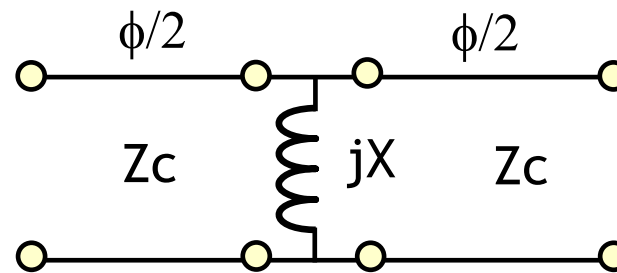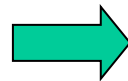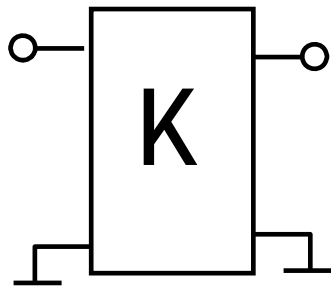

$$X = \frac{K}{1 - \left(\frac{K}{Z_c}\right)^2}, \quad \phi = -\tan^{-1}(2X)$$

## example 1 (cont.)


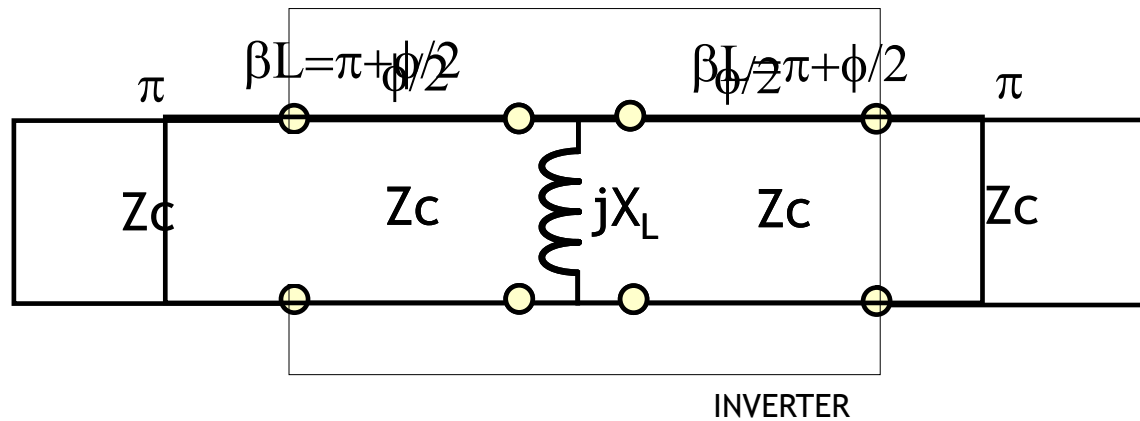


$$\beta L = \pi + \frac{\phi}{2} = \pi - \tan^{-1}(2X_L) \quad X_L = \frac{K}{1 - \left(\frac{K}{Z_C}\right)^2} \approx K \quad (\text{for } K \ll Z_C)$$

$$\text{Equiv. reactance: } \omega_0 L_{eq} = \frac{\pi}{2} Z_C \left(\frac{\lambda_g}{\lambda_0}\right)^2$$

$$\text{Coupling coefficient: } k = \frac{K}{\omega_0 L_{eq}} = \frac{2 X_L}{\pi Z_C} \left(\frac{\lambda_g}{\lambda_0}\right)^2$$
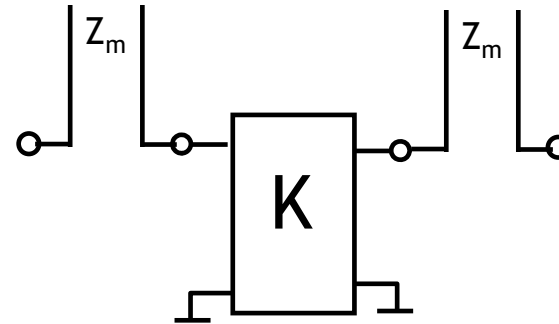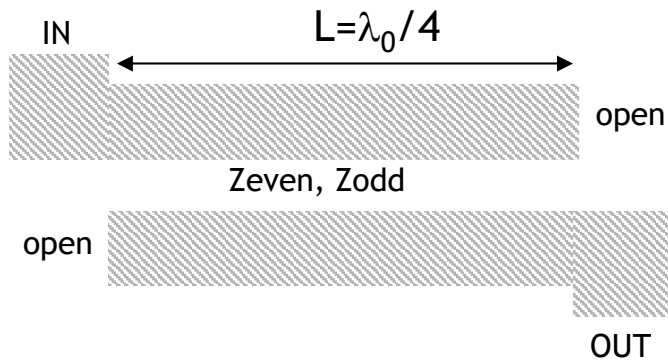
# Resonators with coupled lines: Interdigital





$$\omega_0 L_{eq} = \frac{\pi}{4} Z_m$$

$$Z_m = \frac{1}{2} (Z_{\text{even}} + Z_{\text{odd}})$$

$$K = \frac{1}{2} (Z_{\text{even}} - Z_{\text{odd}}) \frac{1}{\sin(\beta L)}$$

$$k = \frac{K}{\omega_0 L_{eq}} = \frac{4}{\pi} \left( \frac{Z_{\text{even}} - Z_{\text{odd}}}{Z_{\text{even}} + Z_{\text{odd}}} \right) = \frac{4}{\pi} m$$

# Resonators with coupled lines: Comb

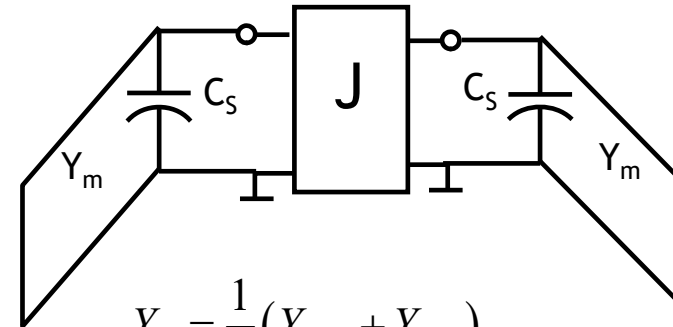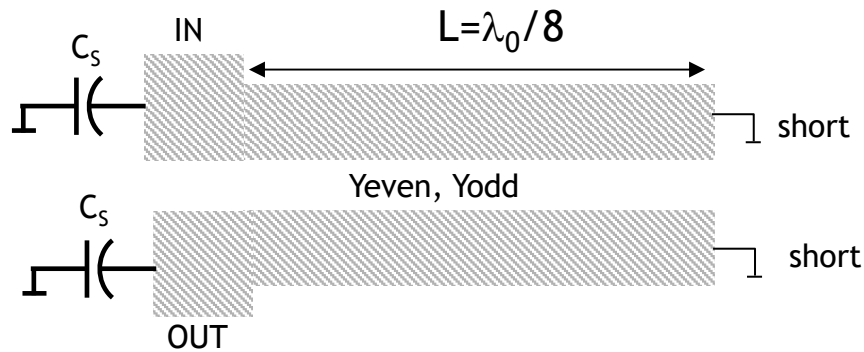

$$Y_m = \frac{1}{2}(Y_{\text{even}} + Y_{\text{odd}})$$

$$J = \frac{1}{2}(Y_{\text{even}} - Y_{\text{odd}}) \frac{1}{\tan(\beta L)}$$

$$\omega_0 C_{eq} = \frac{Y_m}{2} \left[ 1 + \frac{\pi}{2} \right],$$

$$k = \frac{J}{\omega_0 C_{eq}} = \frac{2}{\pi + 2} \left( \frac{Y_{\text{odd}} - Y_{\text{even}}}{Y_{\text{even}} + Y_{\text{odd}}} \right) = \frac{2m}{\pi + 2}$$


Note:  $\frac{Y_{\text{odd}} - Y_{\text{even}}}{Y_{\text{even}} + Y_{\text{odd}}} = \frac{Z_{\text{even}} - Z_{\text{odd}}}{Z_{\text{even}} + Z_{\text{odd}}} = m$


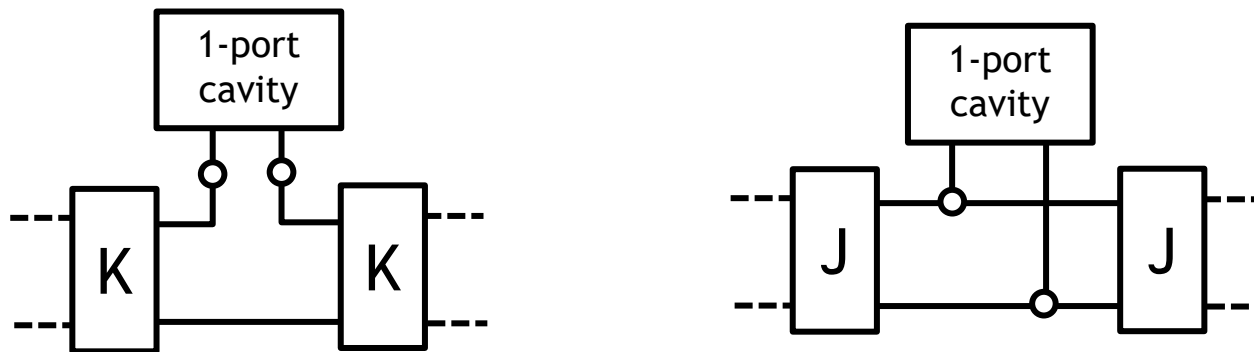
# 1-port and 2-port Cavities


---

Previous results refer to 1-port cavities that can be represented with a series or shunt resonator:




In case of 2-port cavities the equivalence should be imposed on all the elements of  $S$  or  $Z$  or  $Y$  matrix. It is however possible an approximation allowing to still refer to 1-port resonator
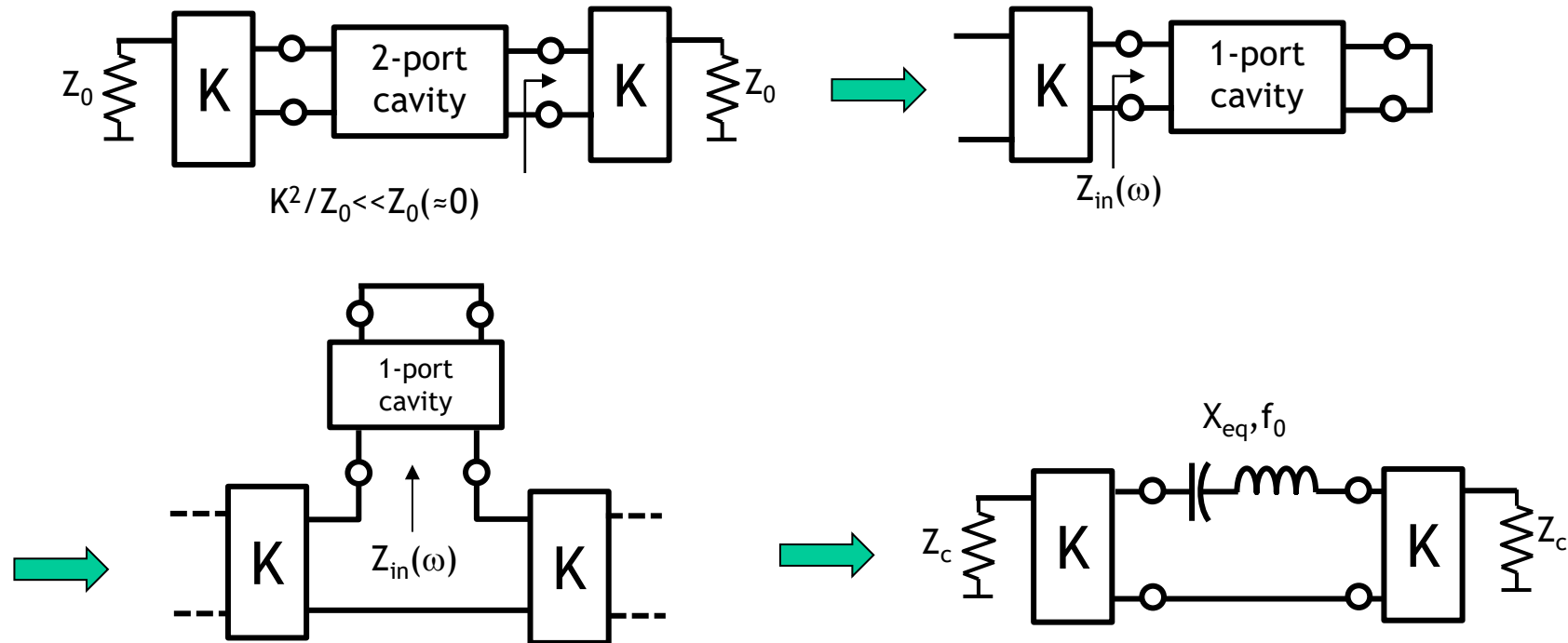
# 1-port equivalent circuit of 2-port cavities



In general, this is acceptable for narrowband filters ( $B/f_0 \ll 1$ ), but represents a further approximation that is added to the approximation of the cavity with a lumped resonator

# Example: Transmission line cavity

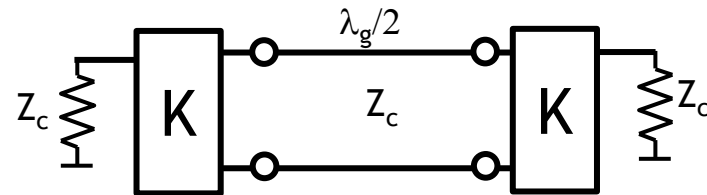

Assuming  $K^2/Z_c \ll 1$ :

