

---

# *Basics Equations for Filters Synthesis*

*Giuseppe Macchiarella*

Polytechnic of Milan, Italy

Electronic and Information Department



# Scattering parameters for lumped-elements filters

---



For linear, lumped-element networks the scattering parameters can be always represented as a polynomial ratio of the complex frequency  $p$  ( $p = \sigma + j\omega$ , with  $\omega = 2\pi f$ ):

$$S_{11} = \frac{N_{11}(p)}{D(p)}, \quad S_{21} = S_{12} = \frac{N_{12}(p)}{D(p)}, \quad S_{22} = \frac{N_{22}(p)}{D(p)}$$

- Roots of  $N_{11}$  ( $N_{22}$ ) : reflection zeros
- Roots of  $N_{21}$  : transmission zeros
- Roots of  $D$  : poles (natural frequencies)

The above polynomials are called *characteristic polynomials*

# Properties of lossless networks

---

For synthesis purposes the 2-port network representing a filter is assumed lossless (i.e. composed by lossless elements)

The scattering matrix of a lossless network is **unitary**:

$$\mathbf{S} \cdot \tilde{\mathbf{S}}^* = \mathbf{U}_2 \quad \longrightarrow \quad \begin{aligned} S_{11}(p) \cdot S_{11}(p)^* + S_{21}(p) \cdot S_{21}(p)^* &= 1 \\ S_{22}(p) \cdot S_{22}(p)^* + S_{12}(p) \cdot S_{12}(p)^* &= 1 \\ S_{11}(p) \cdot S_{21}(p)^* + S_{12}(p) \cdot S_{22}(p)^* &= 0 \end{aligned}$$

As a consequence, the following properties hold for the polynomials defining the scattering parameters ( $n$  is the filter order):

$$\begin{aligned} N_{11}(p) &= N(p), & N_{22}(p) &= (-1)^n N(p)^* \\ N(p) \cdot N(p)^* + N_{21}(p) \cdot N_{21}(p)^* &= D(p) \cdot D(p)^* \end{aligned}$$

The latter expression is known as *Feldtkeller equation*

# Properties of characteristic polynomials

---

- The \* define the paraconjugate operator:  $Q(p)^* = Q^*(-p)$ .  
The roots of  $Q(p)^*$  are given by  $-zQ^*$  (with  $zQ$  roots of  $Q$ )
- The roots of  $D(p)$  are real or complex conjugate pairs.  
The real part must be negative (strict *Hurwitz* polynomial)
- The roots of  $N(p)$  can be everywhere in the complex plane (if complex they occur as conjugate pairs). If they are on the imaginary axis  $N_{22}(p) = N(p)$
- The roots of  $N_{12}(p)$  can be on the imaginary axis (conjugate pair) or on the real axis (pairs with opposite values) or as a complex quad in the  $p$  plane
- The coefficients of all the polynomials are **real numbers**.  
Note that  $Q(p)^* = Q(-p)$  in this case.

# Steps of the synthesis process


---

- Assignment of selectivity specifications (Attenuation mask)
- Selection of a suitable *approximating function* and evaluation of its parameters in order to satisfy the specifications
- Evaluation of the characteristic polynomials from the approximating function
- Synthesis of the network from the polynomials
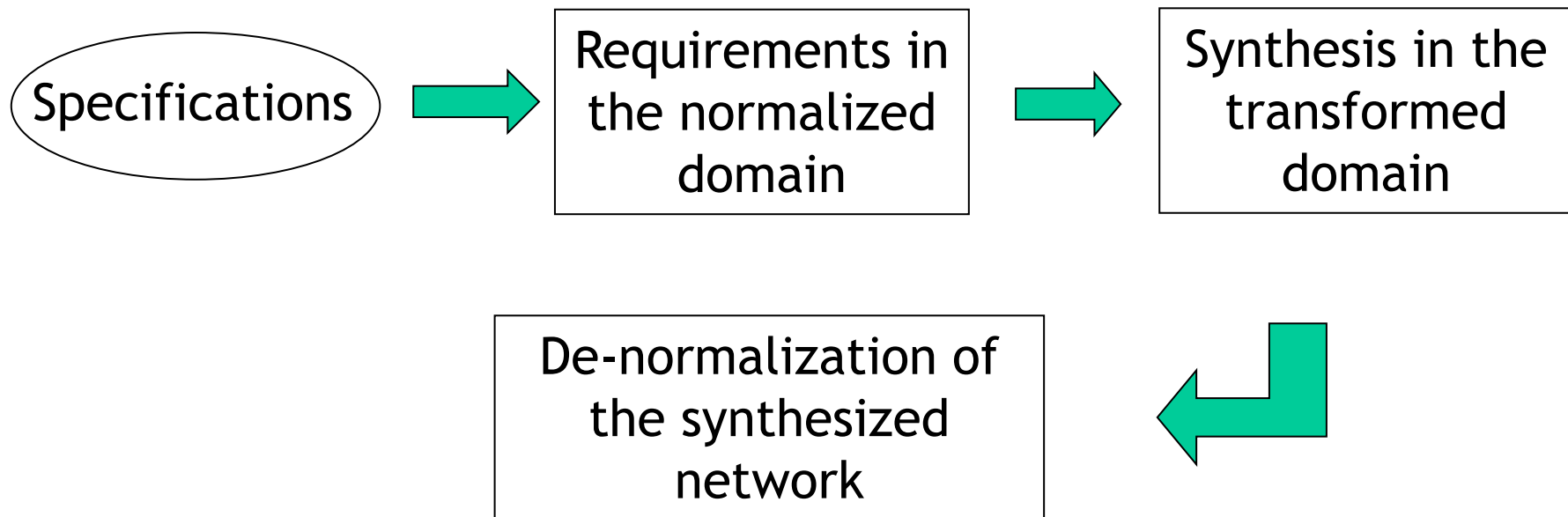
# Synthesis in a transformed frequency domain

---

In order to simplify the design process, the synthesis can be performed in a **normalized low-pass domain**, analytically defined by *frequency transformations*. The synthesized network is then *de-normalized* to the band-pass frequency domain with suitable *circuit transformation*



## Low-pass $\leftrightarrow$ Band-pass transformation

---

Let  $s = \Sigma + j\Omega$  be the normalized low-pass domain where the filter passband is defined  $\Omega_B = -1 \leftrightarrow +1$ .

The following equation relates the normalized domain with a pass-band domain suitably defined:

$$s = \frac{f_0}{B} \left( \frac{p}{f_0} + \frac{f_0}{p} \right)$$

$f_0$  and  $B$  are the frequency parameters defining the transformation:


$$f_0 = \sqrt{f_{p1} \cdot f_{p2}}, \quad B = f_{p2} - f_{p1}$$

*The order of characteristic polynomials in the normalized domain is half of the order in the bandpass domain*
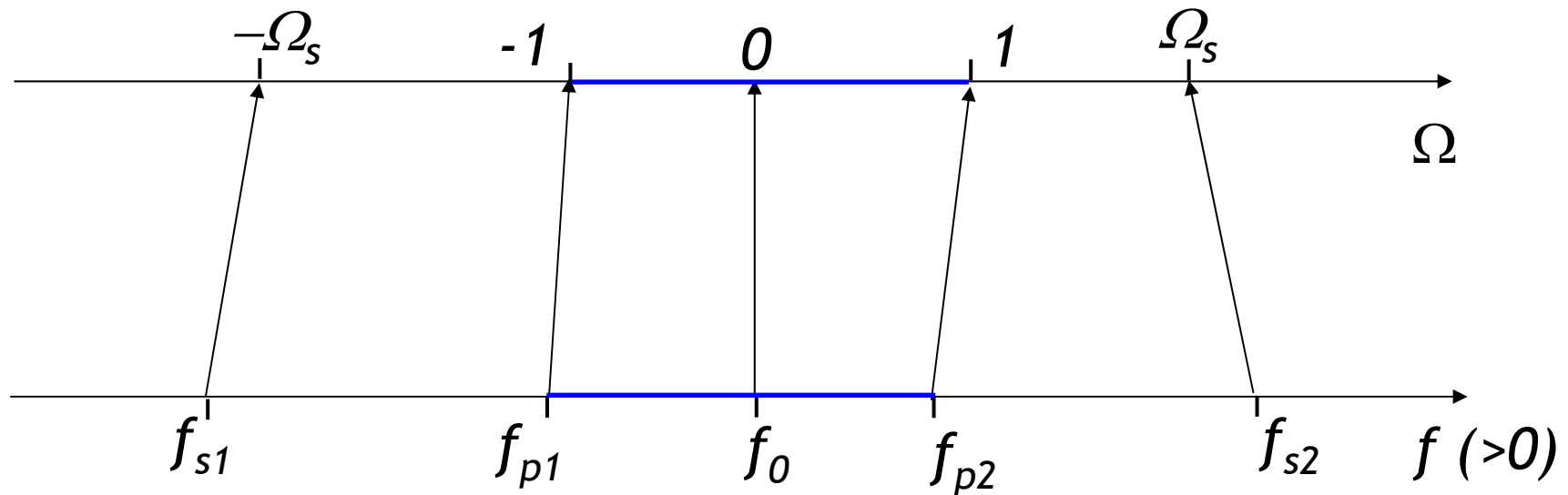
# Properties of the transformation (imaginary axis)

For  $s=j\Omega$  and  $p=j2\pi f$  it has



$$\Omega = \frac{f_0}{B} \left( \frac{f}{f_0} - \frac{f_0}{f} \right)$$



$$f_{p1} \cdot f_{p2} = f_{s1} \cdot f_{s2} = f_0^2$$



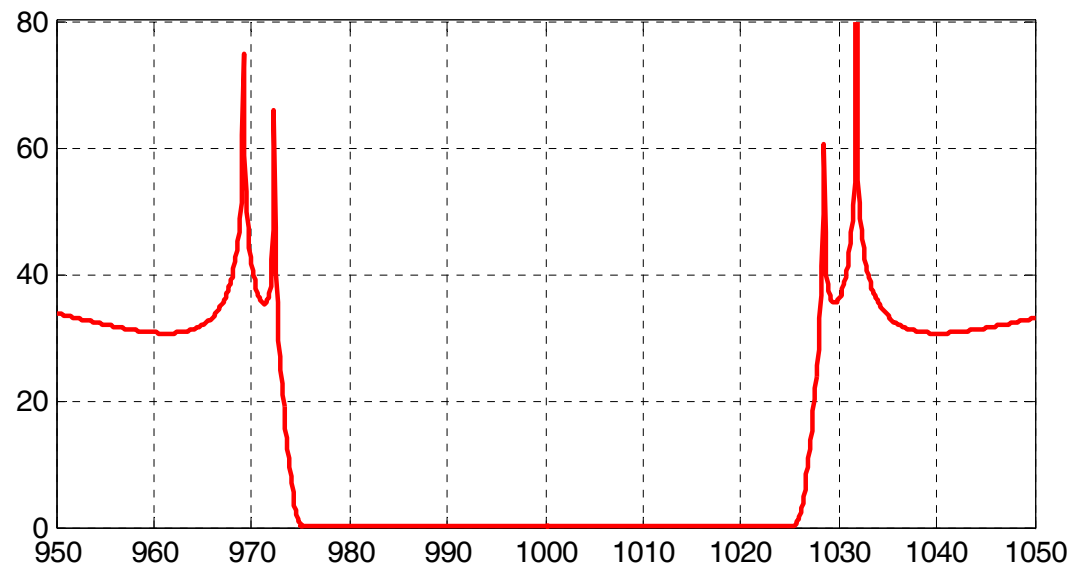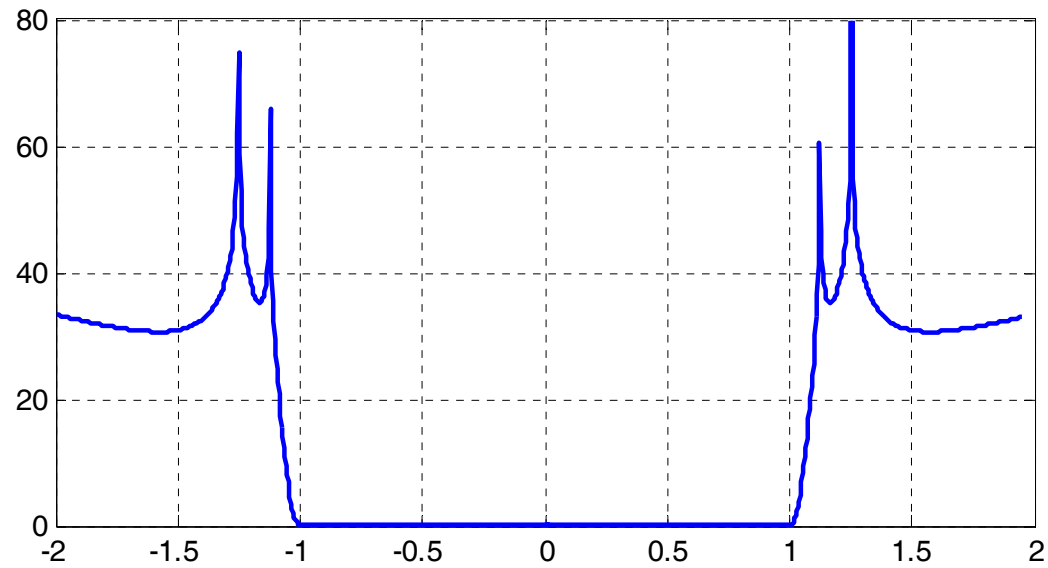
# Conservation of response: $A(j\Omega)=A(j\omega)$



$B=50$  MHz  
 $f_0=1000$  MHz

# Circuit property of the transformation: Conservation of Z and Y


Low pass

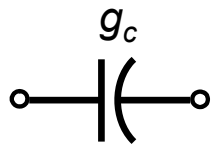

$$Y = s \cdot g_c$$


$$s = \frac{f_0}{B} \left( \frac{p}{f_0} + \frac{f_0}{p} \right)$$

➔

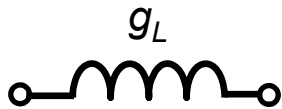


$$Z = s \cdot g_L$$

Band pass

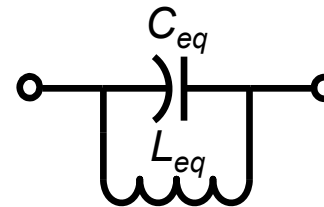

$$Y = p \cdot C_{eq} + \frac{1}{p \cdot L_{eq}} = \frac{f_0}{B} \left( \frac{p}{\omega_0} + \frac{\omega_0}{p} \right) \cdot g_c$$

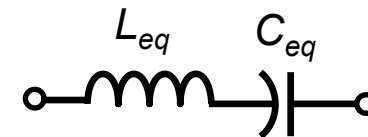
$$C_{eq} = \frac{g_c}{2\pi B}, \quad L_{eq} = \frac{1}{\omega_0^2 \cdot C_{eq}}$$





$$Z = p \cdot L_{eq} + \frac{1}{p \cdot C_{eq}} = \frac{f_0}{B} \left( \frac{p}{\omega_0} + \frac{\omega_0}{p} \right) \cdot g_L$$

$$L_{eq} = \frac{g_L}{2\pi B}, \quad C_{eq} = \frac{1}{\omega_0^2 \cdot L_{eq}}$$

# Specifications in the lowpass domain

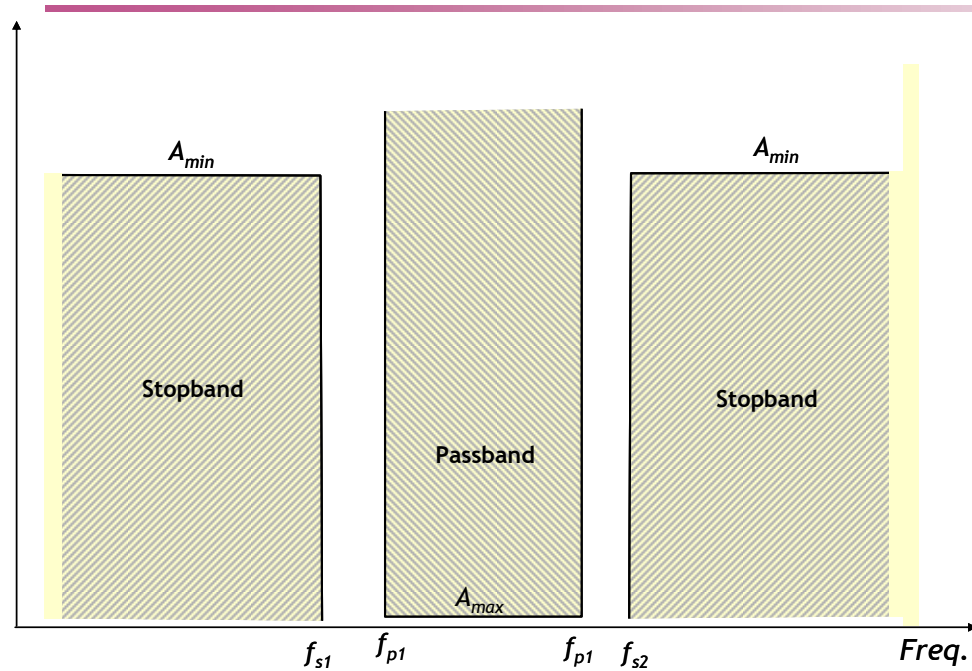

$$f_{s,1} \cdot f_{s,2} = f_0^2$$

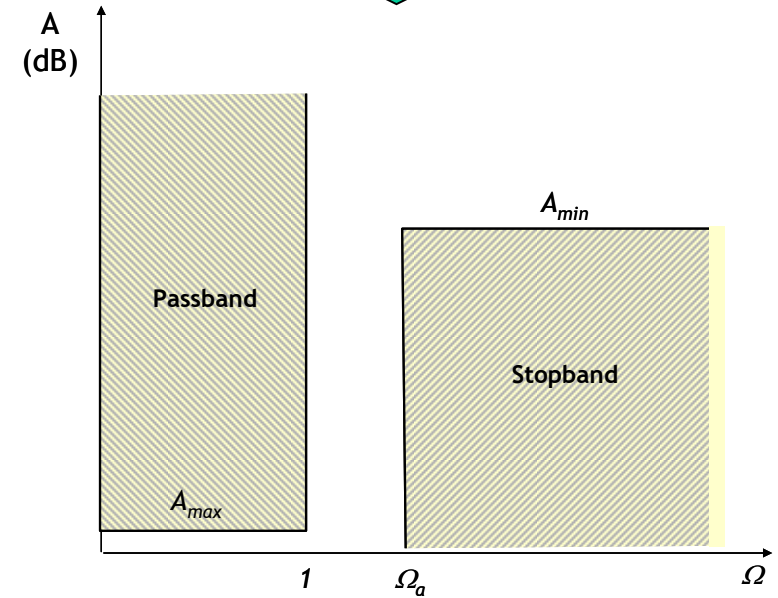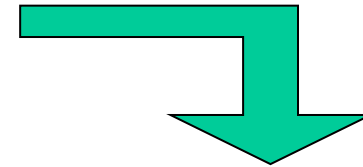

$$\Omega_a = \frac{f_0}{B} \left( \frac{f_{s,1}}{f_0} - \frac{f_0}{f_{s,1}} \right)$$

# Approximation of the ideal Lowpass response

---

General expression for attenuation in the normalized domain:

$$A(\Omega) = 1 + \varepsilon'^2 C_n^2(\Omega) = \frac{1}{|S_{21}|^2} \quad \varepsilon'^2 C_n^2(\Omega) = \frac{|S_{11}|^2}{|S_{21}|^2}$$

$C_n$  is called *Characteristic Function* and defines the approximation of ideal filter response

## Properties:

$$-1 < C_n < 1 \quad \text{for } -1 < \Omega < 1$$

$$|C_n| = 1 \quad \text{for } \Omega = \pm 1$$

$$A(\pm 1) = 1 + \varepsilon'^2$$

## Parameters $\varepsilon'$ and $n$

---

Maximum attenuation in passband:  $A_{\max} = 1 + \varepsilon'^2$

$$A = \frac{1}{|S_{21}|^2} = \frac{1}{1 - |S_{11}|^2}$$

Lossless networks:  $|S_{11}|^2 + |S_{21}|^2 = 1$   
(Unitary S matrix)

$$1 + \varepsilon'^2 = \frac{1}{1 - |S_{11}|_{\max}^2} \quad \Rightarrow \quad \varepsilon'^2 = \frac{|S_{11}|_{\max}^2}{1 - |S_{11}|_{\max}^2} = \frac{10^{-\frac{RL}{10}}}{1 - 10^{-\frac{RL}{10}}}$$

$$-20 \cdot \log\left(|S_{11}|_{\max}\right) = \text{Return Loss (RL)}$$

The parameter  $n$  represents the *order* of the characteristic function and corresponds to the number of resonators in the de-normalized network

# The characteristic function in s domain

---

Being  $s=j\Omega$ , it has:

*analytic continuation*

$$C_n^2(\Omega) = C_n(j\Omega) \cdot C_n(-j\Omega) \Rightarrow C_n^2(s) = C_n(s) \cdot C_n(-s) = C_n(s) \cdot C_n^*(s)$$

$C_n(s)$  is an *analytic function* which can be in general expressed as the ratio of two monic polynomials:

$$C_n(s) = \frac{1}{\varepsilon'} \frac{S_{11}(s)}{S_{21}(s)} = \frac{\varepsilon}{\varepsilon'} \frac{F(s)}{P(s)}$$

The roots of  $F(s)$  are the *reflection zeros* ( $A=1$ ). The roots of  $P(s)$  are the complex frequencies at which the attenuation becomes infinity (*transmission zeros*).

If  $P(s)=1$  it has an *all-pole* characteristic function (Attenuation is infinite only for  $s=\infty$ )

## Characteristic polynomials in s domain

---

From the last expression of  $C_n(s)$  the definition of the scattering parameters in s domain can be derived (all polynomials are monic):

$$S_{11}(s) = \frac{F(s)}{E(s)}, \quad S_{21} = \frac{P(s)/\varepsilon}{E(s)}$$

Note that once  $F(s)$  and  $P(s)$  are known,  $E(s)$  is obtained by applying the unitary condition of S matrix:

$$P(s) \cdot P(-s) + \varepsilon^2 [F(s) \cdot F(-s)] = E(s) \cdot E(-s)$$

$E(s)$  is found from the roots with negative real part of right-hand side (Hurwitz polynomial)

# All-pole characteristic functions (P=cost)

---

- Butterworth function:

$$C_n(\Omega) = \Omega^n$$

Main property: maximum flatness for  $\Omega=0$ , monotonic for  $|\Omega|>0$

- Chebyshev function:

$$\cos(n \cdot \cos^{-1}(\Omega)) \quad |\Omega| \leq 1$$

$$C_n(\Omega) =$$


$$\cosh(n \cdot \cosh^{-1}(\Omega)) \quad |\Omega| > 1$$

Main property: oscillates between  $\pm 1$  for  $|\Omega|<1$  ( $n$  peaks), increases monotonically for  $|\Omega|>1$



# Comparison between Butterworth and Chebicheff

---

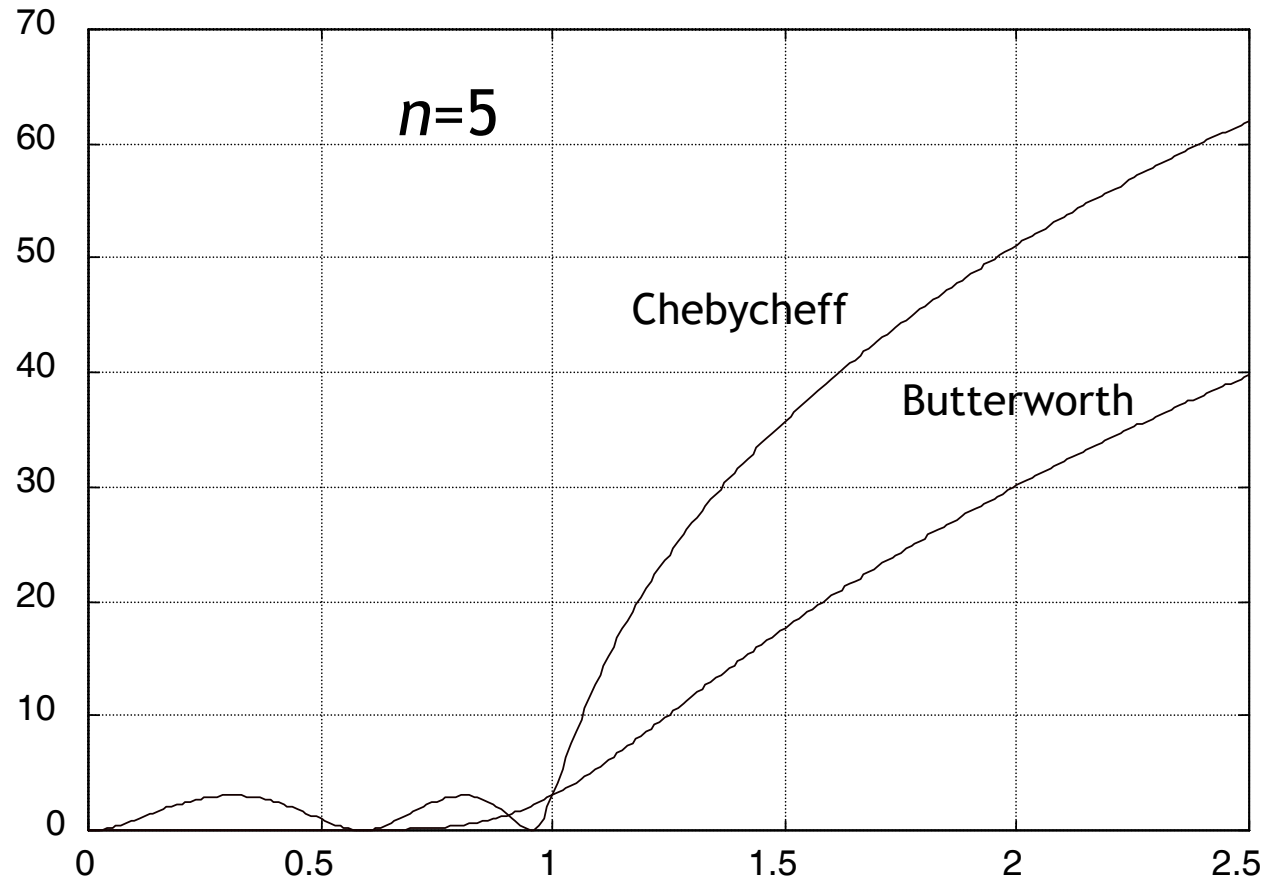

Attenuation of Chebycheff function is  $6(n-1)$  dB larger than Butterworth function for  $|\Omega| \gg 1$

# Evaluation of $\varepsilon$ and $n$

□ Assigned parameters:

- Passband Return Loss in dB (RL)
- Filter bandwidth (B) and center frequency ( $f_0$ )
- Minimum attenuation (dB) in stopband ( $A_M$ )
- Frequencies at the beginning of stopband  $f_{s1}, f_{s2}$  with  $f_{s1} \cdot f_{s2} = (f_0)^2$ .

Evaluation of  $f_{s1}$  in the lowpass domain:  $\Omega_s = \frac{f_0}{B} \left( \frac{f_{s1}}{f_0} - \frac{f_0}{f_{s1}} \right)$


Evaluation of  $\varepsilon' = \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}}$  with  $\Gamma_m = 10^{-(RL/20)}$

$$n \geq \frac{A_M + RL}{20 \log(\Omega_s)} \quad \text{Butterworth characteristic}$$

$$n \geq \frac{A_M + RL + 6}{20 \log(\Omega_s) + 6} \quad \text{Chebycheff characteristic}$$
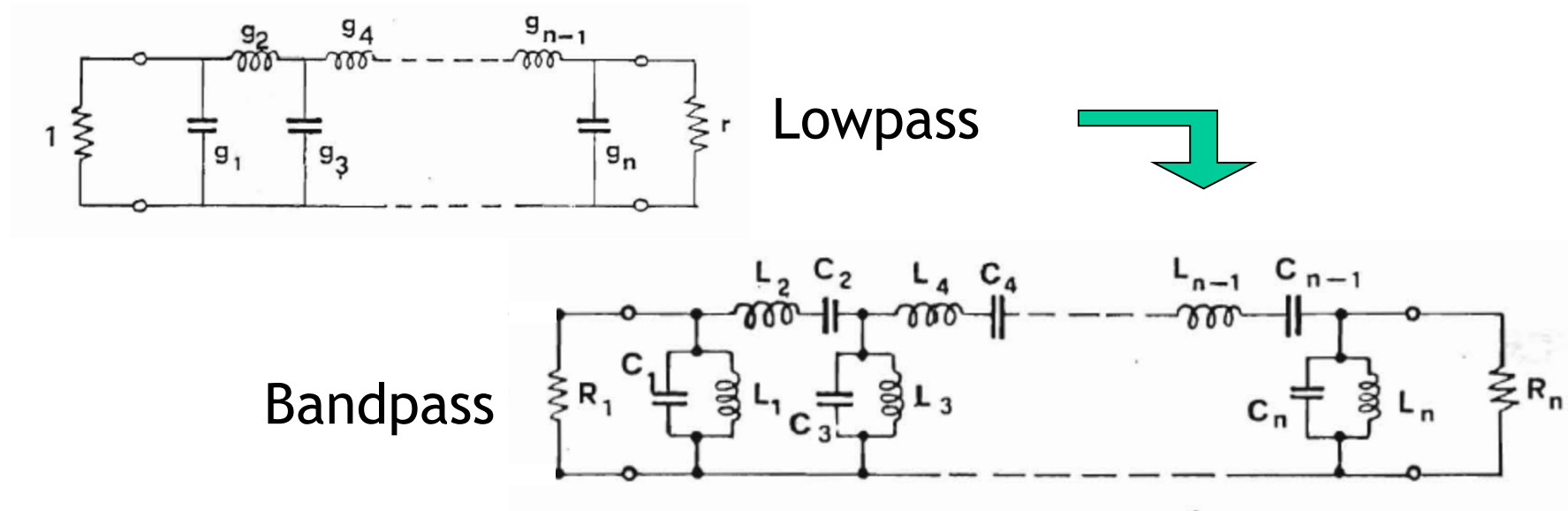
# Normalized low-pass prototype (all-pole)

- Ladder network synthesized in the normalized domain assuming unitary reference load (generator side):



Bandpass de-normalization:

$g_1, g_3, \dots \rightarrow$  shunt resonators with  $C_k = g_k / (R_1 \cdot 2\pi B)$

$g_2, g_4, \dots \rightarrow$  series resonators with  $L_k = R_1 \cdot g_k / (2\pi B)$

# Synthesis of lowpass prototype

## □ Butterworth characteristic


$$r_n = 1, \quad g_q = 2a_q \sqrt[n]{\varepsilon'}, \quad a_q = \sin\left(\frac{(2q-1)\pi}{2n}\right)$$

## □ Chebycheff characteristic

$$r_n = 1 \quad (n \text{ odd}), \quad r_n = \left[ \sqrt{1 + \varepsilon'^2} - \varepsilon' \right]^2 \quad (n \text{ even})$$


$$g_1 = \frac{2a_1}{\gamma}, \quad g_q = \frac{4a_{q-1} \cdot a_q}{b_{q-1} \cdot g_{q-1}}, \quad a_q = \sin\left(\frac{(2q-1)\pi}{2n}\right)$$
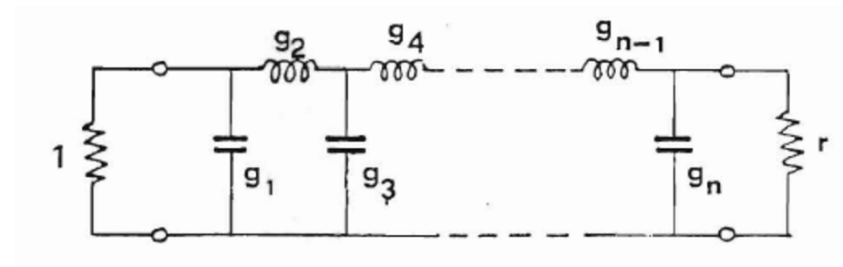
$$\gamma = \sinh\left(\frac{1}{2n} \ln\left(\frac{\sqrt{1 + \varepsilon'^2} + 1}{\sqrt{1 + \varepsilon'^2} - 1}\right)\right), \quad b_q = \gamma^2 + \sin^2\left(\frac{q\pi}{n}\right)$$


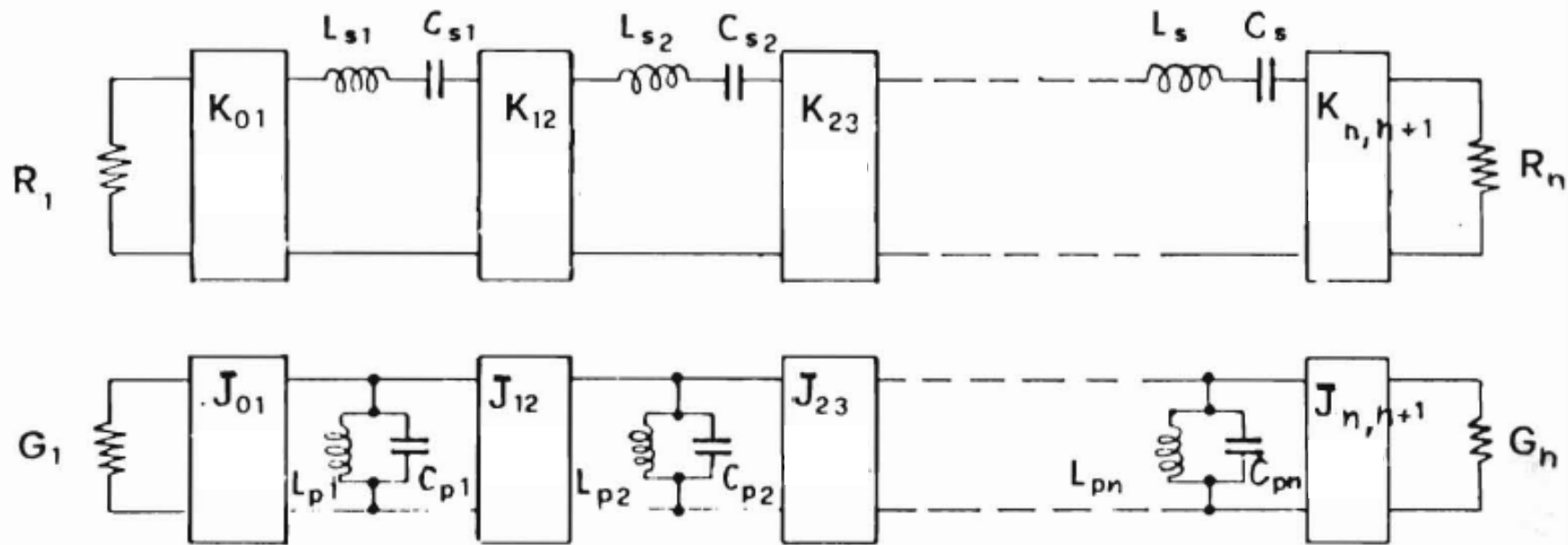
# De-normalized (bandpass) network with only series or shunt resonators

For microwave frequencies implementation is requested to have only one type of resonator (series or shunt). This is obtained with the introduction of impedance (admittance) inverters



# General design equation

---

Introduction of inverter determines additional degrees of freedom which allows the arbitrary assignments of some parameters (inverters or resonators parameter).

The condition to be satisfied are expressed by the following equations:

Series Network

$$K_{01} = \sqrt{\frac{B}{f_0} \frac{\omega_0 L_{s,1}}{g_1} R_1}$$

$$K_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{\omega_0 L_{s,q} \cdot \omega_0 L_{s,q+1}}{g_q \cdot g_{q+1}}}$$

Shunt Network

$$J_{01} = \sqrt{\frac{B}{f_0} \frac{\omega_0 C_{s,1}}{g_1} G_1}$$

$$J_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{\omega_0 C_{s,q} \cdot \omega_0 C_{s,q+1}}{g_q \cdot g_{q+1}}}$$

The bandpass network is assumed symmetric respect the central inverter ( $n$  even) or resonator ( $n$  odd)

# Universal coupling parameters

---

Coupling coefficient:

$$k_{q,q+1} = \frac{K_{q,q+1}}{\sqrt{\omega_0 L_{s,q} \cdot \omega_0 L_{s,q+1}}} = \frac{J_{q,q+1}}{\sqrt{\omega_0 C_{s,q} \cdot \omega_0 C_{s,q+1}}} = \frac{B}{f_0} \sqrt{\frac{1}{g_q \cdot g_{q+1}}}$$


External Q:

$$Q_E = \frac{\omega_0 L_{s,1}}{K_{01}^2 / R_1} = \frac{\omega_0 C_{s,1}}{J_{01}^2 / G_1} = \frac{g_1}{B / f_0}$$

$\omega_0 L_{s,1}$  = Equivalent reactance of series resonators

$\omega_0 C_{s,1}$  = Equivalent susceptance of shunt resonators
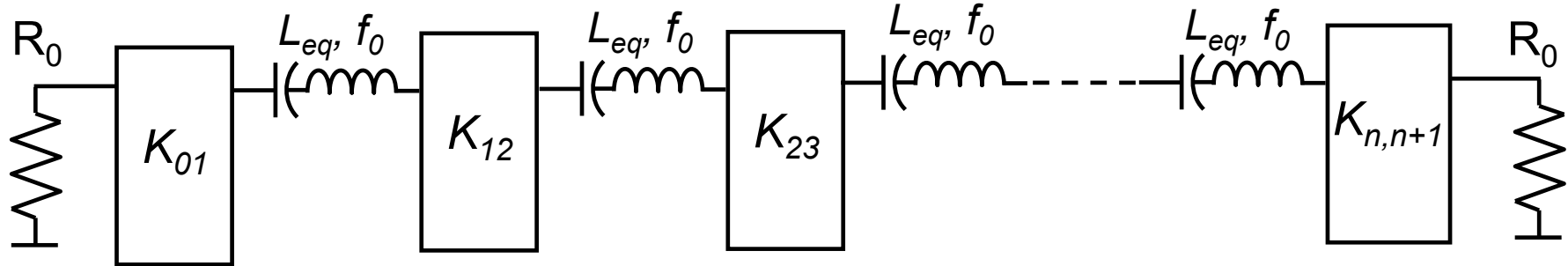
# In-line filters with all-equal resonators



From the general design equations:



$$K_{q,q+1} = k_{q,q+1} \cdot (\omega_0 L_{eq}) \quad K_{01} = K_{n,n+1} = \sqrt{\frac{\omega_0 L_{eq}}{Q_E} R_1}$$

with:

$$k_{q,q+1} = \frac{B}{f_0} \sqrt{\frac{1}{g_q \cdot g_{q+1}}} \quad Q_E = \frac{g_1}{B/f_0}$$



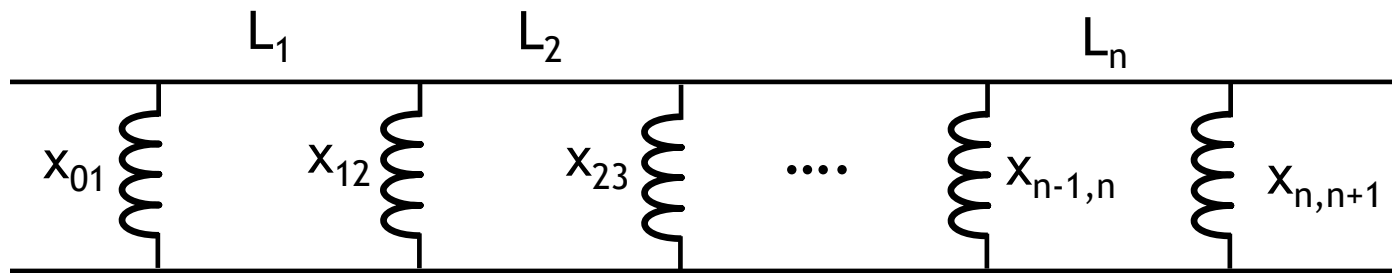
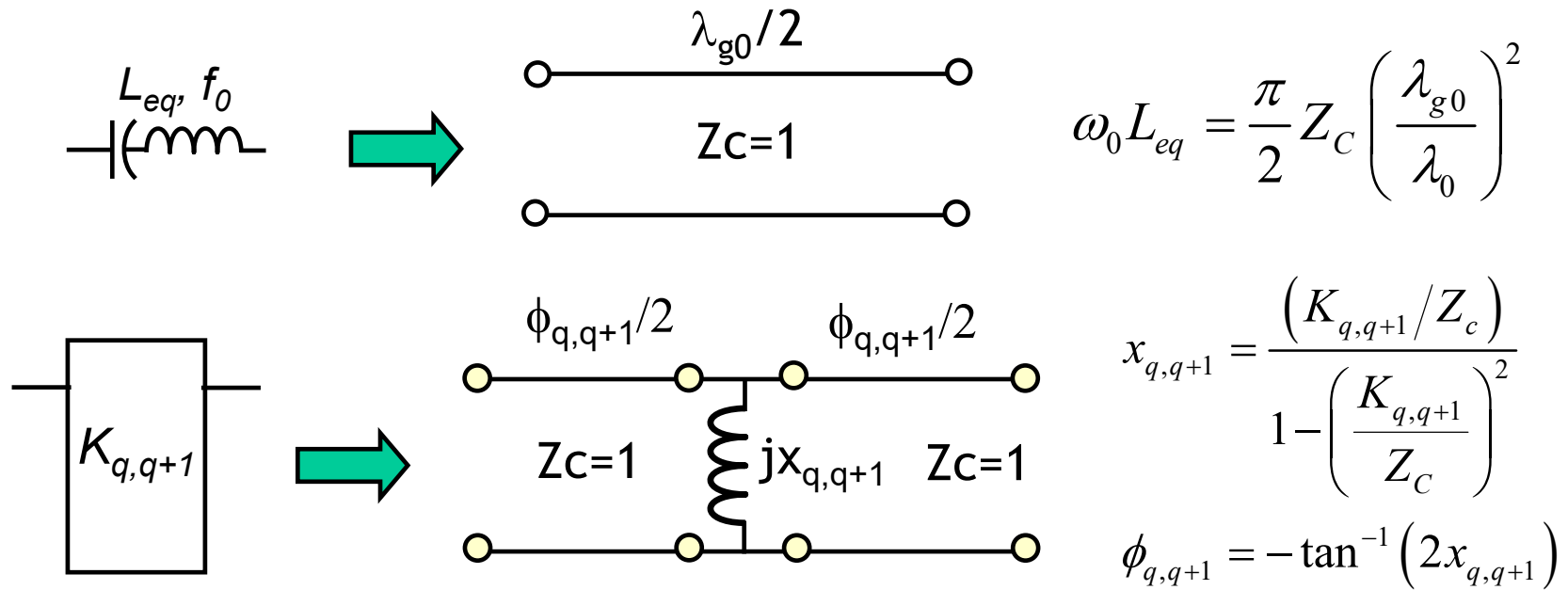
# $\lambda_{g0}/2$ waveguide resonators coupled with inductive reactances



$$L_q = \frac{1}{\beta_{g0}} \left[ \pi + \frac{\phi_{q-1,q} + \phi_{q,q+1}}{2} \right]$$

# Inductive reactances in rectangular waveguide

## □ Iris with finite thickness

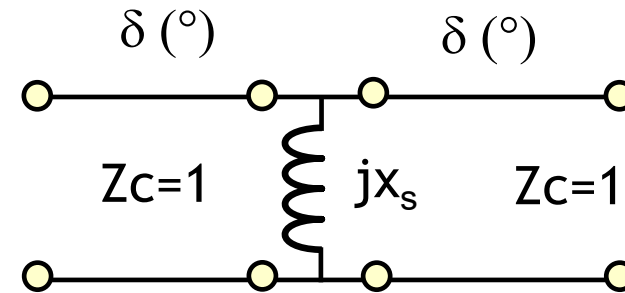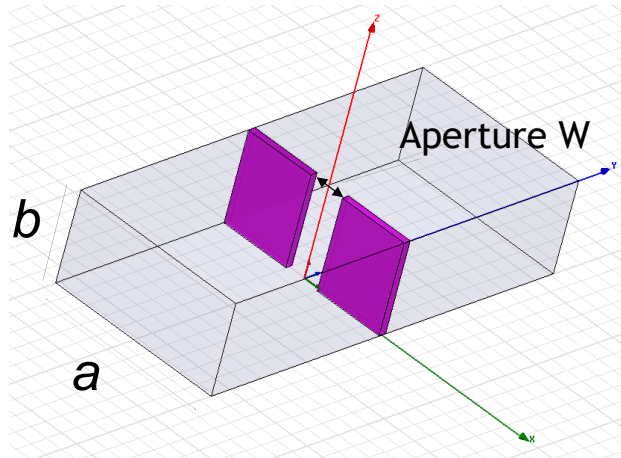


Equivalent circuit (reference sections: symmetry axis)

$$j \frac{X}{Y_c} = -\frac{1}{2} \frac{S_{12}}{S_{11}}, \quad \exp(-j2\delta) = (S_{12} - S_{11})$$


$S_{11}$ ,  $S_{12}$ : scattering parameters (computed numerically with EM simulators)
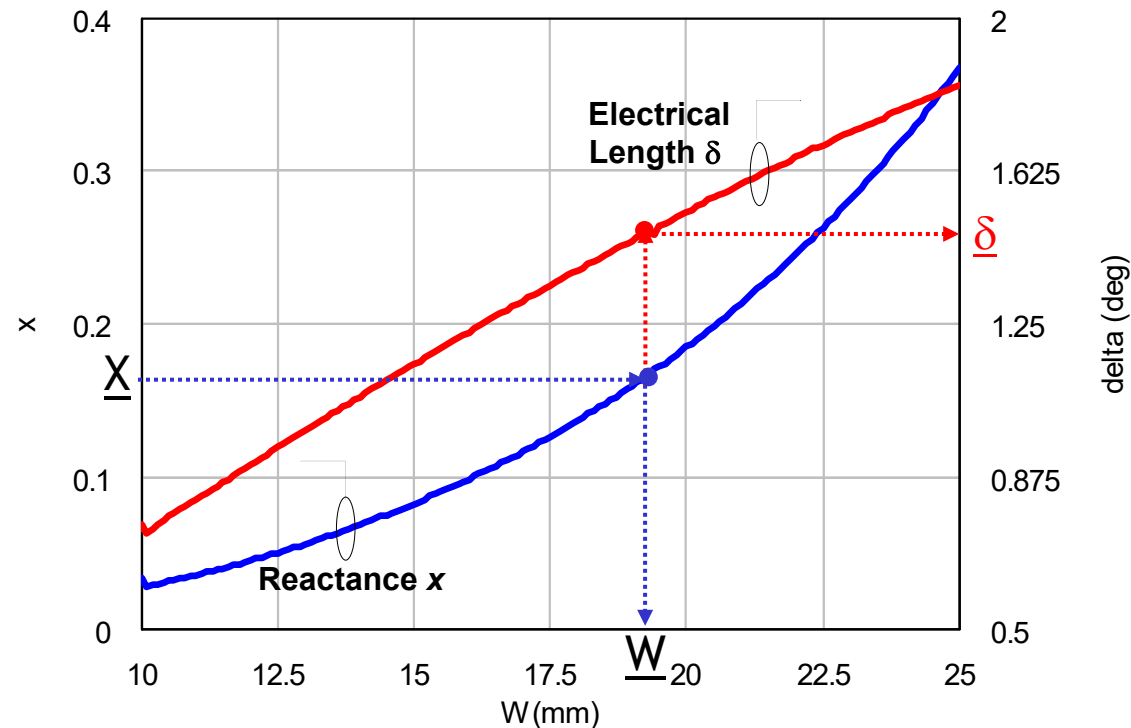
# Evaluation of iris equivalent parameters



- With the previous formulas, the curves of  $x$  and  $\delta$  vs.  $W$  are drawn (see the graph above).
- For the required value  $\underline{X}$  the aperture  $\underline{W}$  is first obtained through the blue curve. The corresponding electrical length  $\underline{\delta}$  is derived from the red curve

# Filter dimensioning

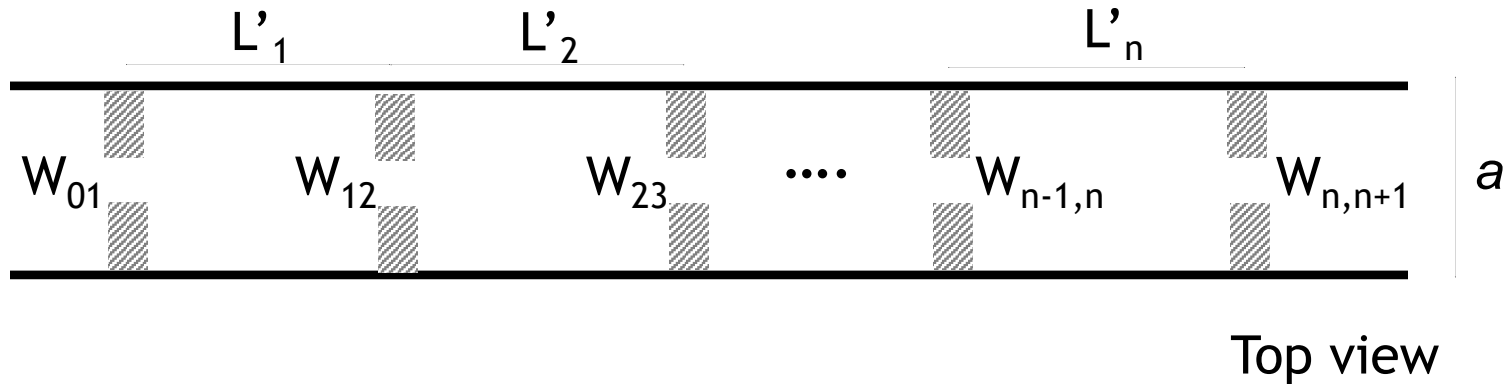

The apertures  $W_{i,i+1}$  are evaluated as explained in the previous slide from the  $K_{i,i+1}$ .

The separation of the iris are obtained from the lengths  $L_q$  corrected with the irises parameters  $\delta_{q,q+1}$ :

$$L'_q = L_q - \frac{1}{\beta_{g0}} (\delta_{q-1,q} + \delta_{q,q+1})$$

## Example of design

### Specifications:

$f_0=4$  GHz,  $B=40$  MHz

Return Loss in passband  $\geq 26$  dB

$A_{s1} \geq 45$  dB for  $f > 4.05$  GHz

$A_{s2} \geq 60$  dB for  $f > 3.9$  GHz

Chebyshev characteristic

*Being  $f_{s1}$  and  $f_{s2}$  not geometrically symmetric, the requested order  $n$  of the filter is obtained by selecting the larger between the following ones:*

$$n_1 \geq \frac{A_{s1} + RL + 6}{20 \log(\Omega_{s1}) + 6} = 5.54$$

$$n_2 \geq \frac{A_{s2} + RL + 6}{20 \log(\Omega_{s2}) + 6} = 4.58$$

$$n=6$$

## Step 1: Evaluation of equivalent circuit param.

---

Selected waveguide:  $a=50\text{mm}$ ,  $b=25\text{mm}$

Waveguide parameters:

Cutoff frequency:  $f_c=v/2a=3\text{ GHz}$

$$\lambda_{g_0} = \frac{\lambda_0}{\sqrt{1-(f_c/f_0)^2}} = 113.3\text{mm}, \quad \left(\frac{\lambda_{g_0}}{\lambda_0}\right)^2 = 2.286$$


Prototype normalized coefficients:

$$g_q = \{0.7919, 1.3649, 1.7002, 1.5379, 1.5089, 0.7163\}$$

Coupling reactances and resonator lengths:

$$X_{q,q+1} = \{0.223, 0.0345, 0.0235, 0.022, 0.0235, 0.0345, 0.223\}$$
$$L_q = \{52.21, 55.56, 55.78, 55.78, 55.56, 52.21\}$$
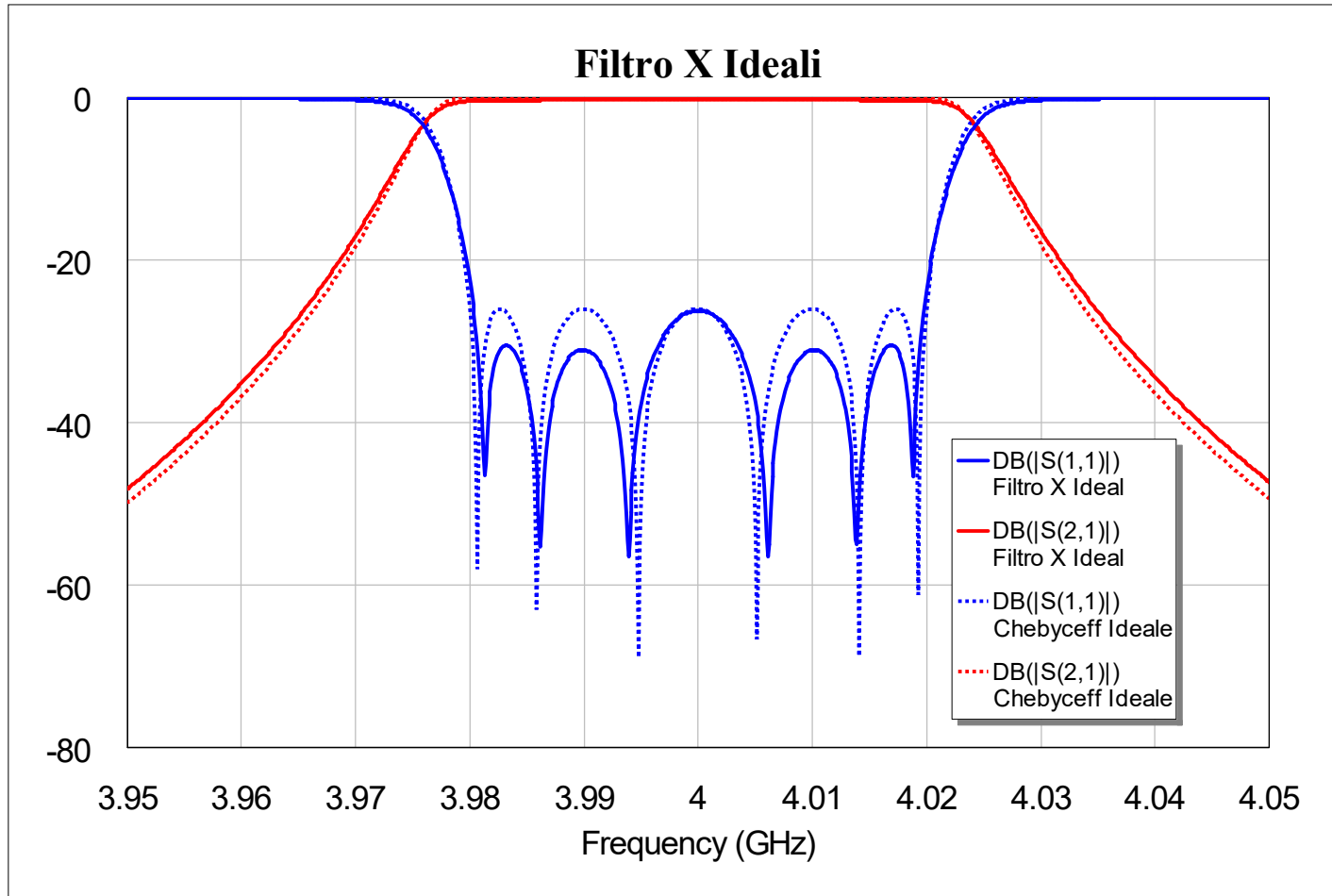
# Filter response (ideal inductive reactance)



The reactances are assumed constant with  $f$


## Step 2: Irises dimensioning

---

$$W_{q,q+1} = \{21.31, 10.85, 9.419, 9.213, 9.419, 10.85, 21.31\} \text{ mm}$$
$$\delta_{q,q+1} = \{0.507, 0.2536, 0.2145, 0.209, 0.2145, 0.2536, 0.507\} \text{ mm}$$

Corrected lengths of resonators:

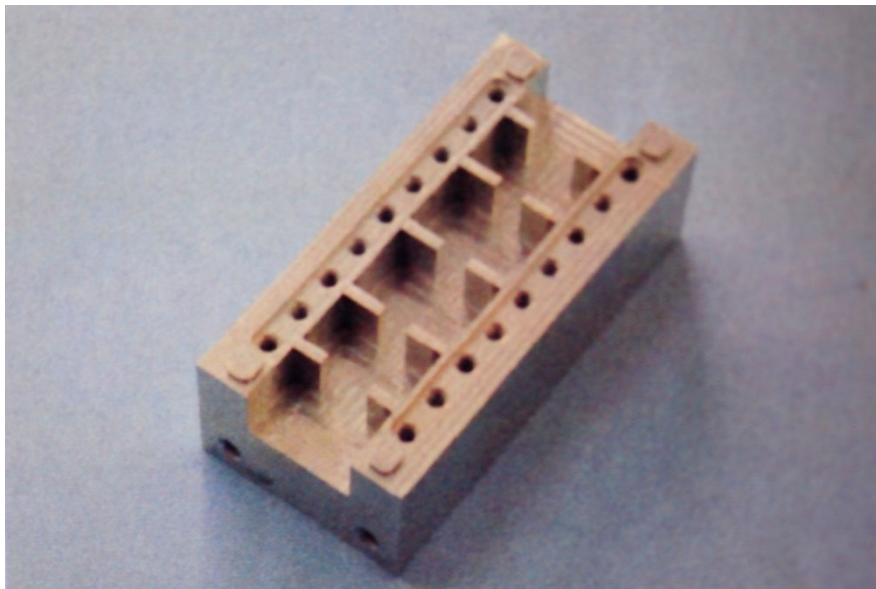
$$L'_q = \{51.45, 55.09, 55.36, 55.36, 55.09, 51.45\} \text{ mm}$$




Example of  
fabricated device (4  
resonators sample)






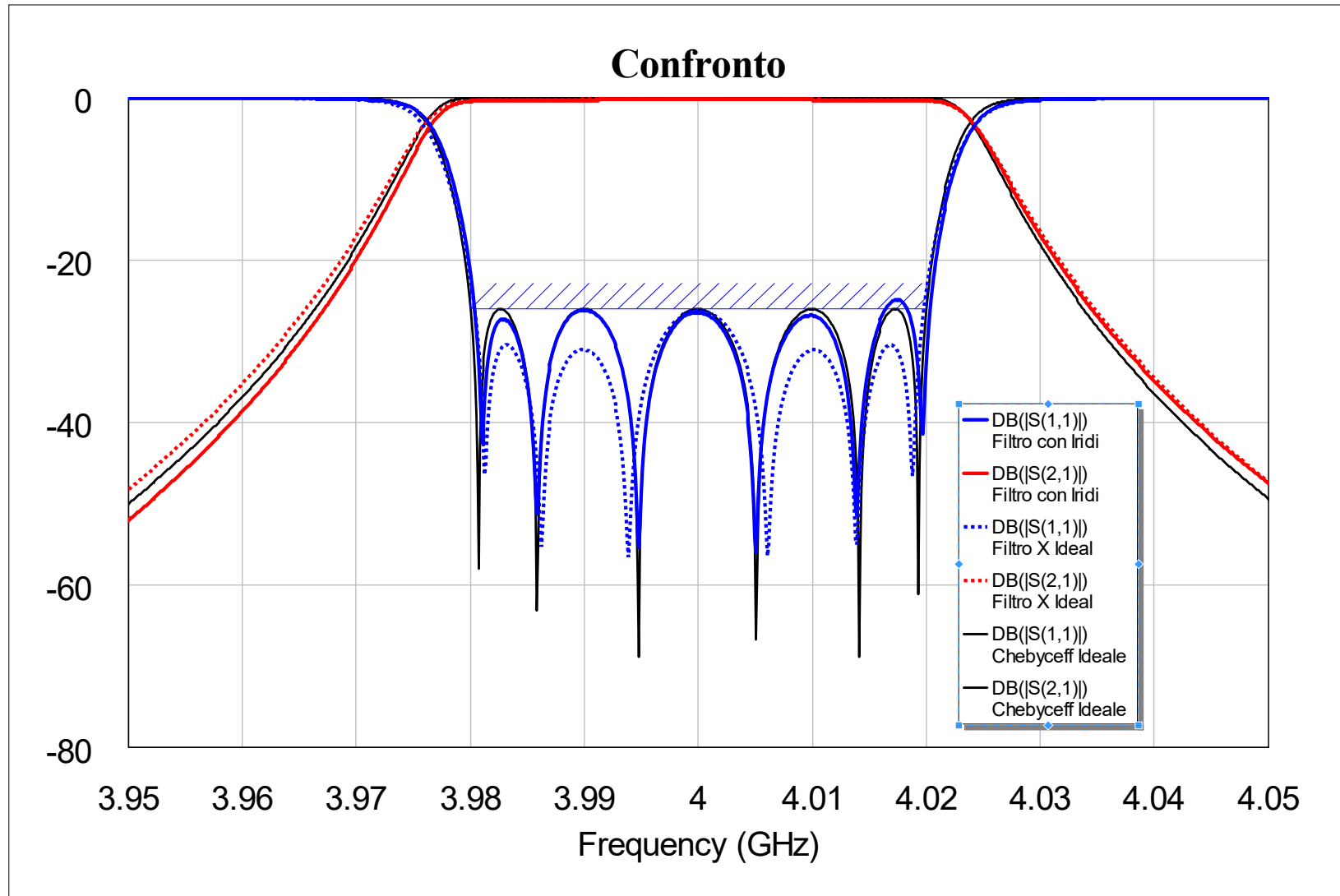
# Computed filter response (Mode Matching)




# Broad frequency range response

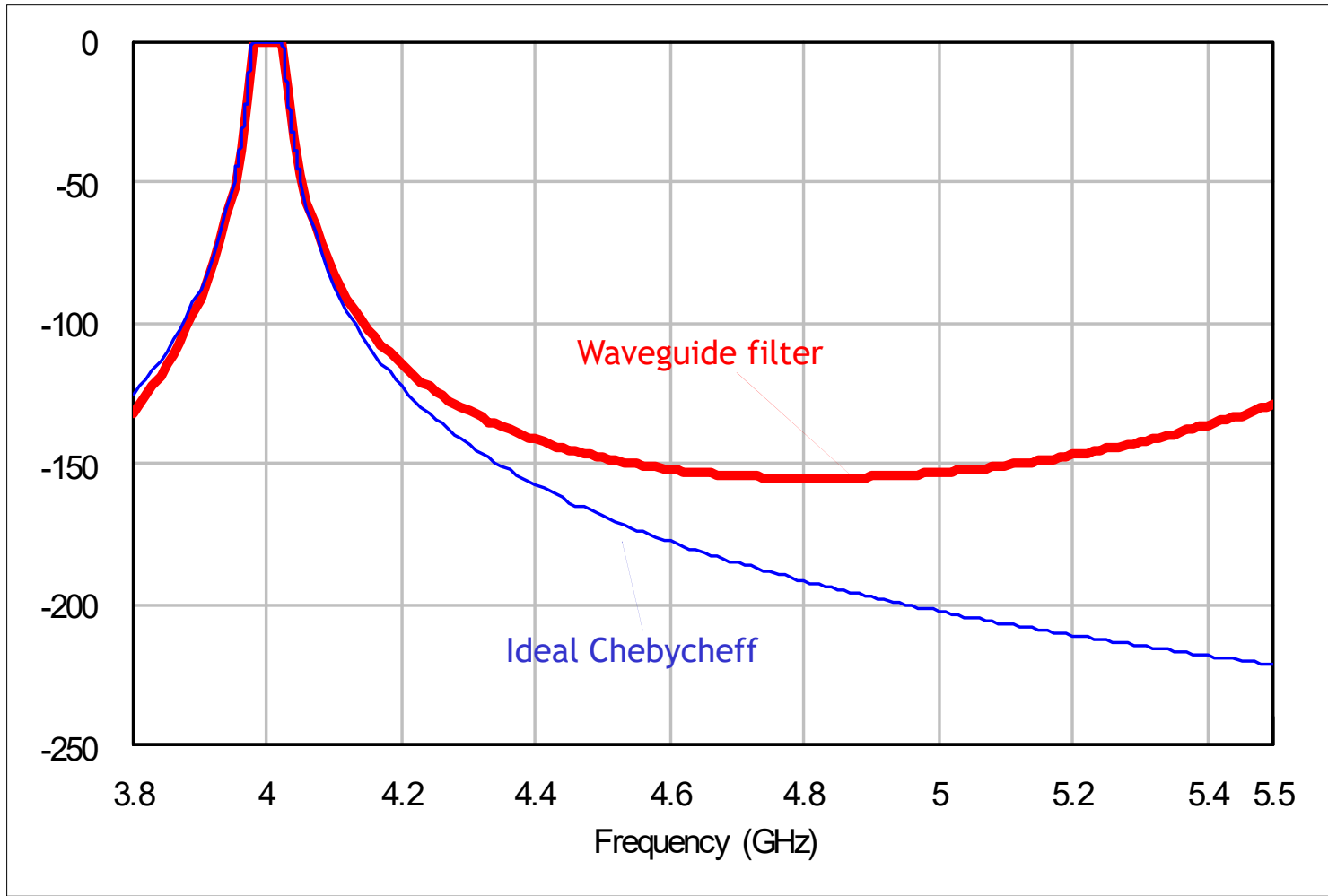

# Effect of filter bandwidth on accuracy

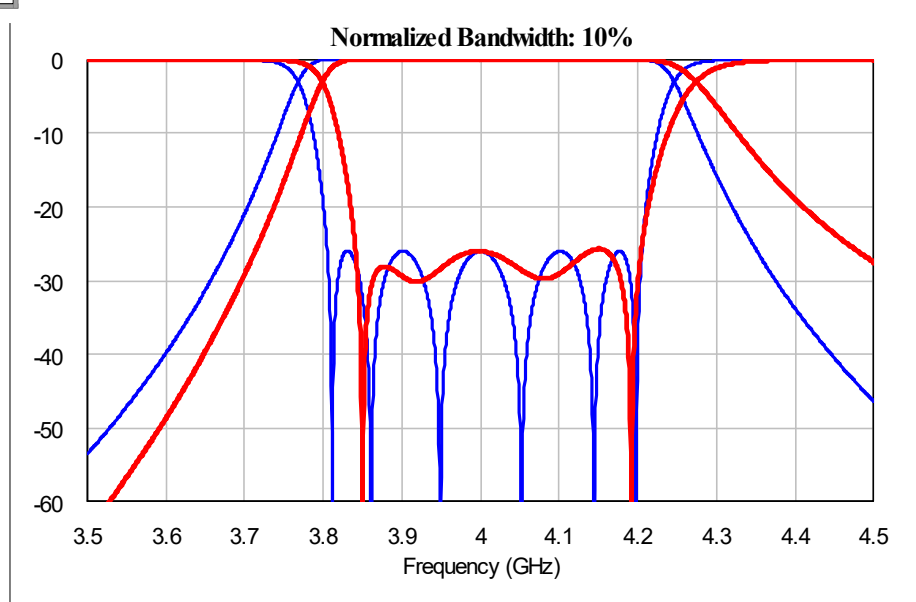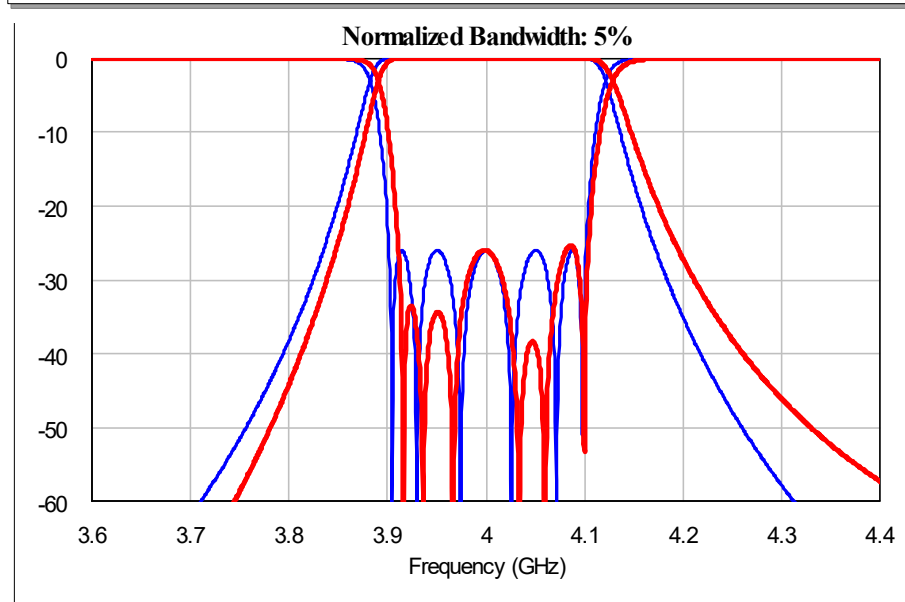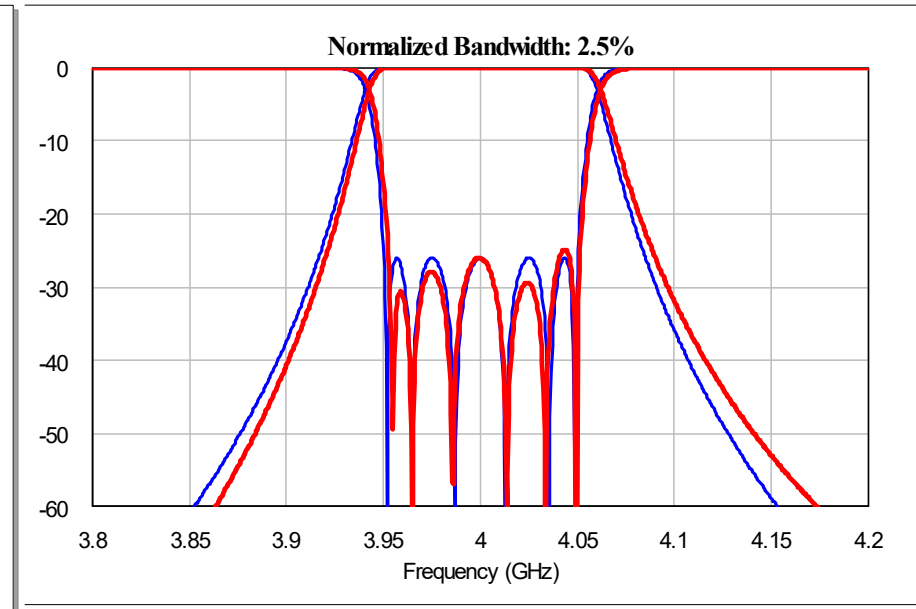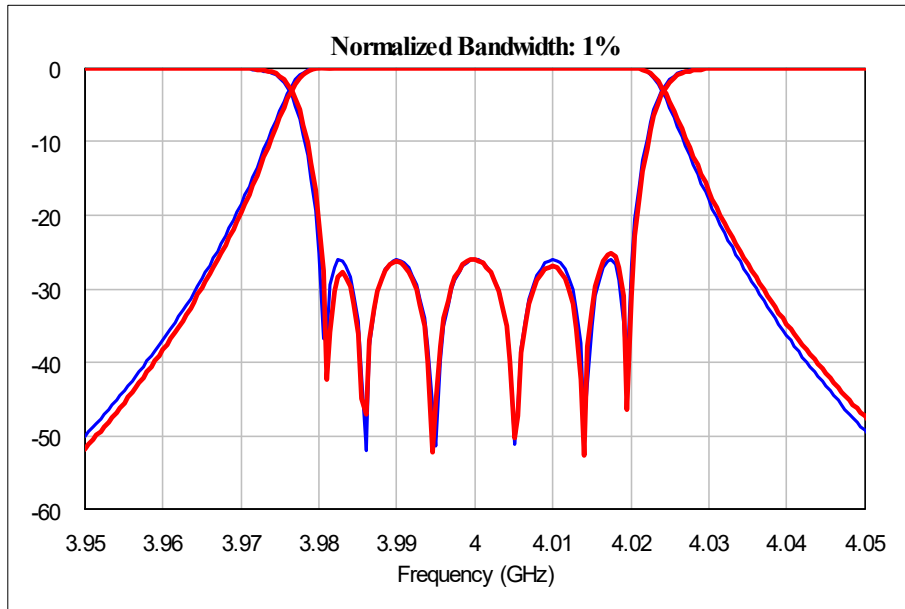

## Multi-port simulation of the filter

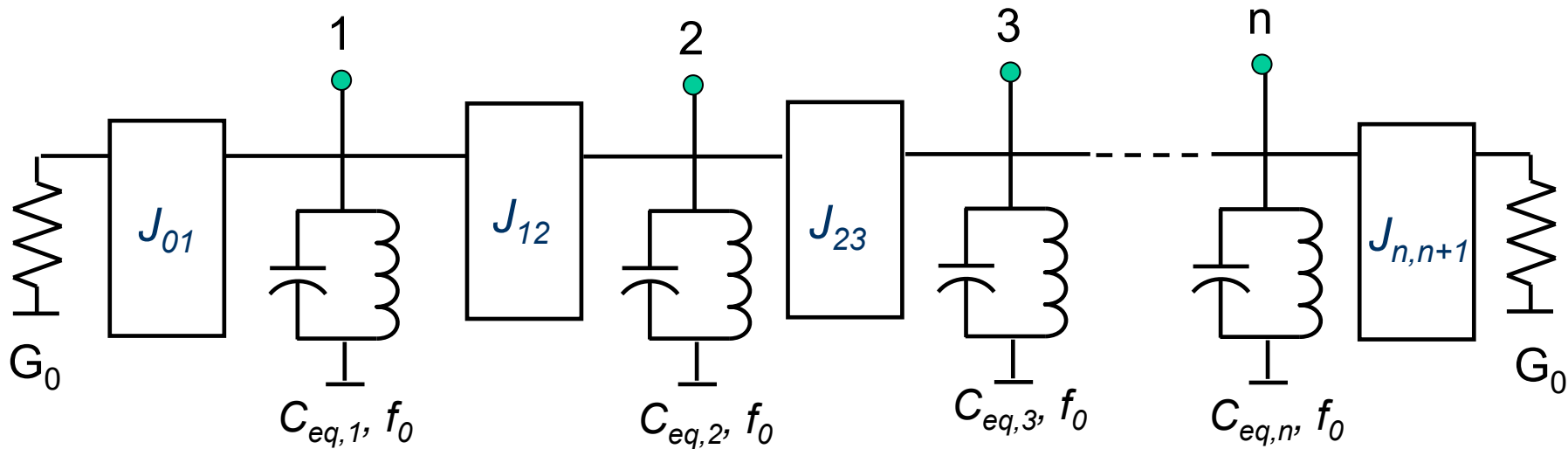

Extraction of matrix Y (EM simulation):

$$y_{i,i} = jB_{ris,i}, \quad y_{i,i+1} = jJ_{i,i+1}$$

$$B_{ris,i}(\omega) = \omega_0 C_{eq,i} \left( \frac{f}{f_0} - \frac{f_0}{f} \right) \Rightarrow \omega_0 C_{eq,i} = B_{eq,i} = \frac{1}{2} \omega_0 \left. \frac{\partial \text{Im}(y_{i,i}(\omega))}{\partial \omega} \right|_{\omega=\omega_0}$$

$$J_{i,i+1} = \text{Im}(y_{i,i+1}(\omega_0))$$

# Extraction of Universal Parameters Y matrix

---

$f_{0,i}$  is the frequency where  $B_{i,i}=0$


$$Q_{ext,1} = \frac{B_{eq,1}}{J_{01}^2} G_0 = \frac{\left[ \frac{1}{2} \omega_0 \frac{\partial \text{Im}(y_{11}(\omega))}{\partial \omega} \Big|_{\omega=\omega_0} \right]}{\text{Re}[y_{11}(\omega_0)]},$$

$$k_{i,i+1} = \frac{J_{i,i+1}}{\sqrt{B_{eq,i} \cdot B_{eq,j}}} = \frac{\text{Im}(y_{i,i+1}(\omega_0))}{\frac{1}{2} \omega_0 \sqrt{\frac{\partial \text{Im}(y_{i,i}(\omega_0))}{\partial \omega} \frac{\partial \text{Im}(y_{j,j}(\omega_0))}{\partial \omega}}}$$


# Example: waveguide filter seen before
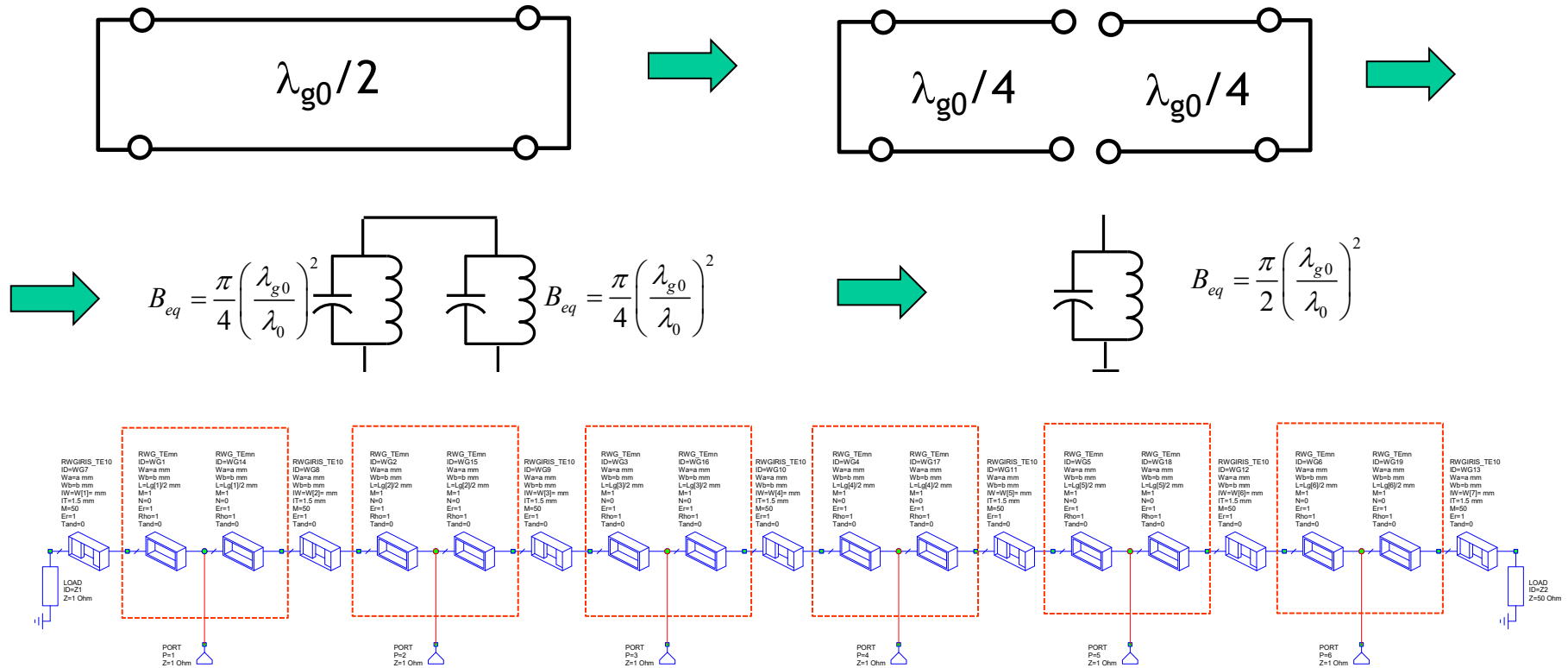
## Note


A short-circuited waveguide resonator of length  $\lambda_{g0}/2$  observed at the center shows a shunt resonance:



# Extracted $B_{i,i}$

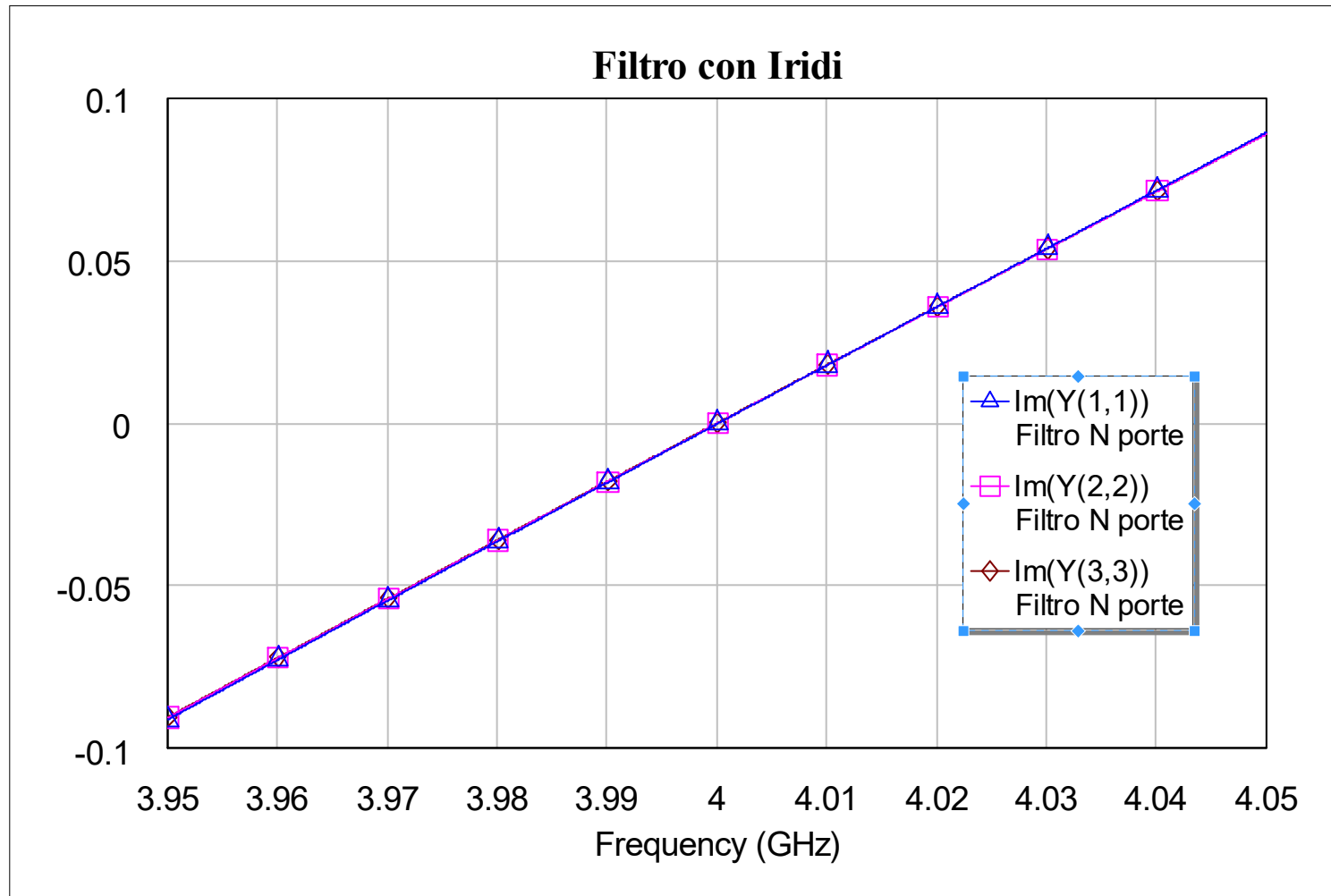

# Extracted $J_{i,i+1}$

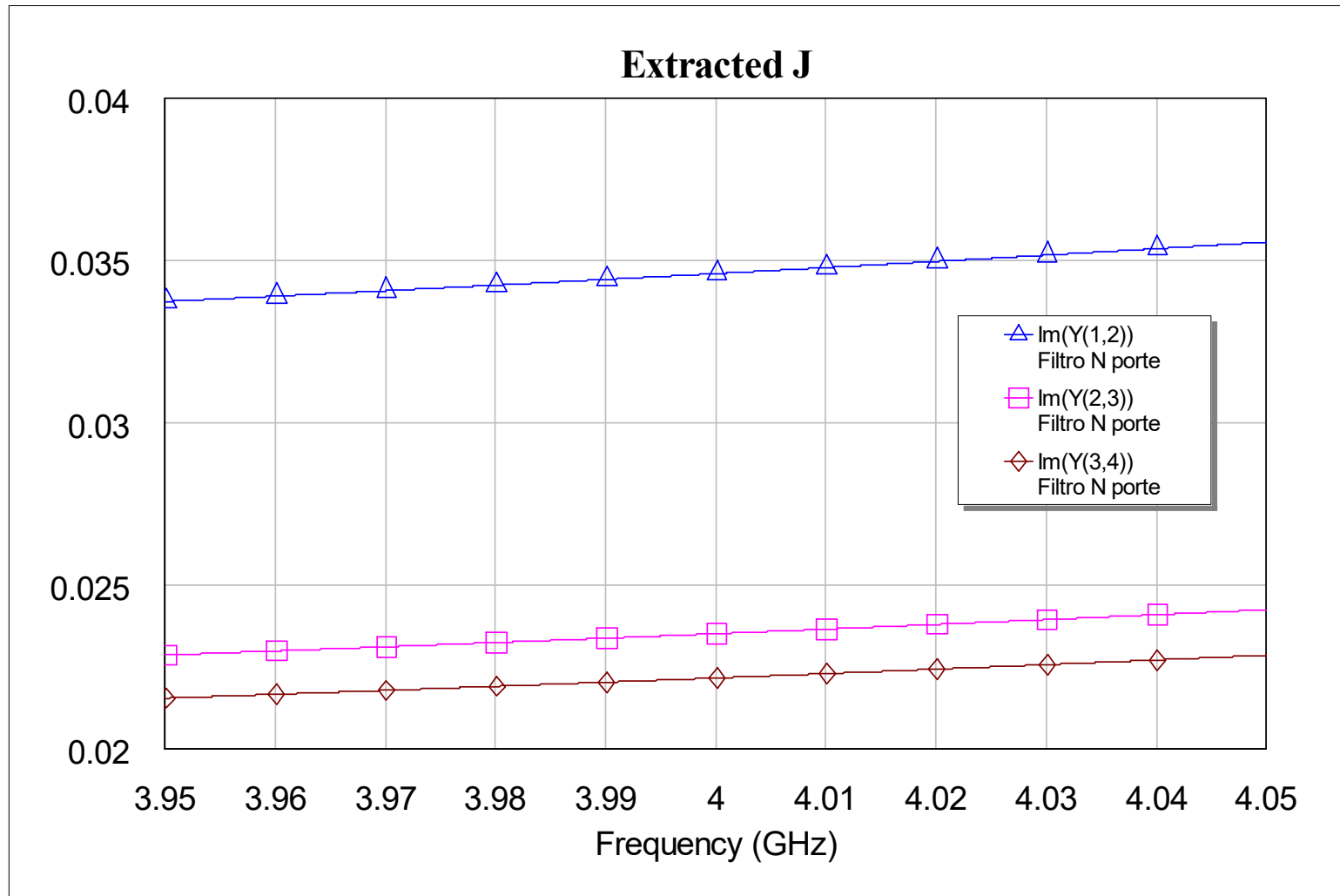



# Computed Universal Parameters

Y11 = Filtro N porte:Y(1,1)  
 Y22 = Filtro N porte:Y(2,2)  
 Y33 = Filtro N porte:Y(3,3)  
 Y12 = Filtro N porte:Y(1,2)  
 Y23 = Filtro N porte:Y(2,3)  
 Y34 = Filtro N porte:Y(3,4)

F= \_FREQ\*1e-6

B11=imag(Y11)  
 B22=imag(Y22)  
 B33=imag(Y33)

J12=imag(Y12)  
 J23=imag(Y23)  
 J34=imag(Y34)

I1=find\_index(B11,0)  
 I2=find\_index(B22,0)  
 I3=find\_index(B33,0)

F[I1]: 4000  
 F[I2]: 4000  
 F[I3]: 4000

I0=find\_index(F,4000)

Beq1=0.5\*der(B11,F)  
 Beq1=Beq1[I1]\*F[I1]

Beq1: 3.611

Beq2=0.5\*der(B22,F)  
 Beq2=Beq2[I2]\*F[I2]

Beq2: 3.59

Beq3=0.5\*der(B33,F)  
 Beq3=Beq3[I3]\*F[I3]

Beq3: 3.588

Qext=Beq1/real(Y11[I1])

1/Qext: 0.01271

Synthesized:

k01= 0.01263

k12=J12[I0]/sqrt(Beq1\*Beq2)

k12: 0.00961

k12=0.0096189

k23=J23[I0]/sqrt(Beq3\*Beq2)

k23: 0.006554

k23=0.0065646

k34=J34[I0]/sqrt(Beq3\*Beq3)

k34: 0.006176

k34=0.0061843