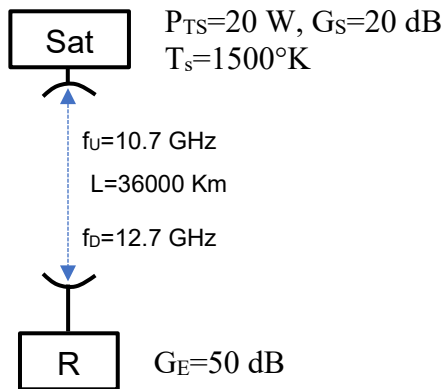


RF SYSTEMS
9 July 2019

Surname & Name
Identification Number
Signature


Exercise 1 (11)

Consider the bi-directional satellite link in the figure (f_U : Earth-to-Satellite, f_D : Satellite-to-Earth). The satellite parameters are given (Transmitter power P_T , Antenna Gain G_S , Equivalent Noise Temperature of the receiving system T_s). The Earth station has only the antenna gain G_E assigned. The required data rate R must be 100 Mb/sec with $E_b/N_0=15$ dB and $B=36$ MHz for both up and down link.



- 1) Evaluate the SNR that must be guaranteed by the receivers of satellite and Earth Station
- 2) Compute the required transmitted power from the earth station
- 3) Compute the required Equivalent Noise Temperature of the earth receiver

Exercise 2 (11)

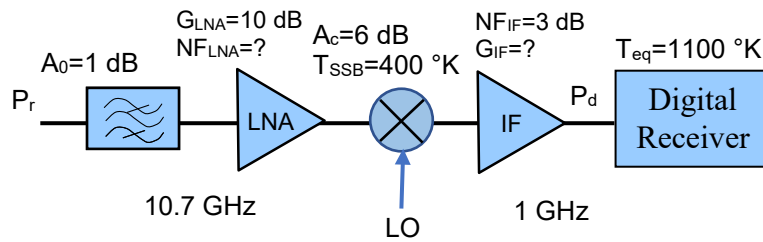


The scheme in the figure represents the receiver on board of the satellite (previous exercise). The digital receiver guarantees $E_b/N_0 = 15$ dB with the input power $P_d \geq -60$ dBm.

- 1) Evaluate the gain of the IF amplifier in order to satisfy the constraint on P_d
- 2) Evaluate the two possible frequencies of the local oscillator. For each LO frequency specify the corresponding image frequency.
- 3) Draw the equivalent noise temperature scheme of the receiver (including the contribution from the antenna $T_a = 300$ °K)
- 4) Write the expression of the noise temperature at the receiver input (T_S)
- 5) Compute the Noise figure NF_{LNA} of the low noise amplifier in order T_S is equal to the value specified in the previous exercise (1500 °K)
- 6) Can LNA be removed from the receiver by suitably decreasing T_{SSB} ? Justify the answer quantitatively!

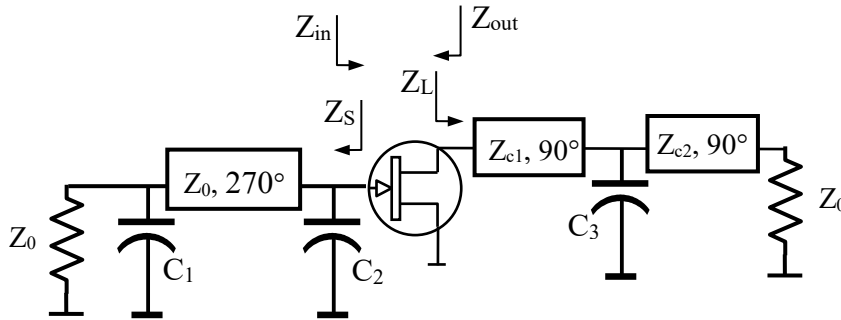Exercise 3 (11)

The following scheme represents a power amplifier (PA) operating at 2 GHz. The matching networks are required to present at input and output of the amplifier the optimum loads Z_S and Z_L , which determine the conjugate matching condition. The amplifier is then unconditionally stable, and the transducer gain G_T is equal to 6 dB. P_{1dB} of the transistor is 50 W.



$Z_S=(Z_{in})^*=(20-j35) \Omega$
 $Z_L=(Z_{out})^*=(2+j4) \Omega$
 $Z_0=50 \Omega$
 $Z_{c1}=20 \Omega$
 $Z_{c2}=?$
 $C_1, C_2, C_3=?$

- 1) Design the two networks (i.e. compute C_1, C_2, C_3, Z_{c2}). Hints: The networks can be assumed as matching networks that transform Z_{in} and Z_{out} into 50 Ohm respectively. Note that Z_S and Z_L are actual values (NOT normalized).
- 2) Assume a 2-tone as input signal. Compute the amplifier back off required for the carrier-to-intermodulation at output (CI) equal to 30 dB (assume $\Delta_p=9$ dB).
- 3) Compute the PEP and average power at amplifier output
- 4) The PA is operating in class AB. With the 2-tone signal at input the DC current absorbed from the bias source is 2.5 A (with $V_{cc}=16$ V). Evaluate the Power Added Efficiency (PAE) of the amplifier

Solutions

Exercise 1

The SNR is given by:

$$SNR = \frac{E_b}{N_0} \frac{R}{B} = 87 \text{ (19.3952 dB)}$$

The noise power at the satellite receiver is given by:

$$N_s = KT_s B = 7.45 \cdot 10^{-13} \text{ W}$$

Then the received power P_s must be: $P_s = N_s \cdot SNR = 6.55 \cdot 10^{-11} \text{ W}$.

Using the Friis equation we obtain the transmitted power from the Earth Station:

$$P_{TE} = \frac{P_s}{G_s G_e} \left(\frac{4\pi L}{\lambda_U} \right)^2 = 1704.2 \text{ W}$$

where λ_U is given by $c/f_U = 0.028 \text{ m}$.

The Friis equation for the down link determines the T_{eq} of the Earth receiver:

$$N_E = \frac{P_E}{SNR} = \frac{P_{TS} G_s G_e}{SNR} \left(\frac{\lambda_D}{4\pi L} \right)^2 = 6.2079 \cdot 10^{-15} \text{ W}$$

$$T_E = \frac{N_E}{KB} = 12.4957 \text{ °K}$$

Exercise 2

The received power in dBm at the satellite receiver is $P_{RS} = -71.84$ dBm (from the previous exercise).

The gain G_{IF} is obtained by imposing $P_d = -60$ dBm:

$$P_d = P_{RS} - A_0 + G_{LNA} - A_c + G_{IF} = -60 \text{ dBm} \rightarrow G_{IF} = 8.84 \text{ dB}$$


The possible local oscillator frequencies are given by

$$f_{LO} = f_{up} \pm 1 \text{ GHz} = (9.7 \text{ GHz}, 11.7 \text{ GHz})$$

The image frequencies are then:

$$f_{IM1} = f_{LO1} - 1 \text{ GHz} = 8.7 \text{ GHz}, f_{IM2} = f_{LO2} + 1 \text{ GHz} = 12.7 \text{ GHz},$$

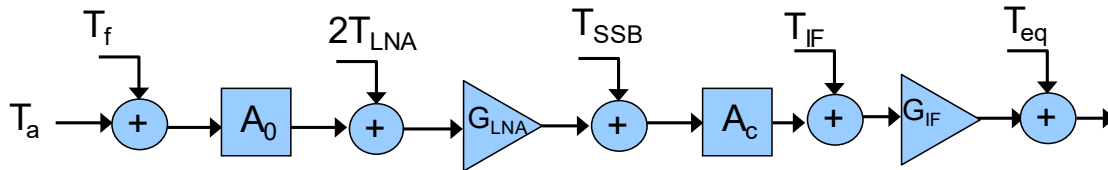Equivalent scheme (the factor 2 in front of T_{LNA} takes into account the image noise at the amplifier output):



The expression of T_{sys} results:

$$T_{sys} = T_a + T_f + 2T_{LNA}A_0 + \frac{A_0}{G_{LNA}}(T_{SSB} + T_{IF}A_c) + \frac{T_{eq}A_0A_c}{G_{LNA}G_{IF}}$$

Equating the above expression to the previously computed values we get the following expression for T_{LNA} :

$$T_{LNA} = \frac{1}{2A_0} \frac{A_0(T_{SSB} + T_{IF}A_c)}{T_{sys} - \left(T_a + T_f + \frac{T_{SSB}A_0}{G_{LNA}} + \frac{T_{eq}A_0A_c}{G_{LNA}G_{IF}} \right)} = 343 \text{ °K}$$

$$NF = 10 \cdot \log_{10} \left(1 + \frac{T_{LNA}}{293} \right) = 3.3659 \text{ dB}$$

Removing the amplifier the expression for T_{sys} becomes:

$$T_{sys} = T_a + T_f + A_0(T'_{SSB} + T_{IF}A_c) + \frac{T_{eq}A_0A_c}{G_{IF}} = 2477.4 + A_0T'_{SSB} = 1500$$

Obviously, this equation has no positive solution for T'_{SSB} , so the LNA cannot be removed.


Exercise 3

The first network is a double stub with load given by $Z_{in}=20+j35$. Using the Smith Chart we get for C_1 and C_2 :

$$B_1=0.786 \cdot 0.02=0.0157 \rightarrow C_1=B_1/(2\pi f_0)=1.25 \text{ pF}$$

$$B_2=1.568 \cdot 0.02=0.0314 \rightarrow C_2=B_2/(2\pi f_0)=2.495 \text{ pF}$$

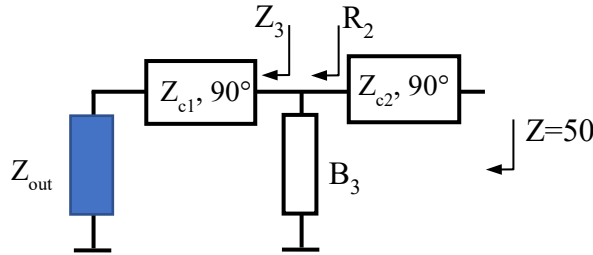For the second network, let consider the impedance Z_3 at the input of line 1 (loaded by $Z_{out}=(2-j4)$ Ohm):



$$Z_3 = \frac{Z_{c1}^2}{Z_{out}} = \frac{400}{2-j4} \Rightarrow Y_3 = \frac{1}{Z_3} = 5 \cdot 10^{-3} - j0.01$$

The susceptance B_3 must cancel the imaginary part of Y_3 so that the impedance Z_2 is real (R_2):

$$Z_2 = Y_3 + jB_3 = \frac{1}{R_2} \Rightarrow B_3 = j0.01, R_2 = \frac{1}{5 \cdot 10^{-3}} = 200 \Omega$$

The capacitance C_3 is then given by: $C_3 = B_3/(2\pi f_0) = 0.796 \text{ pF}$.

The resistance R_2 is transformed into 50 Ohm by selecting Z_{c2} as follows:

$$50 = Z_{c2}^2/200 \Rightarrow Z_{c2} = 100 \text{ Ohm}$$

$$BO = \frac{CI}{2} - \Delta_p - 3 = 3 \text{ dB}$$

$$P_m = P_{1dB} - BO = 25 \text{ W}, PEP = P_m + 3 = 50 \text{ W}$$

$$P_{in} = P_m - G_T = 6.25 \text{ W}, P_{DC} = 16 \cdot 2.5 = 40 \text{ W}$$

$$PAE = \frac{P_m - P_{in}}{P_{DC}} = 0.4688$$