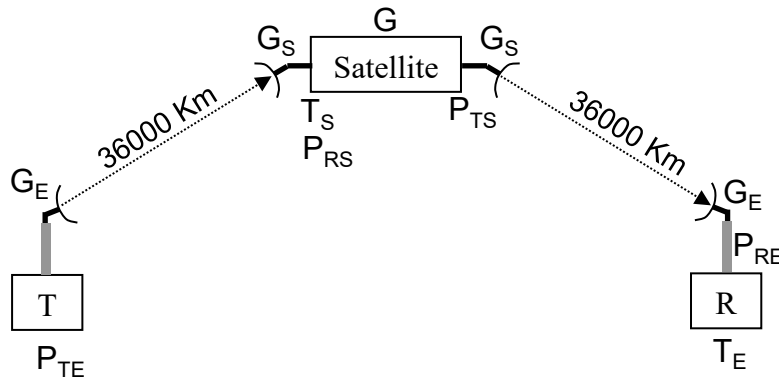



RF SYSTEMS
Written Test of July 14, 2021

Exercise 1




The figure shows a satellite communication system, defined by the following parameters: G_E =gain of the earth antennas; G_S =gain of the satellite antennas; G =Gain of the satellite ($=P_{TS}/P_{RS}$); P_{TE} =transmitted power from the earth station T; P_{TS} =transmitted power from the satellite; T_S =equivalent temperature of the satellite receiver; T_E =equivalent temperature of the earth station receiver; P_{RE} =Receiver power at earth station S; P_{RS} received power at satellite; up-link frequency: 6 GHz; down-link frequency: 4 GHz. All antennas are oriented for the maximum gain.

- 1) Write the Friis equation defining the received power at the earth station R as function of the transmitted power P_{TE} and the other system parameters.
- 2) It is known the directivity function of the earth antennas:
 $f_E(\theta)=1$ for $0<\theta<\theta_{max}$, $f_E(\theta)=0$ for $\theta_{max}<\theta<\pi$ $\theta_{max}=0.5^\circ$.
 Assuming the antennas efficiency $\eta=0.8$ evaluate the gain G_E .
- 3) The following parameters are assigned: $P_{TE}=500$ W; $P_S=100$ W; $G_S=20$ dB; $T_S=500^\circ\text{K}$; $T_E=100^\circ\text{K}$. Evaluate:
 - a. The total noise temperature T_{RT} of the satellite communication system.
 - b. The bit-error-rate (BER) with a data rate $R=100$ Mbit/s and 64-QAM modulation (the figure below shows the relationship between BER and E_b/N_0).
 - c. The signal bandwidth, assuming the roll-off factor $\alpha=0.5$

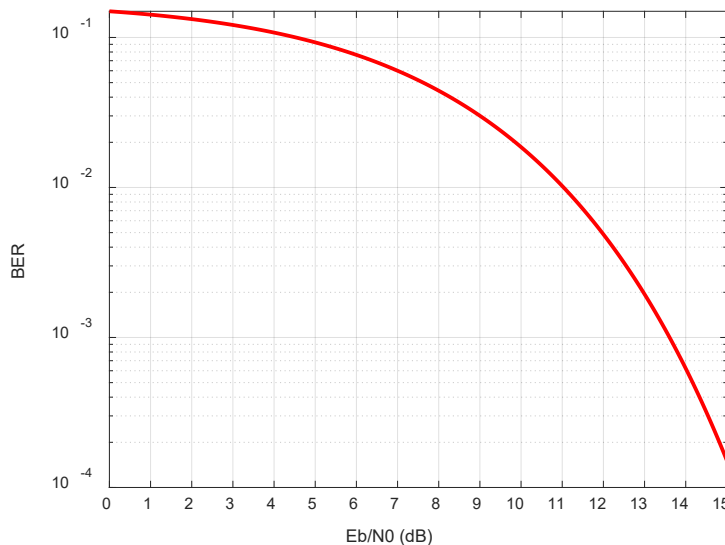


Exercise 2

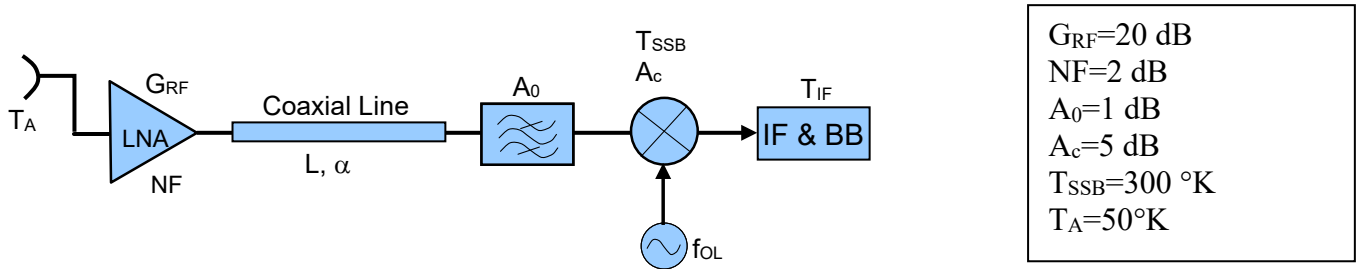

The scheme in the above figure represents the RF front-end of a receiver operating in 1800-1900 MHz band. The LNA is directly connected to the antenna, placed on the top of a mast 15 m height. The following part of the front-end is connected by means of a coaxial cable with length $L=15\text{m}$ and attenuation per unit length $a=0.1 \text{ dB/m}$. Note that the attenuation in the cable is produced by dissipation.

- 1) Assuming $f_{IF}=150 \text{ MHz}$ the intermediate frequency (IF) and $f_{OL}=2000 \text{ MHz}$ the local oscillator frequency, discuss the role of the filter, specifying why it is required and where its rejection band is located.
- 2) Draw the scheme of the front-end referred to the equivalent noise temperature contributions. Evaluate the system noise temperature at the input of the receiver assuming all the contributions after the mixer represented by $T_{IF}=1500 \text{ }^\circ\text{K}$.
- 3) In the proposed scheme there is no filter between the antenna and the LNA. Mention a possible drawback produced by this choice (justify the answer!).

Exercise 3

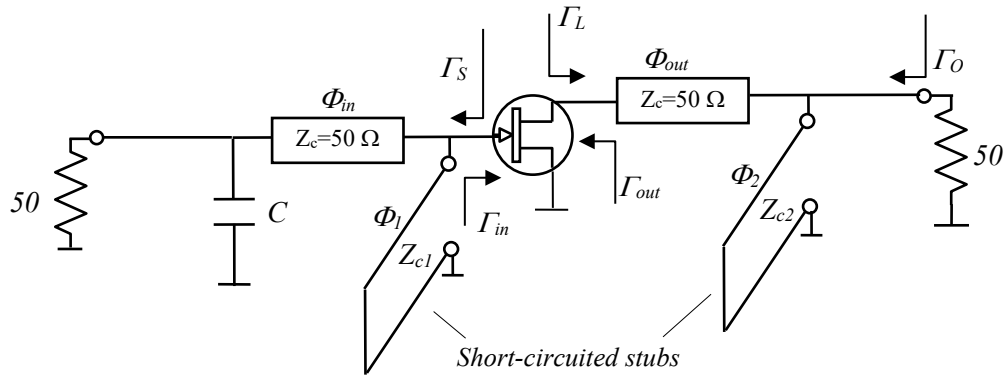

The amplifier in the above figure has been designed to operate at 12 GHz. The following data are given.

Parameters of active device: $S_{11}=0.7\angle -116^\circ$, $S_{21}=2.11\angle 84^\circ$, $S_{12}=0.1\angle 39^\circ$, $S_{22}=0.48\angle -56^\circ$, $\Gamma_{opt}=0.48\angle 155^\circ$, $F_{min}=2$ dB, $R_n=0.2$.

Input network: $C=0.023$ pF, $\Phi_{in}=135^\circ$, $\Phi_1=45^\circ$, $Z_{c1}=26.58 \Omega$

Output network: $\Phi_{out}=33.75^\circ$, $\Phi_2=45^\circ$, $Z_{c2}=24.15 \Omega$.

- 1) Evaluate the reflection coefficients Γ_S and Γ_L determined by the networks connected to the transistor.
- 2) Compute Γ_{in} and Γ_{out} using the Electronic Smith chart. Identify which termination of the transistor is conjugately matched (input or output). Evaluate consequently the Transducer Power gain and the noise figure.
- 3) What is the reflection coefficient Γ_O observed at the amplifier output ?

Solution

Exercise 1

1) $P_{RE} = P_{TE} \cdot G_E^2 \cdot G \cdot G_S^2 \left(\frac{\lambda_u}{4\pi R} \right)^2 \cdot \left(\frac{\lambda_d}{4\pi R} \right)^2$ $R=36 \cdot 10^6$ m, $\lambda_u=0.05$ m, $\lambda_d=0.075$ m

2) The formula to be used is: $G_E = \frac{2\eta}{1 - \cos(\theta_{\max})} = 4.2 \cdot 10^4$ (46.23 dB)

3) The total noise temperature is given by: $T_{RT} = T_{RE} + T_{RS} \cdot \frac{P_{RE}}{P_{RS}}$. The received powers are

computed as follows: $P_{RS} = P_{TE} \cdot G_E \cdot G_S \cdot \left(\frac{\lambda_u}{4\pi R} \right)^2 = 2.5665 \cdot 10^{-11} W$,

$P_{RE} = P_{TS} \cdot G_E \cdot G_S \cdot \left(\frac{\lambda_d}{4\pi R} \right)^2 = 1.1549 \cdot 10^{-11} W$. Replacing: $T_{RT} = T_{RE} + T_{RS} \cdot \frac{P_{RE}}{P_{RS}} = 325$ °K

4) The overall SNR of the system can be expressed as:


$$SNR_{sys} = \frac{P_{RE}}{KT_{RT}B} = \left(\frac{E_b}{N_0} \right) \left(\frac{R}{B} \right) \Rightarrow \frac{E_b}{N_0} = \frac{P_{RE}}{KT_{RT}R} = 25.751 \text{ (14.1 dB)}$$

From the graph we get $BER \approx 6 \cdot 10^{-4}$.

5) The signal bandwidth is expressed by: $B = \frac{R}{\log_2 M} \cdot (1 + \alpha) = 25$ MHz

Exercise 2

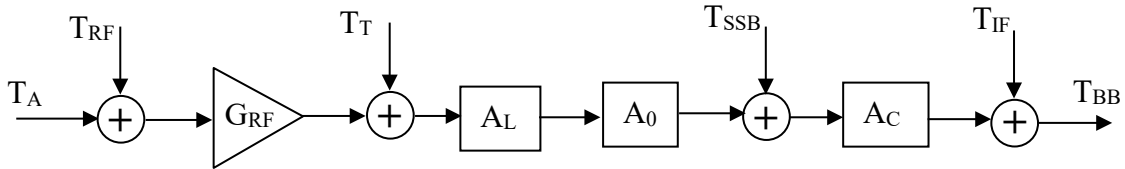- 1) The filter is required to eliminate the image band, which extends from $1800+2f_{IF}=2100$ to $1900+2f_{IF}=2200$ MHz.
- 2) The following scheme is required for the computation of T_{eq} (the image band is not considered because eliminated by the filter). Note that the transmission line is equivalent to an attenuator with attenuation $A_L=\alpha L$ (in dB).



$$T_{RF} = (10^{\frac{NF}{10}} - 1)T_0 = 171.37 \text{ °K}, \quad A_{T,dB} = A_L + A_0 = 0.1 \cdot 15 + 1 = 2.5 \text{ dB}$$

$$T_T = (A_T - 1)T_0 = 228.04 \text{ °K}$$

$$T_{eq} = T_A + T_{RF} + \frac{T_T}{G_{RF}} + \frac{T_{SSB}A_T}{G_{RF}} + \frac{T_{IF}A_C A_T}{G_{RF}} = 319.56 \text{ °K}$$

- 3) The absence of a filter before the LNA limits the dynamic range of the receiver (strong interferers outside the receiver band can lead the LNA to saturation)

Exercise 3

1. Enter the S parameters on the S. C. → Device potentially instable with MSG=13.24 dB
2. Evaluation of Γ_s : compute $b_c=2\pi f_0 C/Y_0=0.0867$. Enter the normalized admittance $y=1+j0.0867$ in the S.C; give a phase of gamma increment equal to $-2\Phi_{in}=-270^\circ$; evaluate the normalized susceptance of the stub: $y_n=-j(Z_0/Z_1)/\tan(\Phi_1)=-j1.8811$; give an increment to the susceptance equal to $-j1.8811$. Result: $\Gamma_s=0.7\angle 131.9^\circ$
3. Evaluation of Γ_L : evaluate the normalized susceptance of the stub: $y_n=-j(Z_0/Z_2)/\tan(\Phi_2)=-j2.0704$; Enter the normalized admittance $y=1-j2.070$ in the S.C; give a phase of gamma increment equal to $-2\Phi_{out}=-67.5^\circ$. Result: $\Gamma_L=0.719\angle 68.48^\circ$
4. Enter Γ_L as current point and select 'gamma IN'. We get: $\Gamma_{in}=0.873\angle -126.816^\circ$; Enter Γ_s as current point and select 'gamma OUT'. We get: $\Gamma_{out}=0.719\angle -68.427^\circ$. It is then $\Gamma_L \approx (\Gamma_{out})^*$, i.e. the output is matched. To evaluate G_T with the S.C. we enter Γ_s and select 'optimum gamma → Load': $G_T=11.99$ dB, NF=3.075 dB
5. Being the transistor output matched and the output network losses, the output reflection coefficient of the amplifier is zero.