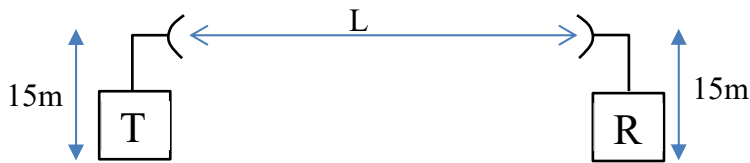


RF SYSTEMS
Written Test of June 17th, 2022

Surname & Name
Identification Number
Signature


Exercise 1



The figure shows a terrestrial link operating at 24 GHz with bandwidth $B=200$ MHz. The two stations are located L km away and the antennas are both placed on top of 15 m high towers. The gain of both antennas is $G=30$ dB, the transmitted power from T is $P_T=20$ dBm and the equivalent noise temperature of the receiving station is $T_{sys}=200$ °K.

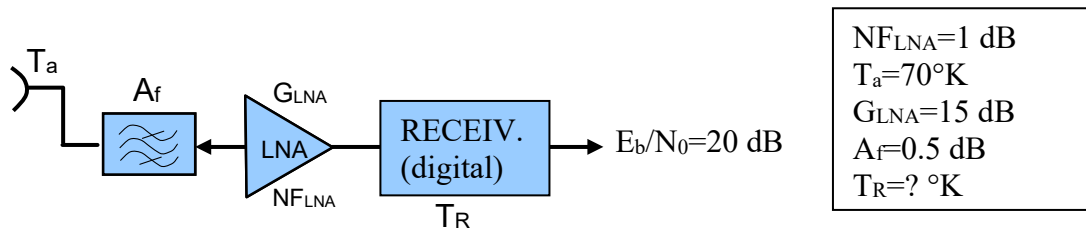- 1) Evaluate the maximum value of L (L_{max}) due to the earth surface curvature
- 2) Assuming the antennas optimally pointed, evaluate the received power for $L=L_{max}$.
- 3) The required value of the signal-to-noise ratio (SNR_{sys}) at R must be ≥ 22 dB. Chose the largest value of L satisfying this requirement and compute the received power and the corresponding value of SNR_{sys} .


Consider the following scheme for the receiving station R:



- 4) Evaluate the equivalent noise temperature of the digital receiver (T_R) compatible with the imposed T_{sys} .
- 5) Assuming $E_b/N_0=20$ dB at the receiver output, what is the maximum data rate DR?

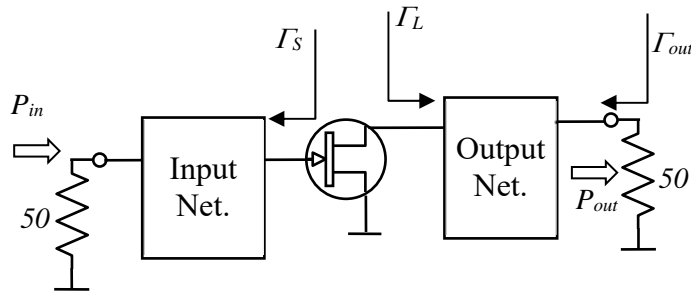Exercise 2

We want design a single stage amplifier at 10 GHz using the scheme in the following figure (input and output networks are lossless):



The transistor to be used has the following parameters:

$$S_{11}=0.57\angle 166^\circ \quad S_{21}=2.59\angle -21^\circ \quad S_{12}=0.144\angle -50^\circ \quad S_{22}=0.39\angle -148^\circ$$

$$\Gamma_{\text{opt}}=0.435\angle 168^\circ \quad F_{\text{min}}=1.15 \text{ dB} \quad R_n=0.095 \text{ (Noise parameters)}$$


3th order Intercept point (IP3): 26 dBm

The amplifier must exhibit the transducer gain as high as possible compatibly with the stability requirement and the noise figure not larger than 2 dB.

- 1) Select a proper value for Γ_S and Γ_L in order to satisfy the above requirements
- 2) Select as desired the topology of the input network and evaluate the values of the components
- 3) Assuming at input a 2-tone signal ($f_0=10 \text{ GHz}$, $\Delta f=200 \text{ MHz}$) with available mean power (P_{in}) equal to 0 dBm, evaluate the output mean power P_{out} . Compute also the power at each intermodulation frequency (specify the value of these frequencies)

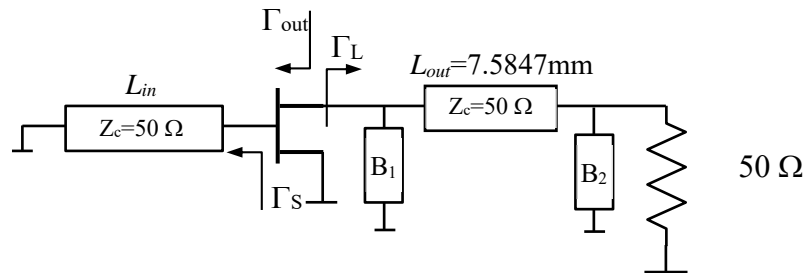Exercise 3

We want to design the oscillator in the figure operating at 10 GHz. Assume the transmission lines (TEM) filled with a dielectric material having $\epsilon_r=2.2$.



The S parameters of the active device at 10 GHz are given in the following table as function of the bias current:

I _{bias}	S ₁₁	S ₁₂	S ₂₁	S ₂₂
5 mA	0.745 \angle -162.9°	0.063 \angle -7.1°	1.875 \angle 25.1°	0.602 \angle -119.6°
10 mA	0.76 \angle -145°	0.06 \angle -1.2°	1.92 \angle 43.6°	0.603 \angle -105.3°
15 mA	0.864 \angle -93.4°	0.064 \angle 27.4°	2.545 \angle 93.8°	0.627 \angle -64.2°

- 1) Select the bias current (checking the necessary condition for the oscillation)
- 2) Imposing $|\Gamma_{out}|=1.1$, evaluate the required Γ_S and the length L_{in} of the input line so that the oscillation can start.
- 3) Compute the reflection coefficient Γ_L to be presented at the transistor output and design the output network (i.e. evaluate the susceptances B_1 and B_2)

Solution

Exercise 1

The maximum value of L in Km is given by $L_{\max} = 3.57 \cdot (\sqrt{H_1} + \sqrt{H_2})$ with $H_1=H_2=15\text{m}$. It is found $L_{\max}=27.65 \text{ Km}$.

The received power at R is obtained from the Friis equation (in logarithmic units):

$$P_R = P_T - 20 \cdot \log\left(\frac{4\pi L}{\lambda}\right) + 2G \text{ with } \lambda=c/f_0=12.5\text{mm. Replacing we get: } P_R=-68.78 \text{ dBm.}$$

The signal-to-noise ratio is defined as $\text{SNR}_{\text{sys}}=P_R/P_N$, with $P_N=KT_{\text{sys}}B=5.52 \cdot 10^{-13}$ (-92.58 dBm) the noise power at R. Imposing $\text{SNR}_{\text{sys}}=22 \text{ dB}$ we get $P_R=P_N \cdot \text{SNR}_{\text{sys}}=-70.58 \text{ dBm}$. Replacing in the Friis equation the value of L can be derived: $L=33.615 \text{ Km}$. This value is however larger than L_{\max} , so the maximum value of L that can be chosen is $L=L_{\max}=27.65 \text{ Km}$. For this value we get $P_R=-68.78 \text{ dBm}$ and $\text{SNR}_{\text{sys}}=-68.78+92.58=23.8 \text{ dB}$.

The expression of T_{sys} as function of the receiving front-end parameters is given by:

$$T_{\text{sys}} = T_a + T_f + a_f T_{LNA} + \frac{a_f T_R}{g_{LNA}} \text{ with } a_f = 10^{A_f/10}, T_f = 293 \cdot (a_f - 1), T_{LNA} = 293 \cdot (10^{NF_{LNA}/10} - 1), g_{LNA} = 10^{G_{LNA}/10} .$$

$$\text{Deriving } T_R \text{ we get: } T_R = \frac{g_{LNA}}{a_f} (T_{\text{sys}} - (T_a + T_f + a_f T_{LNA})) = 257.22 \text{ }^\circ\text{K} .$$

We know that $\text{SNR}_{\text{sys}}=(E_b/N_0)(DR/B)$. Then, it has $DR=B \cdot \text{SNR}_{\text{sys}}/(E_b/N_0)=479.77 \text{ Mbit/sec}$.

Exercise 2

After entering the transistor parameters in the S.C. we found that the device is potentially unstable with $G_{max}=12.549$ dB.

As the problem requires a minimum noise figure $NF=2$ dB, we draw on the S.C. the corresponding noise figure circle. Then we look for a point (Γ_S) on this circle determining the largest Available Gain (G_{AV}). This point is the one where the circle with constant G_{AV} is tangent to the circle with constant NF. It is found $\Gamma_S=0.648\angle-157.34^\circ$ and $G_{AV}=11.825$ dB.

The value of Γ_L is obtained by imposing the conjugate matching at the transistor output. Using the S.C. we get $\Gamma_L=0.609\angle174.95^\circ$. Once this is imposed, it has $G_T=G_{AV}=11.825$ dB.

A single stub network can be easily designed for the input network:

The value of Γ_S is entered in the S.C. and stored in memory. The circle with constant gamma passing through the current point is drawn together with the circle with $g=1$. The first intersection of the two circles in the direction of the load is selected and the phase in the Delta Gamma tab gives the length of the transmission line: $\Phi=27.07/2=13.535^\circ$. The imaginary part of Y (current point) gives the value of $b=1.695$.

The value of P_{out} is given by $P_{out}=P_{in}+G_T=11.825$ dBm. The power in each line is $P_0=11.825-3 = 8.825$ dB. The power in the intermodulation lines is computed by the following formula:
 $P_{int}=3P_0 - 2IP_3=-25.525$ dBm.

Exercise 3

The bias selection is carried out by checking the oscillation condition (potential instability). It is found that only for $I_B=15\text{mA}$ this condition is verified.

To select Γ_S , we draw the source mapping circle with $|\Gamma_{\text{out}}|=1.1$. Being Γ_S generated by a lossless network (the short-circuited stub), the point to be selected on this circle must be on the intersection with the outer circle ($|\Gamma_S|=1$). We have selected $\Gamma_S=1\angle 89.78^\circ$. Being generated by a S.C. stub, it holds true $\Gamma_S=\exp(\pi-2\phi_{\text{in}})$, where ϕ_{in} is the electrical length of the line: $\phi_{\text{in}}=\beta L_{\text{in}}=(\pi-\phi_S)/2$. From this latter we get: $L_{\text{in}} = \frac{\phi_{\text{in}}}{\beta} = \frac{c}{f_0\sqrt{\epsilon_r}} \frac{\pi - \phi_S}{4\pi} = 2.534 \text{ mm}$.

Once Γ_S is assigned, the value of Γ_{out} can be obtained by the S.C.: $\Gamma_{\text{out}} = 1.1 \angle -137.25^\circ$. y_{out} is also available: $y_{\text{out}}=-0.346+j2.514$. We then assign $y_L=-g_{\text{out}}/3-b_{\text{out}}=0.115-j2.514$, which corresponds to $\Gamma_L=0.969\angle 136.688^\circ$.

The design of the output network starts drawing the circle $g=1$ rotated by $2\beta L_{\text{out}}=270^\circ$ in the source direction, together with the circle with $g=\text{const}$ passing through Γ_L . The value of Γ_L is then entered and stored in memory. We select the first intersection between the two circles and read the value in the Delta Y tab (imaginary part). This value, with the sign reversed, represents $b_1=-3.98$. We then move the current point in the load direction by 270° and get as new current point $y=1-j5.049$. The value of b_2 is the imaginary part of y : $b_2=-5.049$.