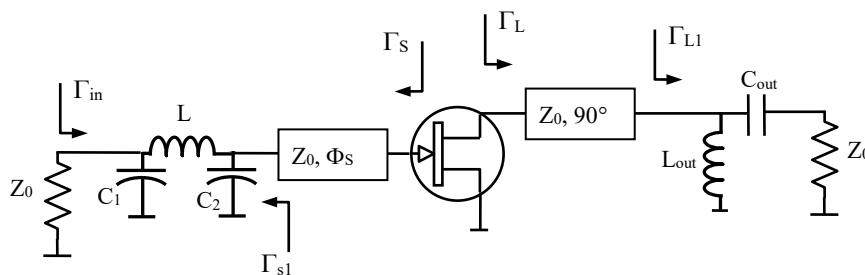


RF SYSTEMS – End Term test
22th January 2020

Surname & Name
Identification Number
Signature

Exercise 1

The following scheme shows a an amplifier operating at 6.5 GHz ($Z_0=50\ \Omega$)



The transistors are characterized by the following parameters ($Z_0=50\ \Omega$):

$$S_{11}=0.814\angle -144.78^\circ, S_{12}=0.075\angle -15.38^\circ, S_{21}=2.612\angle 45.62^\circ, S_{22}=0.55\angle -108.91^\circ$$

$$NF_{\min}=1\ \text{dB}, \Gamma_{\min}=0.8\angle 122^\circ, r_n=0.26$$


Note that the transistor is potentially instable with $MSG=15.4\ \text{dB}$

The input network is constituted by an assigned PI circuit ($C_1=0.6\ \text{pF}$, $L=3.82\ \text{nH}$, $C_2=0.182\ \text{pF}$), followed by a transmission line with electrical length Φ_S and characteristic impedance Z_0 . Note that Γ_{s1} and Γ_s differ only by the phase value.

- 1) The Power Gain (G_P) of the amplifier is required to be 15 dB. Chose a real value of Γ_L in order this requirement is satisfied
- 2) Evaluate Γ_s in order to get the Transducer Gain (G_T) equal to G_P .
- 3) Evaluate Γ_{s1} from the assigned PI network with the electronic Smith Chart. Verify that $|\Gamma_s|=|\Gamma_{s1}|$
- 4) Compute the electrical length Φ_S to get the required Γ_s .
- 5) Design the transforming network at output. Note that L network transforms $50\ \Omega$ into Γ_{L1} , which can be evaluated from Γ_L being the electrical length of the output line assigned ($\Phi = 90^\circ$). Note: the computed values of the lumped components in the network must be positive!
- 6) Evaluate the noise figure and the input reflection coefficient Γ_{in} of the amplifier

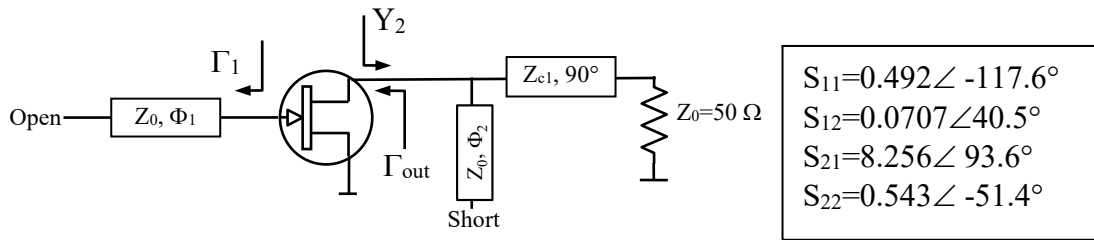Exercise 2

The following scheme refers to an oscillator working at $f_{osc}=2$ GHz. The S parameters of the transistor are also reported on the figure (defined with respect to $Z_0=50 \Omega$).



- 1) Find the value of Γ_1 (realizable with the assigned network) that determines the maximum of $|\Gamma_{out}|$. Hint: draw various mapping circles of Γ s with increasing value of $|\Gamma_{out}|$ until the mapping circle does not intersect the unit circle.
- 2) Evaluate the electrical length Φ_1 of the input stub.
- 3) From Γ_{out} evaluate the admittance Y_2 and compute the parameters Φ_2 and Z_{c1} of the output network. Hint: the 90° line transforms the load impedance into a pure resistance; the short-circuited stub add a pure susceptance in parallel to the transformed resistance.
- 4) Assuming about constant the S parameters, verify if the oscillation is still possible at 2.35 GHz

Solutions

Exercise 1

- 1) Draw the circle $G_P=15$ dB and select the intersection with the real axis. $\Gamma_L=0.389\angle 180^\circ$.
- 2) To get $G_I=G_P$ we must impose the input matched. Then $\Gamma_S = \Gamma_{in}^* = 0.893\angle 144.13^\circ$.
- 3) First we must evaluate the normalized susceptance and reactance of the circuit elements:

$$b_1 = \frac{2\pi f_0 C_1}{Y_0} = 1.225, \quad b_2 = \frac{2\pi f_0 C_2}{Y_0} = .3717, \quad x = \frac{2\pi f_0 L}{Z_0} = 3.12$$

We enter the current point in the S.C. as the admittance with $g=1$ and $b=b_1$. Then we give the following increments: reactance=3.12, susceptance=.3717. We get $\Gamma_{s1}=0.893\angle 0$. Actually $|\Gamma_S|=|\Gamma_{s1}|$.

- 4) Store Γ_s . Enter Γ_{s1} . The phase of Delta Gamma divided by 2 is the length $\Phi_S=107.94^\circ$
- 5) First evaluate Γ_{L1} by increasing of 180° the phase of Γ_L . $\Gamma_{L1}=0.389\angle 0^\circ$. Then evaluate b_{out} and x_{out} with the S.C. Note that both of them must be negative to be implemented with the imposed components. We get: $b_{out}=-0.496$, $x_{out}=-1.129$. Then we derive the lumped components:

$$L_{out} = -\frac{1}{2\pi f_0 \cdot b_{out} \cdot Y_0} = 2.47 \text{ nH}, \quad C_{out} = -\frac{1}{2\pi f_0 \cdot X_{out} \cdot 50} = 0.434 \text{ pF}$$

- 6) To get the noise figure we enter Γ_S in the S.C. and ask for the optimum Γ_L . We get NF=3 dB. The input reflection coefficient is zero because we imposed the input matched (and the input network is lossless).

Exercise 2

- 1) Following the suggestion we get $|\Gamma_1|=1\angle 129.1$ with $|\Gamma_{out}|=1.58$.
- 2) Store Γ_1 . Enter the open circuit ($\Gamma=1$). The increment of Delta Gamma Phase divided by 2 is $\Phi_1=115.44^\circ$.
- 3) With the computed Γ_1 we get $Y_{out}=-0.348+j0.705$. Then $Y_L=0.115-j0.705$. The short-circuited stub must produce $b=-0.705 \rightarrow x=1.4184 \rightarrow \Phi_2=\text{atan}(x)=54.82^\circ$. The 90° line must transform 50 Ohm into $1/(0.02 \cdot 0.115)=434.78$ Ohm. We get $Z_{c1} = \sqrt{50 \cdot 434.78} = 147.44 \Omega$.
- 4) At $f=2.35$ GHz the electrical length of the input line becomes: $\Phi'_1 = \Phi_1 \frac{f}{f_0} = 135.64^\circ$. Then $\Gamma_1=1\angle 88.72^\circ$. Entering this value in the S.C. we get $|\Gamma_{out}|=0.93$ then oscillation is not possible.