

RF SYSTEMS
Written Test of February 22th, 2017

Surname & Name
Identification Number
Signature

Exercise 1

It is known the directivity function of an antenna operating at 300 MHz:


$$f(\theta) = \frac{25 \cdot \sqrt{5}}{16} \sin^4(\theta) \cos(\theta) \text{ for } 0 < \theta < 90^\circ, f(\theta) = 0 \text{ elsewhere.}$$

- 1) Evaluate the value of θ where f is maximum (θ_{max}). Hint: You can find θ_{max} either numerically or analytically, remembering that $(f(x) \cdot g(x))' = f'(x) \cdot g(x) + f(x) \cdot g'(x)$
- 2) Evaluate the directivity gain D_M . Recall: $\int f^n(x) f'(x) dx = \frac{f^{n+1}(x)}{n+1}$
- 3) Evaluate the minimum efficiency of the antenna which determines the gain G equal to 5 dB
- 4) Assuming that the antenna is used in reception, evaluate the output voltage determined by an incident wave arriving from the direction $\theta_{inc} = 45^\circ$ with power density $S_R = 10^{-8} \text{ W/m}^2$. Assume that the radiation impedance of the antenna is 50Ω and the load Z_L connected to the antenna is matched ($Z_{rad} = Z_L^*$).

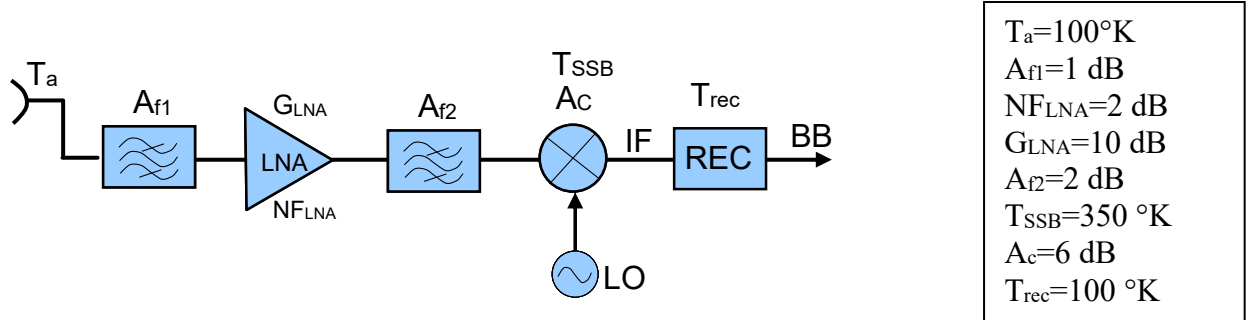Exercise 2

Consider the following scheme of a receiver operating at 6 GHz (signal band 20 MHz). The block REC represents the demodulator at intermediate frequency (IF), producing the bit streaming in base band (BB). It is characterized by the noise temperature T_{rec} (at input).


Assume that the filters eliminate completely the image band (no noise contribution at IF).



- 1) Evaluate the equivalent noise temperature at the input of the receiver (T_{eq}).
- 2) Assuming $E_b/N_0=20\text{ dB}$, what is the minimum signal power at IF allowing a data rate $R=40\text{ Mbit/sec}$?
- 3) If we want remove the LNA and the second filter, we must improve the mixer in order to get the receiver performances unchanged (i.e. the same T_{eq} computed above). Assuming that the new value of the mixer losses is $A'_c=3\text{ dB}$, what is the new value of T_{SSB} ?

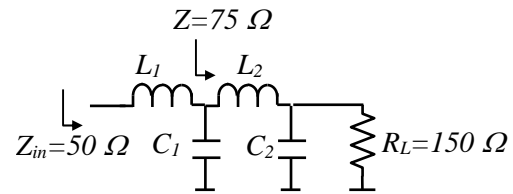Exercise 3

Consider the following matching network operating at 1 GHz:




Imposing the intermediate impedance $Z=75 \Omega$, evaluate the value of L_1 , L_2 , C_1 , C_2 that determines the input impedance $Z_{in}=50 \Omega$. Note: explain clearly the procedure adopted for the computation. Reporting only the final values without any explanation is not accepted

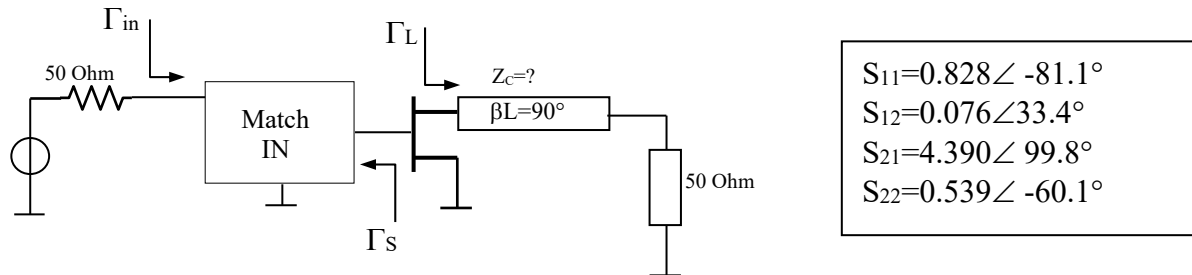Exercise 4

We want to design the amplifier in the figure operating at 2 GHz, with matching at input ($\Gamma_{in}=0$). It is known that the Match IN network is lossless.

The S parameters of the active device at 2 GHz are given in the following table.



- 1) Evaluate Γ_s and Γ_L in order to get the highest transducer gain compatibly with stability and the matching requirement (note that the Γ_L selected must be realizable with the output network assigned)
- 2) Evaluate the characteristic impedance Z_c of the output transmission line.

Solution

Exercise 1

1) To find the angle θ_{\max} we compute the derivative of $f(\theta)$ and equate to 0:

$$\begin{aligned} f'(\theta) &= 4 \sin^3(\theta) \cos^2(\theta) - \sin^5(\theta) = \sin^3(\theta) [4 \cos^2(\theta) - \sin^2(\theta)] = \\ &= \sin^3(\theta) [5 \cos^2(\theta) - 1] = 0 \quad \Rightarrow \quad \theta_{\max} = \cos^{-1}\left(\frac{1}{\sqrt{5}}\right) = 63.43^\circ \end{aligned}$$

$$2) D_M = 4\pi \left[\int_0^{2\pi} d\varphi \int_0^{\pi/2} f(\theta) \sin\theta d\theta \right]^{-1} = \frac{2 \cdot 16}{25 \cdot \sqrt{5} \int_0^{\pi/2} \sin^5(\theta) \cos(\theta) d\theta} = \frac{2 \cdot 16 \cdot 6}{25 \cdot \sqrt{5} \sin^6\left(\frac{\pi}{2}\right)} = 3.43 \text{ (5.36 dB)}$$

$$3) G = \eta D_{\max} \Rightarrow \eta = 10^{(5.36-5)/10} = 0.921$$

$$4) A_e = \lambda^2 \frac{G}{4\pi} = 0.251 \text{ m}^2, \quad P_r = S_R A_e f(45^\circ) = 10^{-8} \cdot 0.251 \cdot 0.6176 = 1.55 \cdot 10^{-9} \text{ W}$$

$$P_r = \frac{1}{8} \frac{|V_{\max}|^2}{50} \Rightarrow |V_{\max}| = \sqrt{50 \cdot 8 \cdot P_r} = 0.788 \cdot 10^{-3} \text{ V}$$

Exercise 2

1) Evaluation of T_{eq} :

$$T_{eq} = T_a + T_{f1} + T_{LNA} A_{f1} + T_{f2} \frac{A_{f1}}{G_{LNA}} + T_{SSB} \frac{A_{f1} A_{f2}}{G_{LNA}} + T_{rec} \frac{A_{f1} A_{f2} A_c}{G_{LNA}} = 559.25 \text{ }^\circ\text{K}$$

$$T_{f1} = 290 \left(10^{\frac{A_{f1}}{10}} - 1 \right) = 75.088^\circ\text{K}, \quad T_{f2} = 290 \left(10^{\frac{A_{f2}}{10}} - 1 \right) = 169.62^\circ\text{K}$$

$$T_{LNA} = 290 \left(10^{\frac{NF}{10}} - 1 \right) = 169.62^\circ\text{K}$$

2) Evaluation of P_{IF} :

$$SNR_{sys} = \frac{P_r}{KT_{eq} B} = \left(\frac{E_b}{N_0} \right) \frac{R}{B} = 20 + 10 \log(40/20) = 23 \text{ dB}$$

$$KT_{eq} B = 1.38 \cdot 10^{-23} \cdot 559.25 \cdot 20 \cdot 10^6 = 1.543 \cdot 10^{-13} \text{ (-128.1 dBW)}$$

$$P_r = SNR_{sys} + KT_{eq} B \Big|_{dBW} = -105.1 \text{ dBW}$$

$$P_{IF} = P_r - A_{f1} - A_{f2} - A_c + G_{LNA} = -104.1 \text{ dBW}$$

3) Evaluation of T'_{SSB} :

$$T'_{eq} = T_a + T_{f1} + T'_{SSB} A_{f1} + T_{rec} A_c A_{f1} = T_{eq}$$

$$T'_{SSB} = \frac{T_{eq} - (T_a + T_{f1} + T_{rec} A_c A_{f1})}{A_{f1}} = 105.62 \text{ }^\circ\text{K}$$

Exercise 3

For the second network (the closed to the load):

$$B_{p2} = \sqrt{\frac{1}{R_L} \left(\frac{1}{Z} - \frac{1}{R_L} \right)} = \frac{1}{150} \left[\sqrt{\frac{150}{75} - 1} \right] = 6.666 \cdot 10^{-3} \text{ S}, \quad X_{s2} = Z \left[\sqrt{\frac{R_L}{Z} - 1} \right] = 75 \text{ } \Omega$$

$$C_2 = \frac{B_{p2}}{2\pi f_0} = 1.061 \text{ pF}, \quad L_2 = \frac{X_{s2}}{2\pi f_0} = 11.94 \text{ nH}$$

For the first network (the closed to the source):

$$B_{p1} = \sqrt{\frac{1}{Z} \left(\frac{1}{Z_{in}} - \frac{1}{Z} \right)} = \frac{1}{75} \left[\sqrt{\frac{75}{50} - 1} \right] = 9.428 \cdot 10^{-3} \text{ S}, \quad X_{s1} = Z_{in} \left[\sqrt{\frac{Z}{Z_{in}} - 1} \right] = 35.35 \text{ } \Omega$$

$$C_1 = \frac{B_{p1}}{2\pi f_0} = 1.5 \text{ pF}, \quad L_1 = \frac{X_{s1}}{2\pi f_0} = 5.63 \text{ nH}$$

Exercise 4

We draw the circle $G_p=17 \text{ dB}$ ($<MSG=17.62 \text{ dB}$). Then select one of the points on this circle crossing the horizontal axis: $\Gamma_L=0.195$, to which corresponds $\Gamma_S=(\Gamma_{in})^*=0.77 \angle 83.56^\circ$. Being the output matched: $G_T=G_P=17 \text{ dB}$.

The impedance Z_L corresponding to Γ_L is $Z_S=50 \cdot 1.485=72.25 \text{ } \Omega$. Then $Z_c=\sqrt{50 \cdot 72.25}=60.93 \text{ } \Omega$.