

RF SYSTEMS
Written Test of July 25th, 2022

Surname & Name
Identification Number
Signature


Exercise 1

The Mars Reconnaissance Orbiter (MRO) was launched in 2005 to study the geology and climate of Mars. It is equipped with a digital transmitter operating at 8.439 GHz (transmitted power $P_T=100$ W). The antenna of the spacecraft is a 3m dish with aperture efficiency $e_a=0.6$. The receiving station on the Earth has a 70m dish antenna with $e_a=0.65$ and the (G/T) parameter of the receiving station is 60 dB (T represents the equivalent noise temperature of the receiver).

Assuming the required E_b/N_0 equal to 10 dB and the average distance (L) between Earth and MRO equal to $60 \cdot 10^6$ Km, answer the following questions.

- 1) Evaluate the gain of both antennas and the half-power beamwidth θ_{3dB} of the Earth station antenna (assume the directivity gain of the earth antenna (D) about equal to its gain G)
- 2) Evaluate the power received by the Earth station and the data rate R allowed by the assigned E_b/N_0 , including in the link losses a supplementary attenuation $A_S=10$ dB to account for possible atmospheric events (rain, etc).
- 3) MRO is equipped with a camera which takes high resolution pictures of the Mars surface (max resolution: 800 Mpixels). Each photo (16.4 Gbit) is compressed to 5 Gbit before transmission to Earth. Considering that MRO is occulted from the Earth for about 1/3 of the orbit time around Mars, the data can be sent to Earth for 10 hours a day. How many high-resolution photos can be sent in a day?

Exercise 2

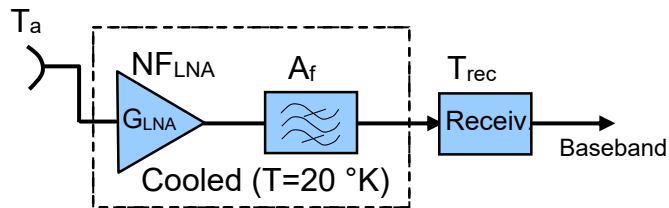

$T_a = 10^\circ\text{K}$
$NF_{LNA} = ?$
$G_{LNA} = 20 \text{ dB}$
$A_f = 0.5 \text{ dB}$
$T_{rec} = 100^\circ\text{K}$


The scheme in the above figure represents the front-end of the Earth Station receiver of exercise 1 (note that the low noise amplifier and the filter are cooled at 20°K).

- 1) Draw the equivalent scheme including the noise sources (equivalent temperatures) and write the expression of the system temperature (T_{sys})
- 2) Imposing the value of T_{sys} previously computed, evaluate the noise figure of the LNA
- 3) If the system SNR must be 13 dB, what is the system bandwidth?

Note: in case the previous exercise has not been solved assume $T_{\text{sys}} = 25^\circ\text{K}$.

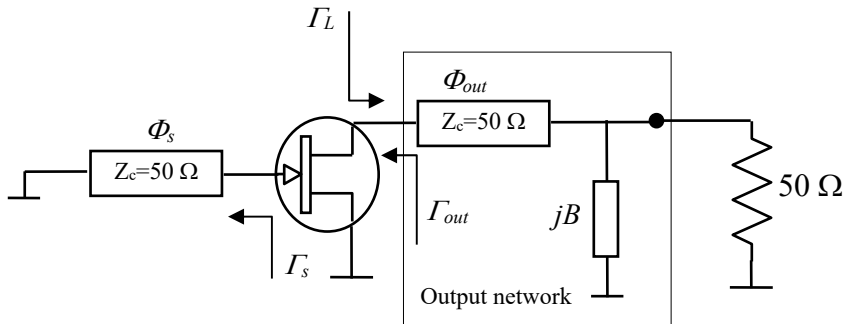Exercise 3

We want design the oscillator in the following figure, operating at 5 GHz:



The scattering parameters of the transistor are given by:

$$S_{11} = 0.844 \angle -62.3^\circ, S_{21} = 5.273 \angle 121.7^\circ, S_{12} = 0.069 \angle 42.7^\circ, S_{22} = 0.521 \angle -52.6^\circ$$

- Select a value for Γ_s and evaluate the electrical length Φ_s of the first line. (Hint: set $|\Gamma_{out}| = 1.2$ and select the Γ_s which determines the minimum value of Φ_s)
- Design the output network, once the required value of Γ_L has been computed

Solutions

Exercise 1

- 1) The gain is computed with the following formula:

$$G = A_e \frac{4\pi}{\lambda^2} = \left(e_a \frac{1}{4} \pi d^2 \right) \frac{4\pi}{\lambda^2} = e_a \left(\frac{d\pi}{\lambda} \right)^2$$

with $\lambda = c/f_0 = 0.0355$ m. Replacing e_a and d we get $G_S=46.25$ dB, $G_E=73.96$ dB.

The half-power beamwidth can be assumed equal to the aperture of the cone with constant gain G:

$$\Delta\theta = 2 \cos^{-1} \left(1 - \frac{2}{D_{MAX}} \right) \cong 2 \cos^{-1} \left(1 - \frac{2}{G} \right) = 0.046^\circ$$

- 2) The received power is obtained from the Friis equation:

$$P_R = P_T - 20 \log_{10} \left(\frac{4\pi L}{\lambda} \right) + G_E + G_S - A_S \quad (\text{logarithmic units})$$

with $P_T=20$ dBm, $L=6 \cdot 10^{10}$ m, $A_S=10$ dB. Replacing, we get $P_R=-136.32$ dBW.

The data rate (R) is related to the signal-to-noise ratio:

$$SNR_{sys} = \frac{P_r}{KT_{sys} B} = \left(\frac{E_b}{N_0} \right) \left(\frac{R}{B} \right) \Rightarrow R = \frac{P_r}{KT_{sys} (E_b/N_0)}$$


T_{sys} is obtained from (G/T)=60 dB: with $G_E=73.96$ it has $T_{sys}=13.96$ dB $\rightarrow 24.89$ °K.

Replacing in the formula ($K=1.38 \cdot 10^{-23}$) we get $R=6.79$ Mbit/sec

- 3) Each photo requires the transmission of 5 Gbit at R bit/sec, so the transmission time results $t_{ph} = 5 \cdot 10^9 / 6.79 \cdot 10^6 = 736.38$ sec. The number of transmitted photos in 10 h (=36000 sec) is then given by $N_{ph} = \text{int}(36000/736.38) = 48$.

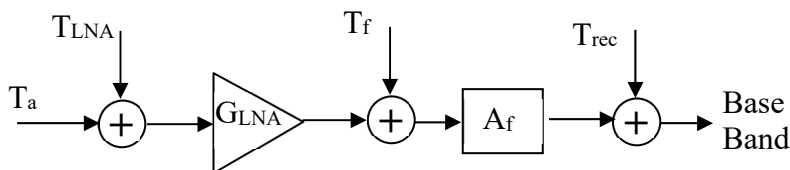Exercise 2

Equivalent scheme with the noise sources:



T_{sys} is the equivalent system temperature defined at the input:

$$T_{sys} = T_a + T_{LNA} + \frac{T_f}{G_{LNA}} + T_{rec} \frac{A_f}{G_{LNA}}$$

Imposing $T_{sys}=24.89$ °K and $T_f=T_0(10^{(A_f/10)}-1)=2.44$ °K (note that $T_0=10$ °K) we get T_{LNA} :

$$T_{LNA} = T_{sys} - T_a - \frac{T_f}{G_{LNA}} - T_{rec} \frac{A_f}{G_{LNA}} = 24.89 - 10 - 2.44/100 - 100 \cdot 1.122/100 = 13.74$$
 °K

Then $NF=10 \cdot \log_{10}(1+T_{LNA}/T_0)=2.27$ dB

With SNR=13 dB we have:

$$SNR_{sys} = \frac{P_r}{KT_{sys} B} = 20 \Rightarrow B = \frac{P_r}{KT_{sys} 20} = 3.4 \text{ MHz}$$

Exercise 3

After entering the S parameters in the S.C. we discover that the transistor is potentially unstable ($K=0.399$) so the design of the oscillator is possible.

- a) The mapping circle with $|\Gamma_{out}|=1.2$ is then drawn and one of the intersections with the outer circle defines the value of Γ_s . The one to be selected is the closest to the short circuit, i.e. $\Gamma_s=1\angle 94.493^\circ$. It has then $\phi_s=(180-94.493)/2=42.75^\circ$.
- b) The value of Z_{out} is then obtained from the S.C.: $Z_{out}=-0.538-j2.163$. The load impedance is then given by $Z_L=0.538/3+j2.163=0.179+j2.163$ ($\Gamma_L=0.939\angle 49.379^\circ$).
To design the output network the circle with $|\Gamma_L|=0.939$ is first drawn together with the circle $g=1$. The current point (Γ_L) is stored and the first intersection of the two circles is selected ($\Gamma=0.939\angle 159.91^\circ$). The phase of Delta Gamma tab determines the length $\phi_{out}=110.532/2=55.266$. The current admittance tab gives $Y=1-j5.468$ then $B=-5.468$.