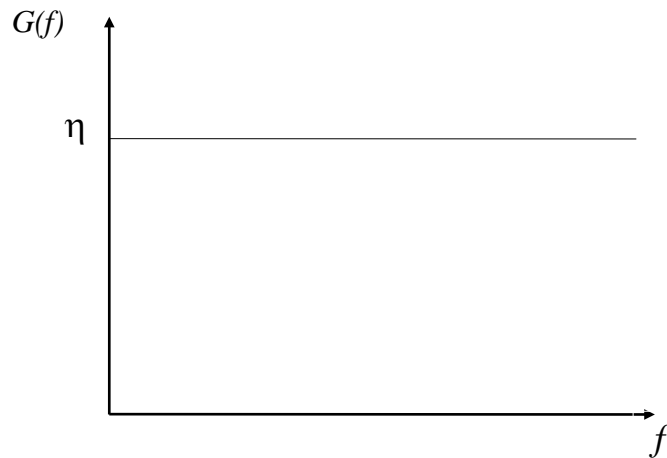


Main Sources of Electronic Noise

Thermal Noise

- It is always associated to dissipation phenomena produced by currents and voltages. It is represented by a voltage or current sources randomly variable in time.
- It is analytically described by a stationary process
- Amplitude distribution: GAUSSIAN with zero mean value
- Power Spectral Density: constant (white noise)




$$\eta = \text{Power spectral density} = K \cdot T$$

Main Sources of Electronic Noise

Shot noise

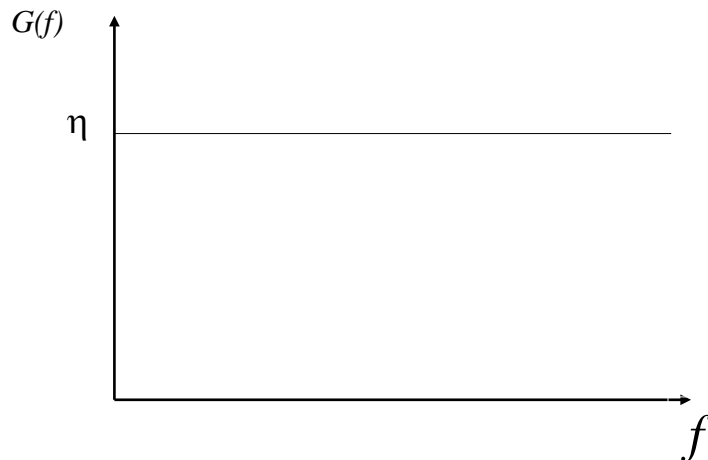- It arises typically in *PN junctions* forwardly biased; it is due to the discrete nature of current through the junction, which results randomly variant around the imposed bias value
- Amplitude distribution: GAUSSIAN with zero mean value
- Constant spectrum (white noise)



$$\eta = \text{Power spectral density } (=2q \cdot I)$$

Main Sources of Electronic Noise

Flicker noise (1/f)

1. It arises in semiconductor devices, due to impurities and defects in the crystal structure).
2. Its spectrum is not constant (energy is concentrated at low frequency).

Power Spectrum:

$$G(f) = \bar{K} \frac{I^a}{f^b} \quad W / Hz$$

K: depends on the fabrication process


I: DC current through the device

a: typically 0.5 ÷ 2

b: $\cong 1$

Nota: The amplitude distribution is not always GAUSSIAN

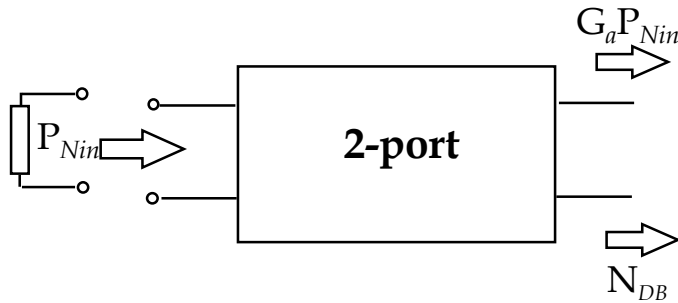Noise Characterization in microwave devices



N_{DB} = Added Power (from the 2-port)

$P_{Nout} = G_a P_{Nin} + N_{DB}$ = Total noise Power

The noise figure NF: define the attitude of the 2-port of adding noise at the output:

$$NF = \frac{P_{Nout}}{G_a \cdot P_{Nin}}$$

P_{Nout} is the actual noise power at output while $G_a \cdot P_{Nin}$ is the noise power at output if the 2-port would not add noise power (G_a is the available power)

Actually NF is a function of frequency, so the above powers must be assumed per unit band (i.e. they represent actually power densities). Moreover NF depends also on the source impedance Γ_s (being G_a depending on Γ_s)

NF dependance on Γ_s

$$NF = (NF)_{min} + 4r_n \frac{|\Gamma_s - \Gamma_{min}|^2}{|1 + \Gamma_{min}|^2 \cdot (1 - |\Gamma_s|^2)}$$

- $(NF)_{min}$ = Minimum value of NF
- Γ_{min} value of Γ_s which determines $NF = NF_{min}$
- r_n = Normalized noise resistance

All these parameters are frequency dependent. Typically, they are made available by the manufacturers of commercial devices (directly into .s2p data files).

Constant Noise Figure Circles


If we plot the equation expressing NF as function of Γ_S on the Smith Chart (representing Γ_S), we obtain a circle with the following center and radius:

$$C_F = \frac{\Gamma_{min}}{1 + N_i}, \quad r_F = \frac{1}{1 + N_i} \sqrt{N_i^2 + N_i (1 - |\Gamma_m|^2)}$$

N_i is given by:

$$N_i = \frac{NF - (NF)_{min}}{4r_n} \cdot (1 + |\Gamma_{min}|^2)$$

Noise Figure for cascaded stages

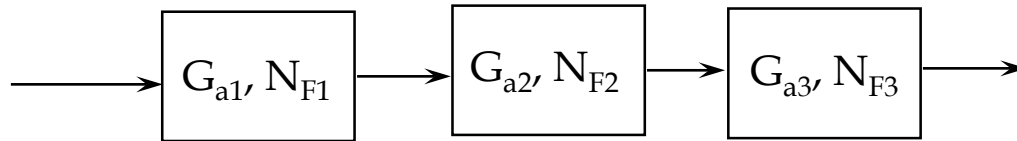

$$(NF)_{TOT} = NF_1 + \frac{NF_2 - 1}{G_{a1}} + \frac{NF_3 - 1}{G_{a1}G_{a2}} + \dots$$


The noise figure is mainly determined by the first stage

NOTE: In general the value of Γ_s that determines the minimum value of NF is different by the one that maximizes G_T ; the choice of Γ_s for the first stage is then the result of a compromise between the *noise figure* and gain

Design of a low noise amplifier

The choice of Γ_s is a compromise between G_T and NF.

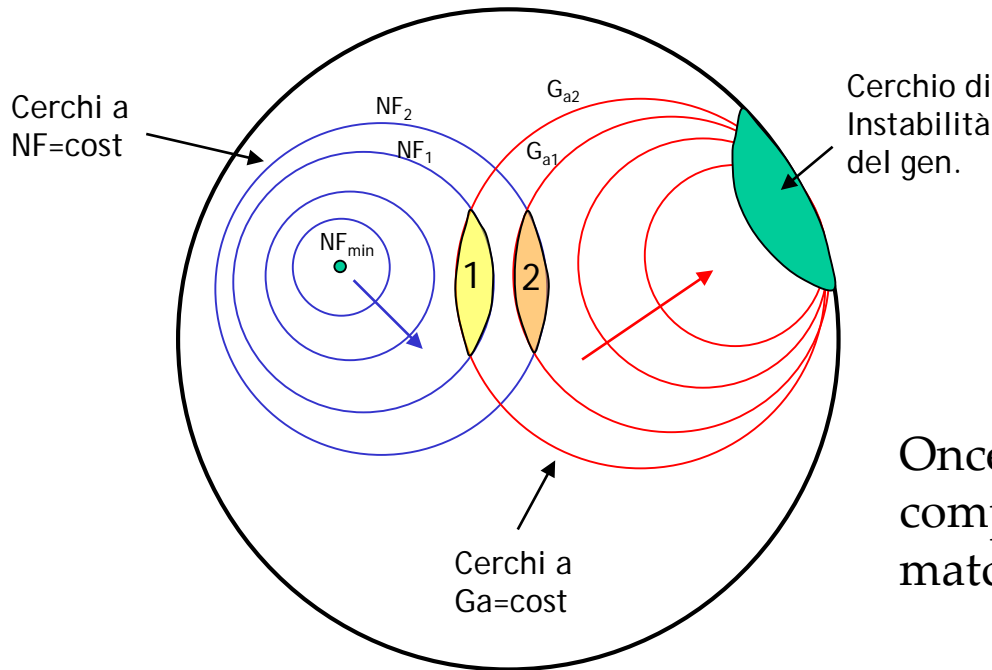Some circles with $NF=\text{cost}$ and $G_a=\text{cost}$ are first plotted on the Smith chart (Γ_s). The value of Γ_s is selected within the common area of two circles. Considering that NF increases with the radius while G_a decreases with it, we have (with reference to the zones 1 and 2):



In zone 1: $NF \leq NF_1$ and $G_a \geq G_{a2}$
NF is privileged

In zone 2: $NF \leq NF_2$ and $G_a \geq G_{a1}$
 G_a is privileged

Once assigned $\Gamma_{s,opt}$, $\Gamma_{L,opt}$ is computed by imposing the matching at output (then $G_T = G_a$)

Example of design

Amplifier Requirements

Frequency Band: 6.2 – 6.8 GHz

Minimum Transducer Gain: 10.5 dB

Maximum Noise Figure: 1.5 dB

Substrate: Duroid

$\epsilon_r = 2.54$

H= 0.508 mm

t = 35 μ


Active Device

MGF1923 Mitsubishi (GaAs Mesfet)


MSG (6.8 GHz): 15.16 dB (with NF=3.1 dB)

Minimum NF (6.8 GHz): 1.13 dB (with Gt=8.06 dB)

Topology:

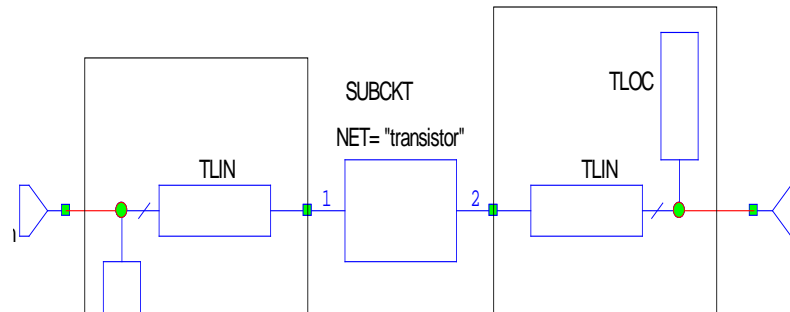


Biasing network of the active device

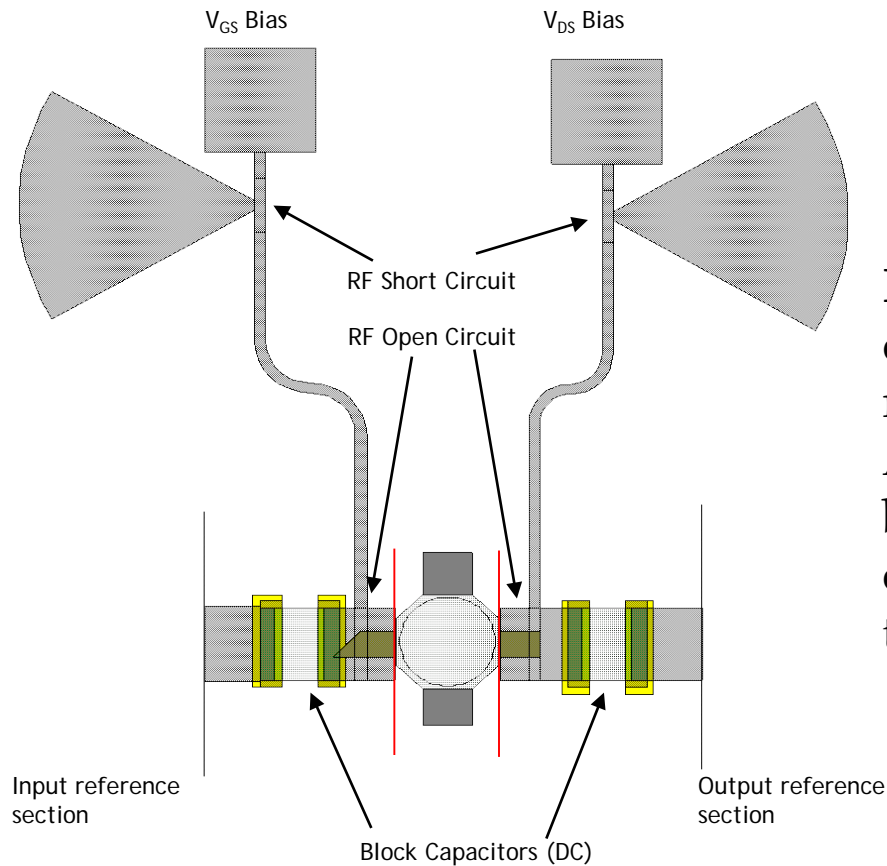

NOTE: The S parameters delivered by the manufacturer refers to the red sections. After the biasing network has been assigned, the S parameters changes to the ones referred to the black sections

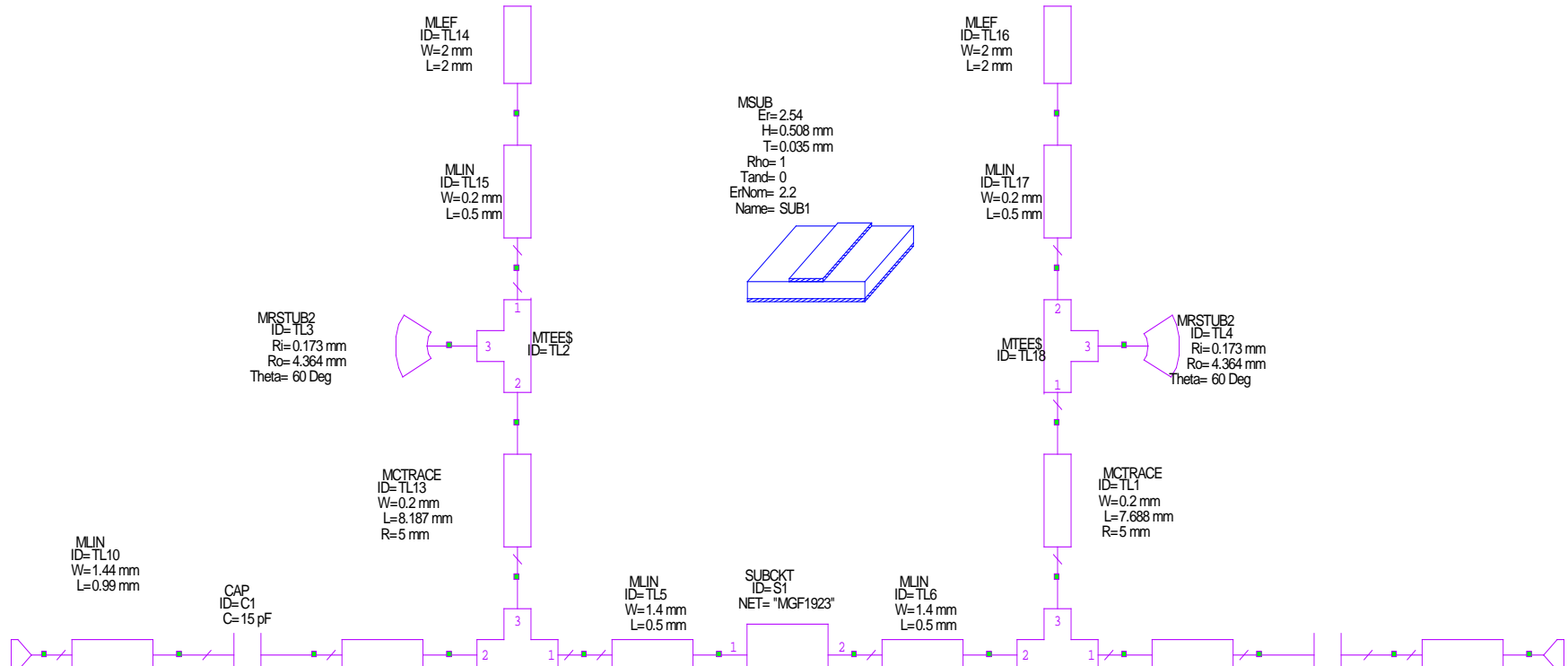Evaluation of the S parameters of the biased active device



S parameters for the design

Frequency: 6.8 GHz

S11 (Mag, Phase deg) 0.80304 , -164.13

Potentially INSTABLE

S12 (Mag, Phase deg) 0.07083 , -32.616

Maximum Stable Gain (dB): 15.155

S21 (dB, Phase deg) 7.3143 , 23.642

Stability Coefficient K: 0.66826


S22 (Mag, Phase deg) 0.58075 , -130.99

Minimum Noise Figure (dB): 1.1651


Optimum Gamma Source (Mag, Phase deg): 0.57413 , 109.84

Normalized Noise Resistance: 0.20827

Γ_S selected for maximum gain

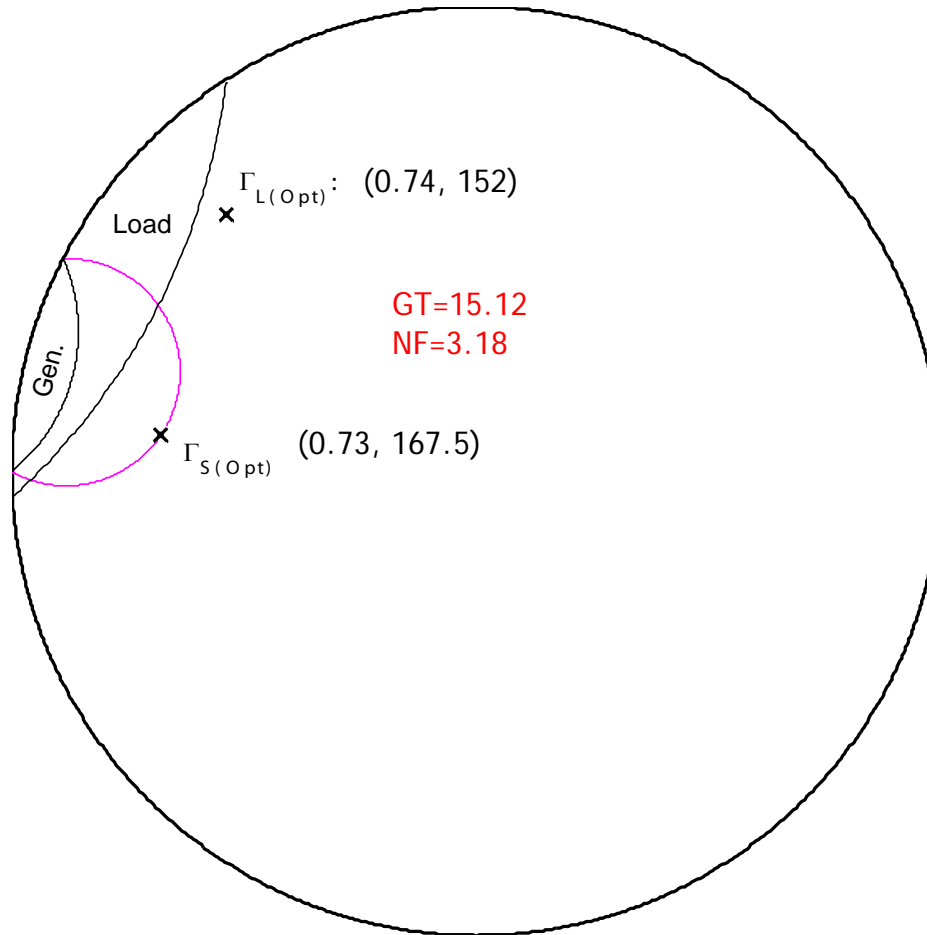

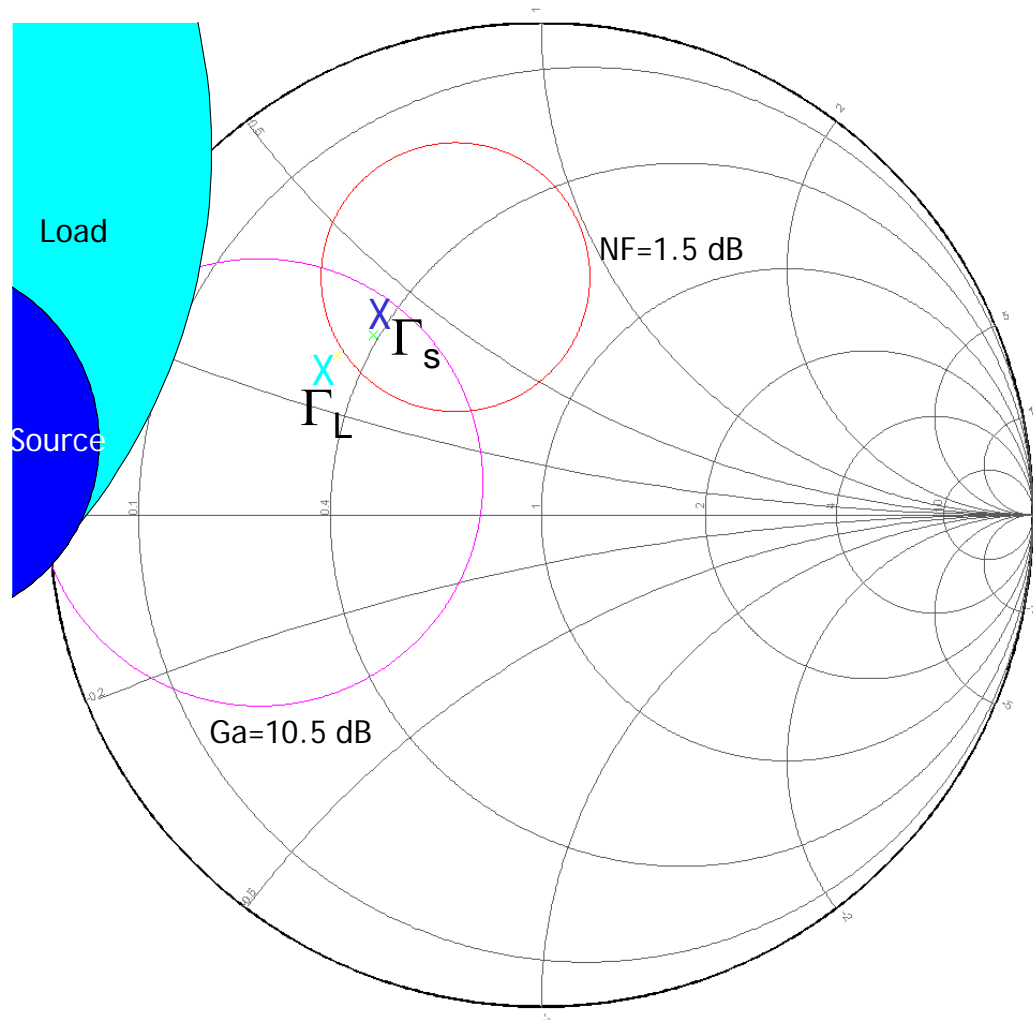Selection of Γ_S as a compromise between G_T and NF





$$G_T = 10.7 \text{ dB}$$

$$NF = 1.36 \text{ dB}$$



$$\Gamma_L = 0.524 \angle 142.1^\circ$$

$$\Gamma_S = 0.5 \angle 133^\circ$$


Input matching network

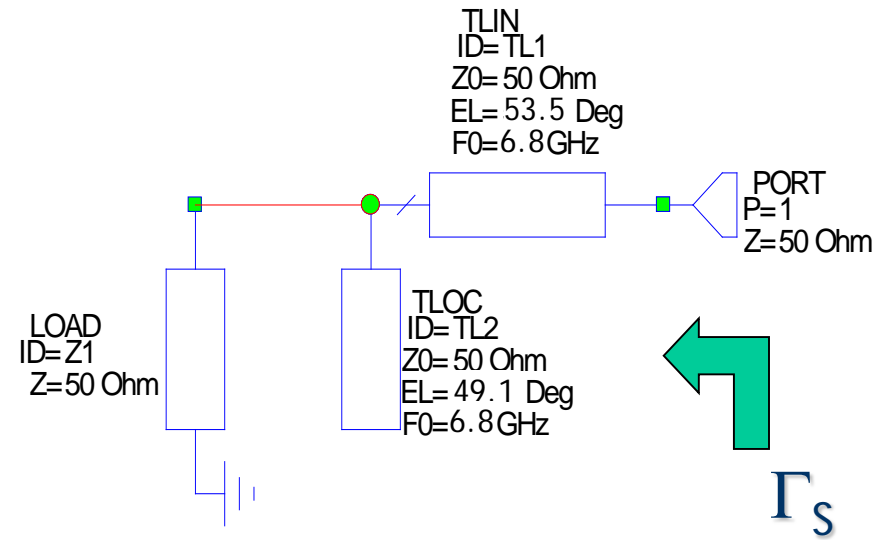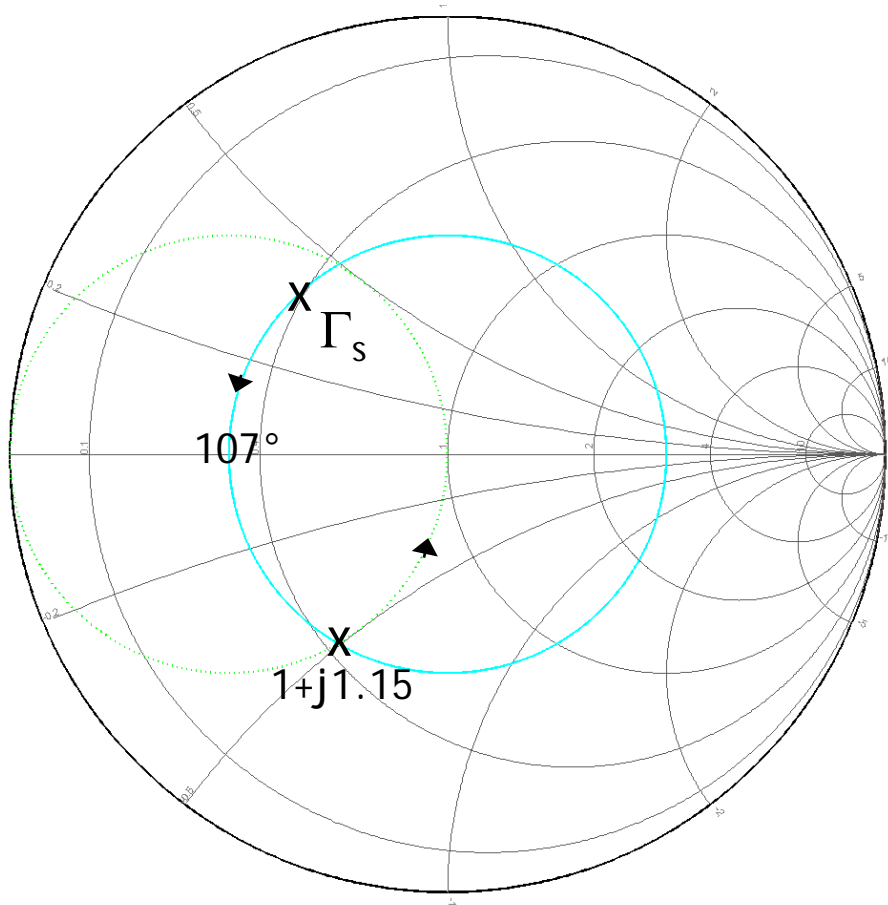


Output matching network

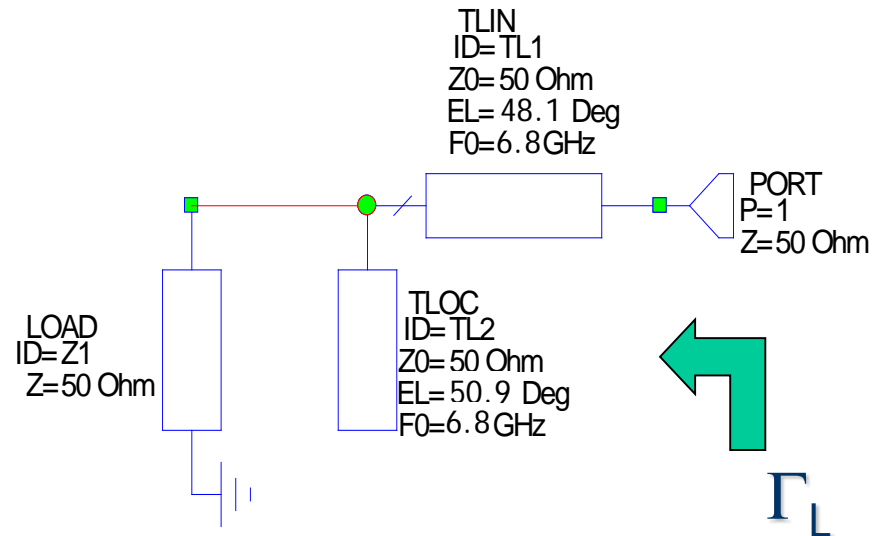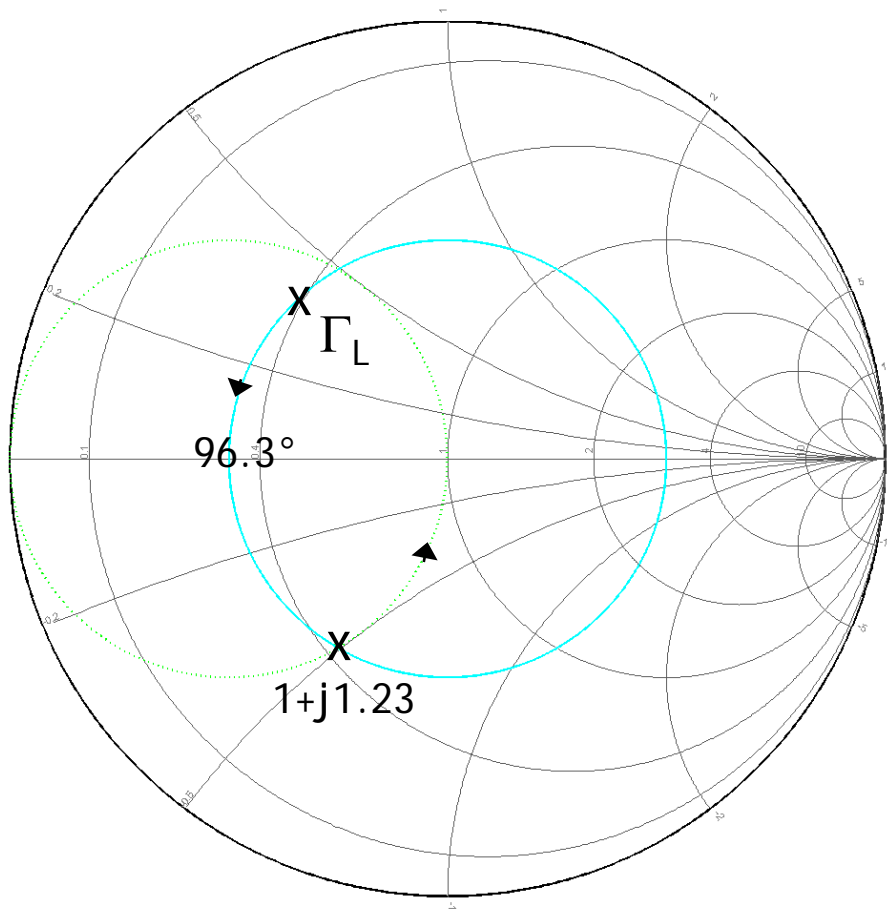

Initial design response (ideal lines)

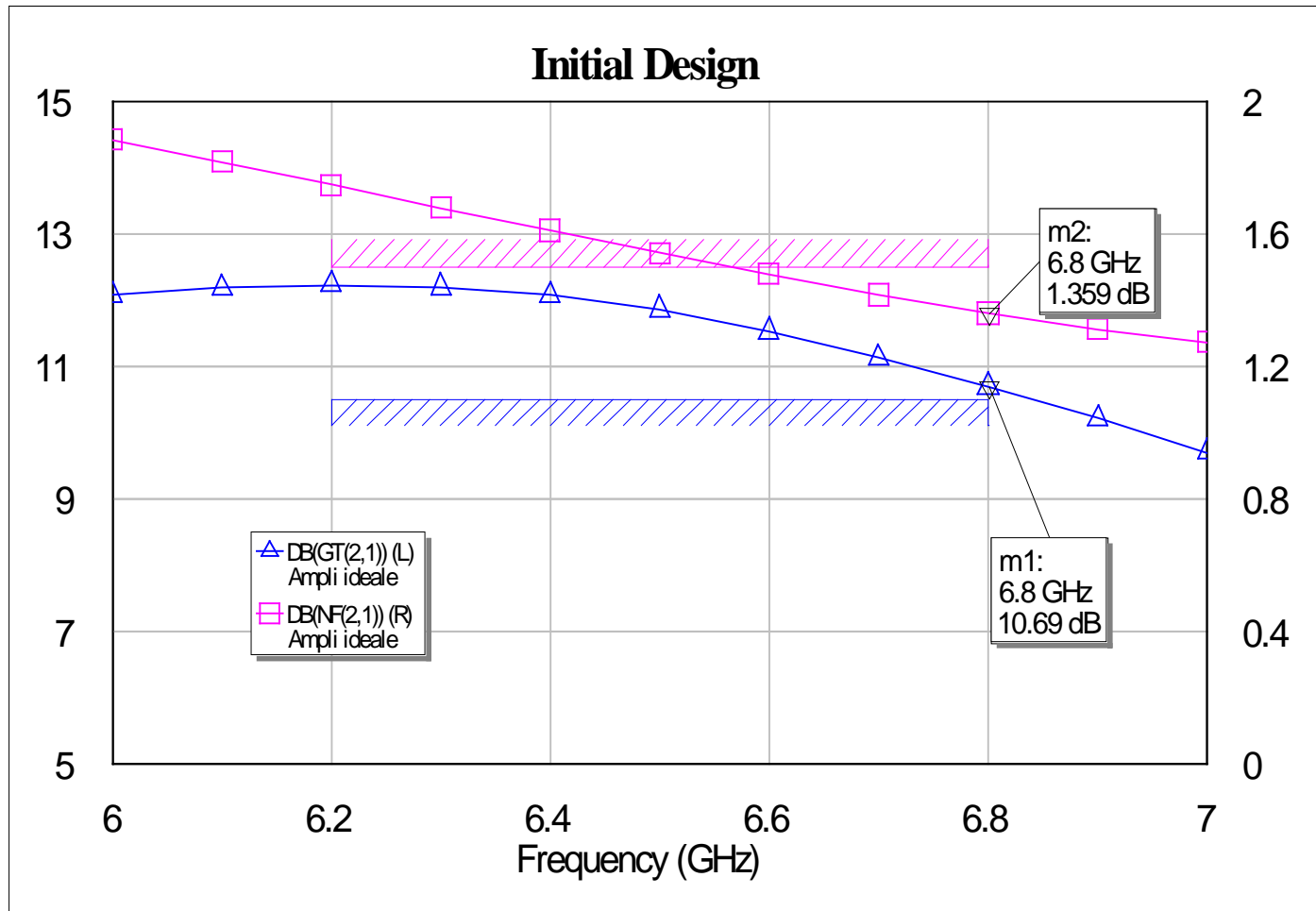


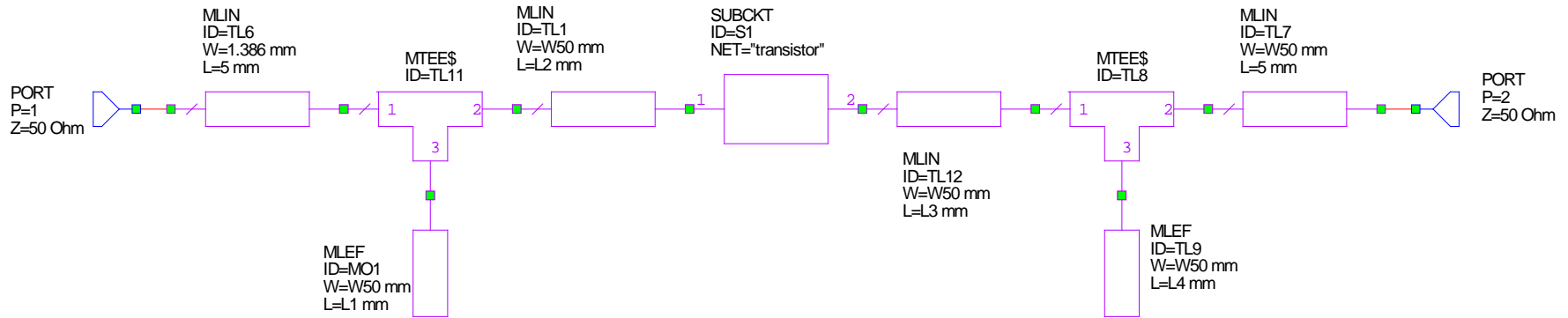Microstrip implementation (including discontinuities)




W50=1.38645
L1=4.13952
L2=4.51048
L3=4.05522
L4=4.29128


Amplifier Layout (initial)

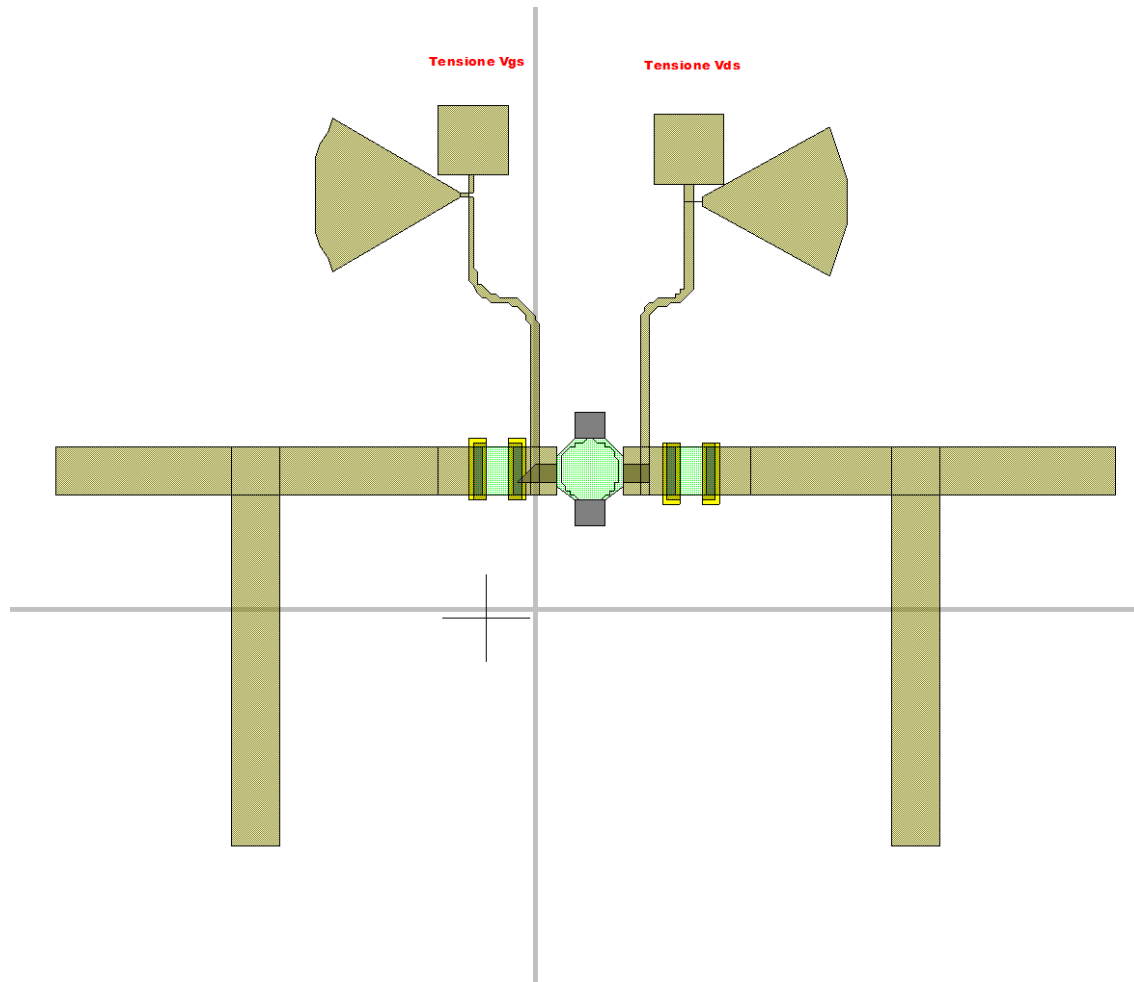


Amplifier Response (initial/optimized)

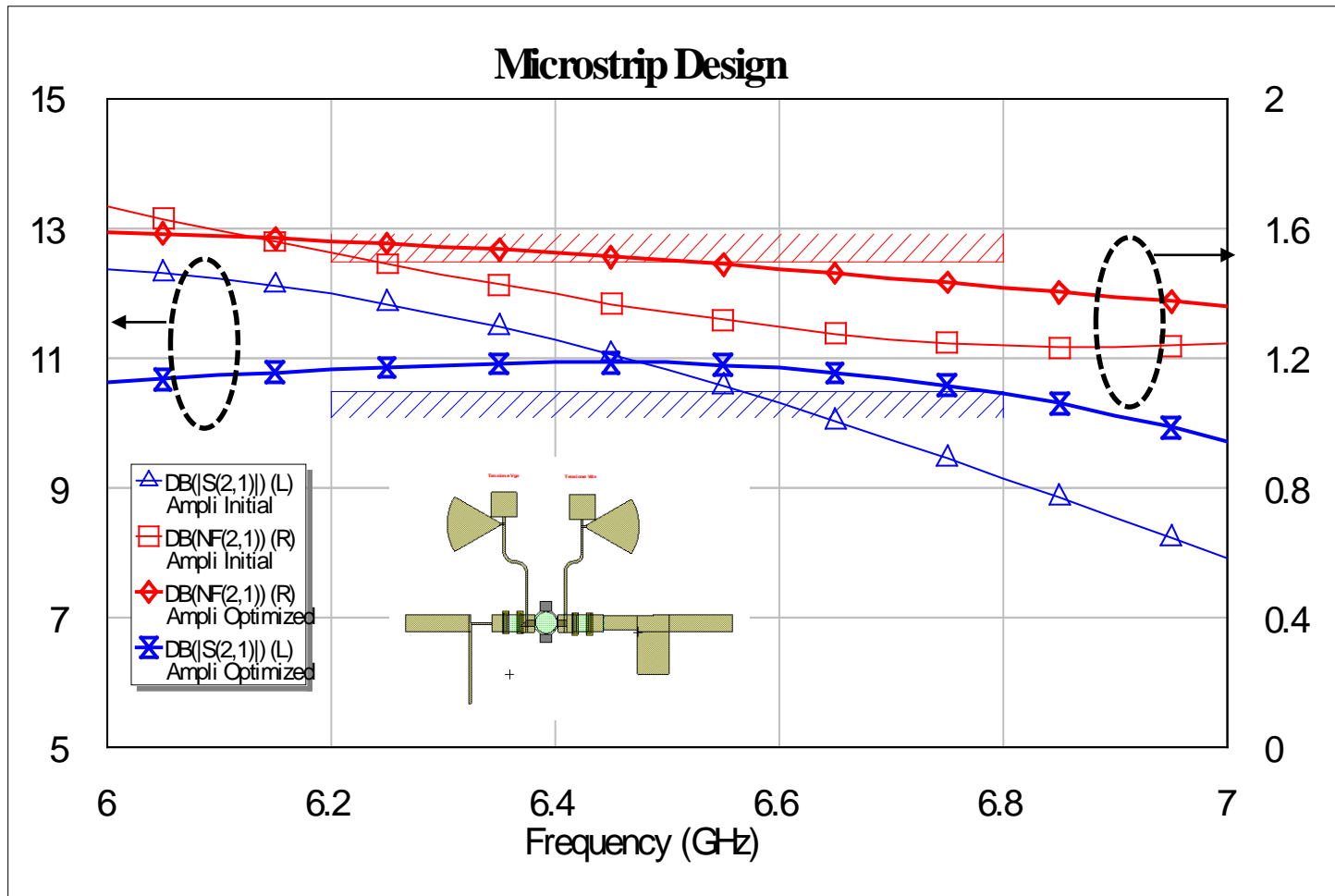


Alternative Scheme (optimized)

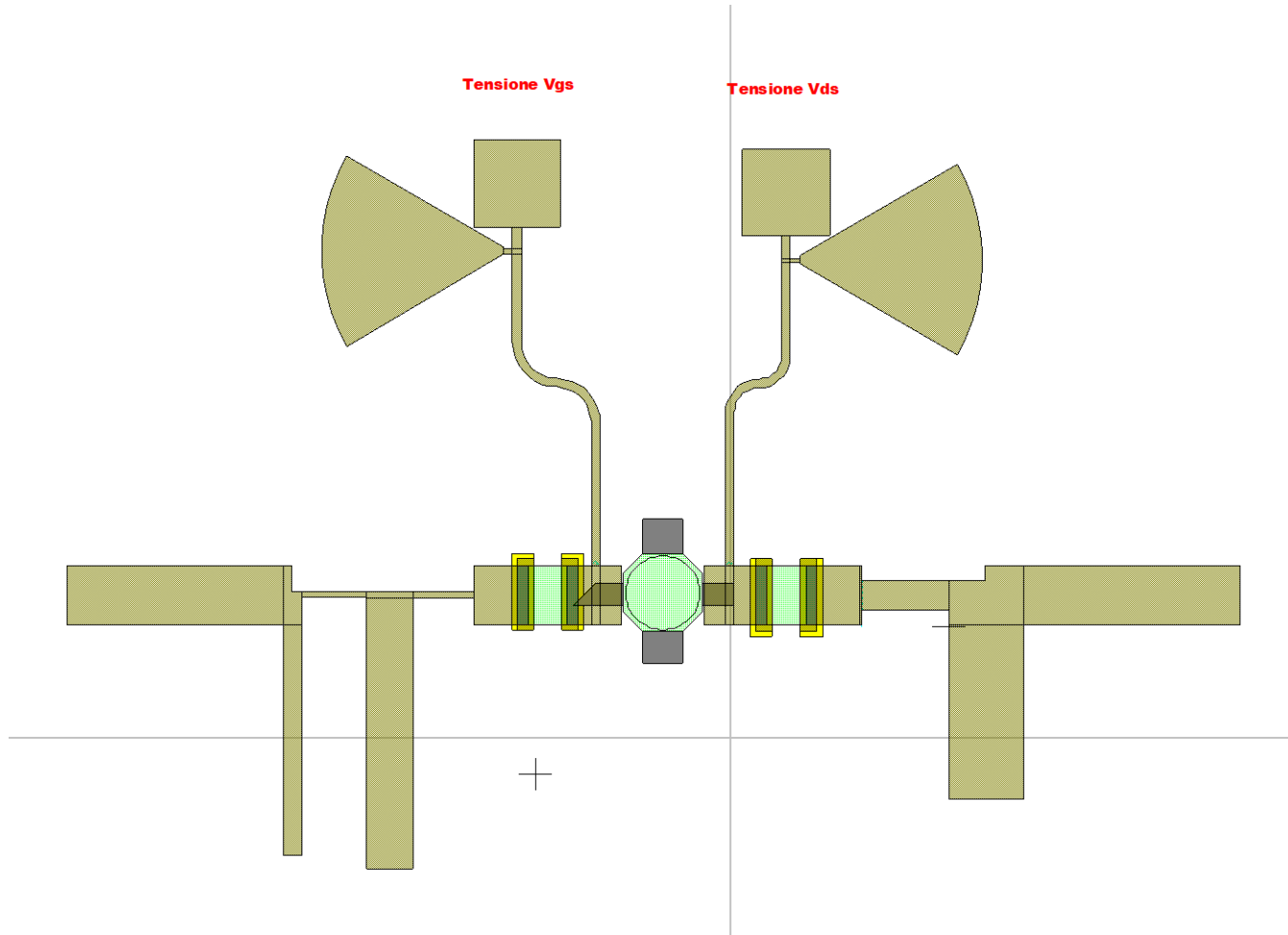

Final response

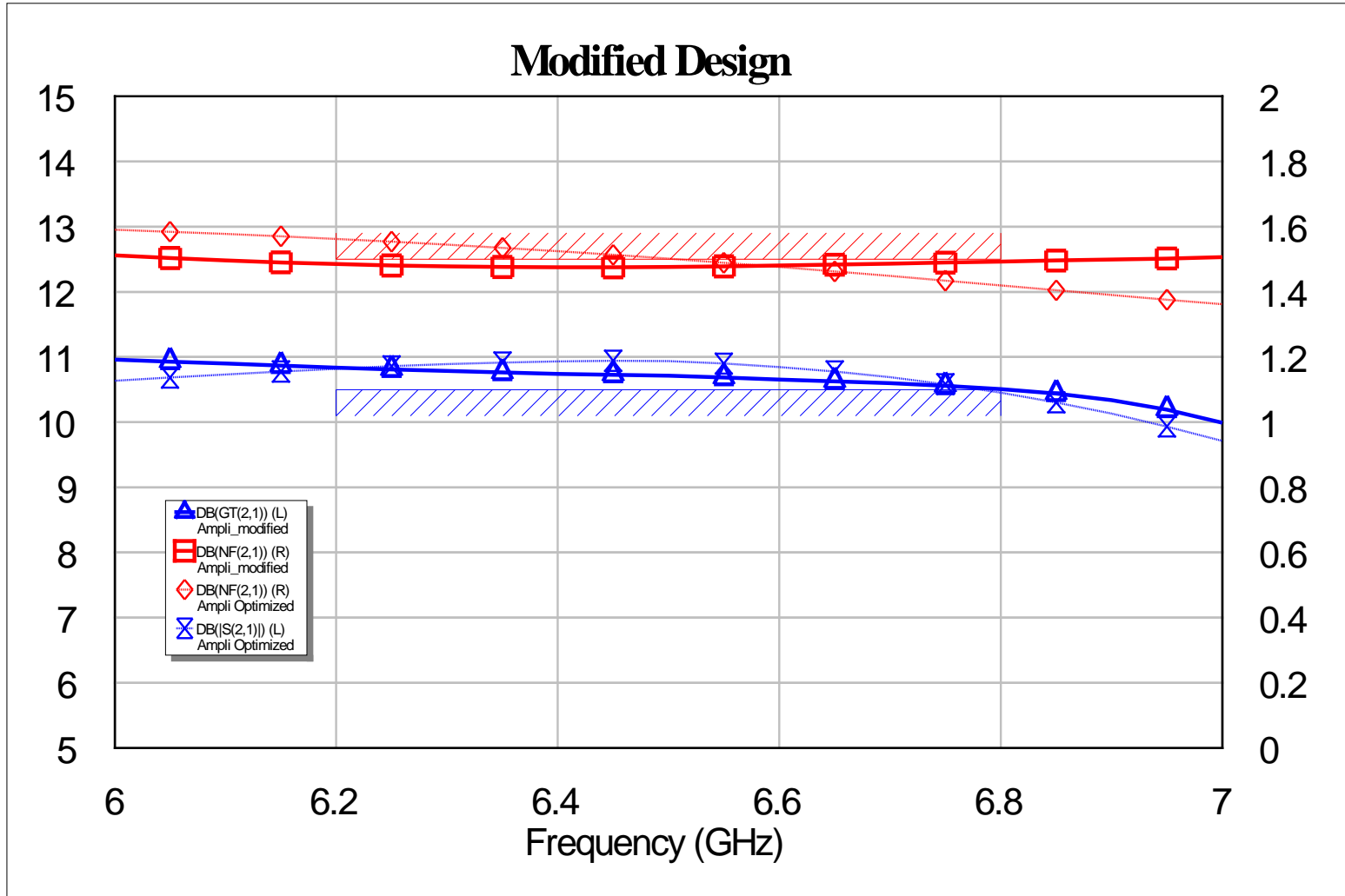

Scheme of a power microwave amplifier

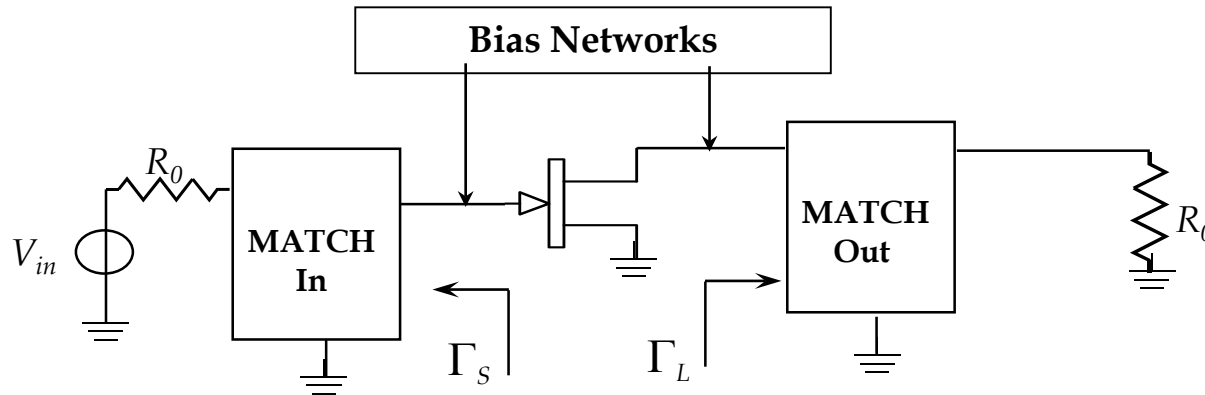

The concept is identical to the ones seen before. In this case however the main design goals concern the output power, linearity and efficiency. The values of Γ_S and Γ_L should determine the best compromise among the main goals (but taking also into account the gain and the matching conditions).

Instability issues (also potential) have to be absolutely avoided (commercial devices are generally pre-matched internally for unconditional stability).


The active device must be characterized for large signal operation

Device characterization

- ❑ The device model should allow the evaluation of absolute quantities (Pout, Intermodulation, Efficiency), to be used in non-linear Harmonic Balance simulators.
 - ❑ Unfortunately non-linear circuit models of commercial devices are rarely available
 - ❑ As a much less accurate alternative, behavioral models based on the information delivered by the manufacturers can be employed also in circuit simulations
 - ❑ Such models are memoryless and usually adopt a polynomial model together with the saturated Pout. They are defined by $P_{1\text{dB}}$ and IP_3 , which however are not related by the simple relation valid for 3th order nonlinearity.
-



Selection of the active device

- In this phase the behavioral models are most suited
- If the requirements concern modulated (RF) signals, it could be convenient to use system simulators
- Some system simulators (e.g. VSS), other than models of PA based on polynomial characterization, also include models based on concurrent circuit simulation (Harmonic Balance). However, also these models adopt a polynomial characterization derived from the circuit response

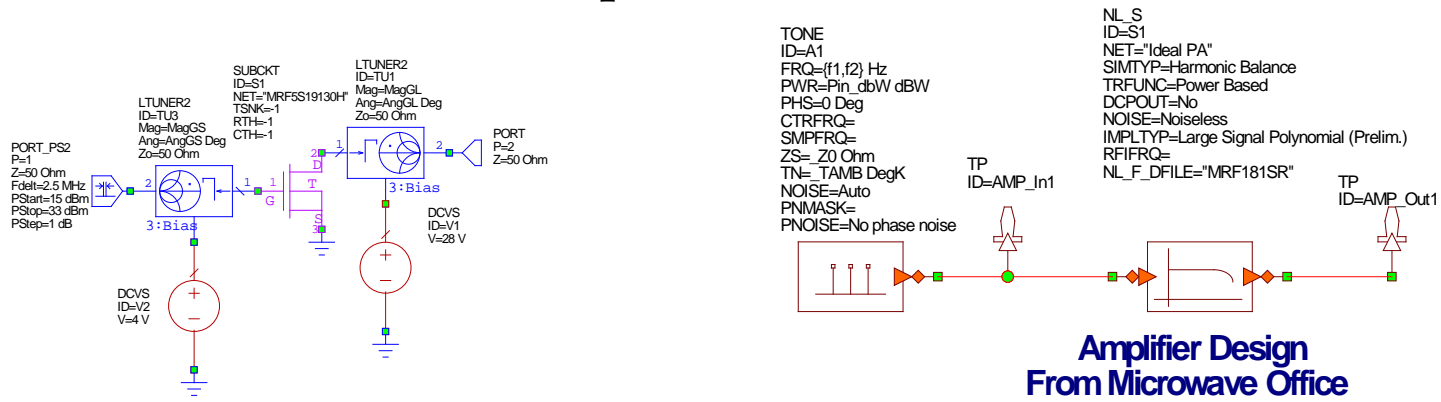



Optimum Γ_S and Γ_L

- These parameters are generally specified by the manufacturer in the typical operating conditions (exciting signal and output average power)
- If a non-linear model of the device is available, the optimum values can be searched through non-linear simulations (starting with those suggested in the device data sheet)
- In most cases, the topology of the matching networks must be those provided by the manufacturer (especially when the optimum impedances are very low)

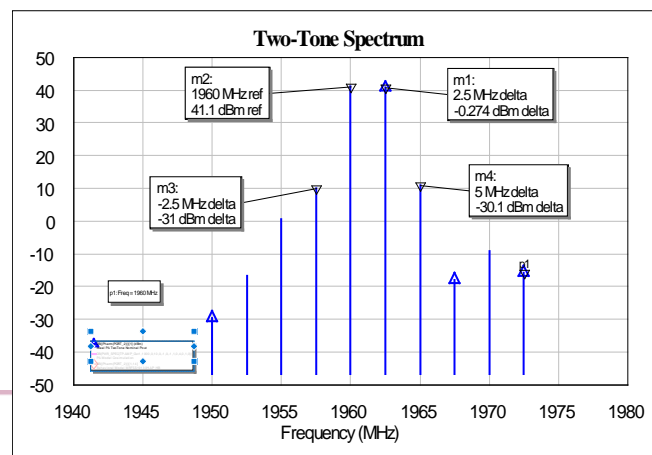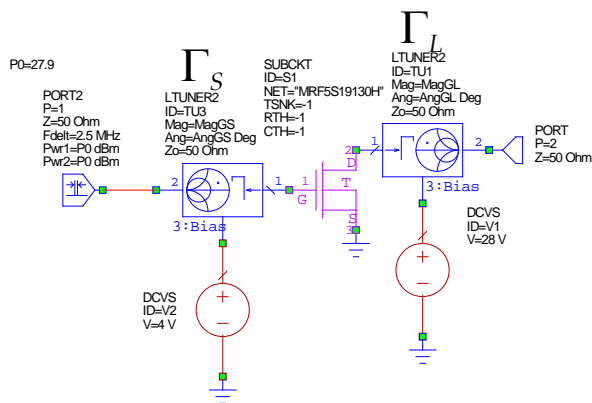

Matching Networks Layout

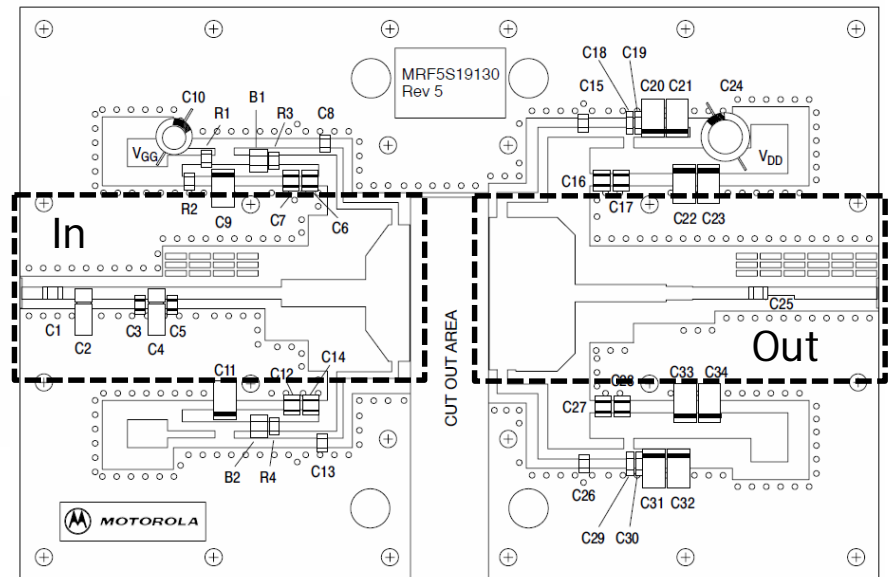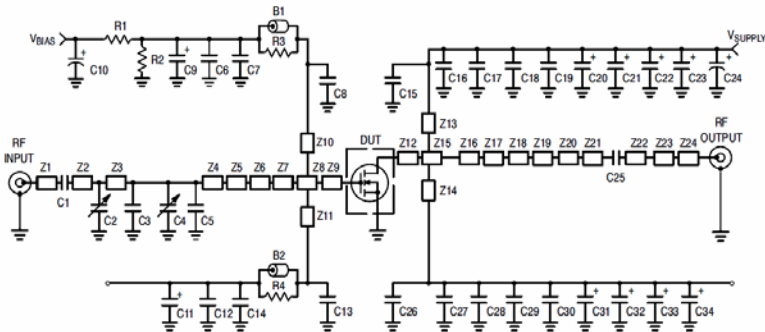- ❑ The most suited topology is generally suggested by the manufacturer (also the biasing circuits are specified).
- ❑ If a non-linear model is available, a fine tuning of the network dimensions can be carried out



Design of a “line -up” for N-CDMA


General Specifications

- Center Frequency: 1960 MHz, Band : 1930-1990 MHz
- Channel band: 1.2288 MHz (IS-95) Channels spacing: 2.5 MHz
- Output power: ≥ 100 W PEP (2-tone)
- Gain: ≥ 27 dB (max input power 200 mW PEP (23 dBm))
- Linearity: C/I ≥ 30 dB (2-tone)


PAE $> 25\%$ with 2-tone at rated PEP

Possible topologies

- Due cascaded stages

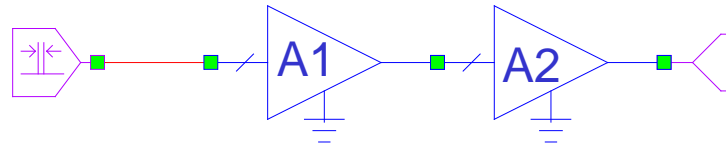

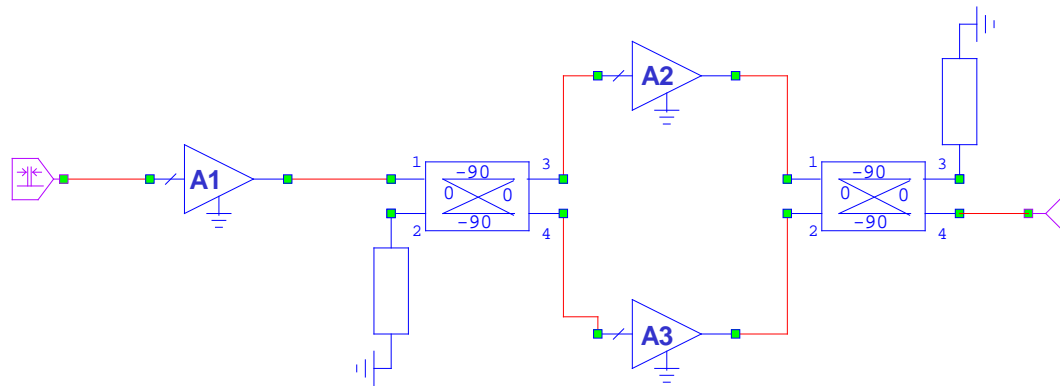- Single stage followed by a balanced pair



Devices choice

Manufacturer: Freescale

Final stage

MRF5S19130 (P1dB=125W, Vdd=28V, Gt=13 dB, η =33%) → Topology 1

MRF7S19100 (P1dB=100W, Vdd=28V, Gt=17.5 dB, η =30%) → Topology 1

MRF6S19060 (P1dB=60W, Vdd=28V, Gt=16 dB, η =35%, IM3=-35 dBc) → Topology 2

MRF19045 (P1dB=45W, Vdd=26V, Gt=14.5 dB, η =36%, IM3=-30 dBc) → Topology 2

Driver

MRF6S20010 (P1dB=20W, Vdd=28V, Gt=16 dB, η =41%, IMD=33 dBc) → Topology 1/2

MRF282 (P1dB=10W, Vdd=26V, Gt=12 dB, η =33%, IMD=31 dBc) → Topology 1/2

2 cascaded stages

Chosen final device: MRF5S19130 ($IP_3=61.5$ dBm, $G_{final}=13$ dB).

Evaluation of IP_3 of the driver (imposing the overall CI3):

$$P_{\omega_1} = PEP - 6 \text{ dB} = 44 \text{ dBm}$$

$$IP_{3,tot} = \frac{CI + 2P_{\omega_1}}{2} = 59 \text{ dBm}$$

Sum in power of distortion

$$IP_{3,tot} = IP_{3,final} - 10 \log \sqrt{\left(1 + 10^{(IP_{3,final} - G_{T,final} - IP_{3,driver})/5}\right)}$$

$$\rightarrow IP_{3,driver} = 46.82 \text{ dBm}$$

$$IP_{3,driver} = IP_{3,final} - G_{T,final} - 5 \log \left(10^{(IP_{3,final} - IP_{3,tot})/5} - 1\right)$$


Sum in voltage of distortion

$$IP_{3,tot} = IP_{3,final} - 10 \log \left(1 + 10^{(IP_{3,final} - G_{T,final} - IP_{3,driver})/10}\right)$$


$$\rightarrow IP_{3,driver} = 49.58 \text{ dBm}$$

$$IP_{3,driver} = IP_{3,final} - G_{T,final} - 10 \log \left(10^{(IP_{3,final} - IP_{3,tot})/10} - 1\right)$$

Verification with behavioral models


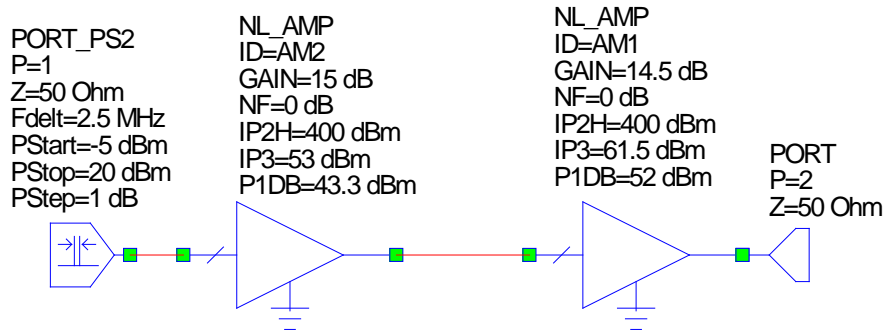


Requested
outP/tone:
44 dBm

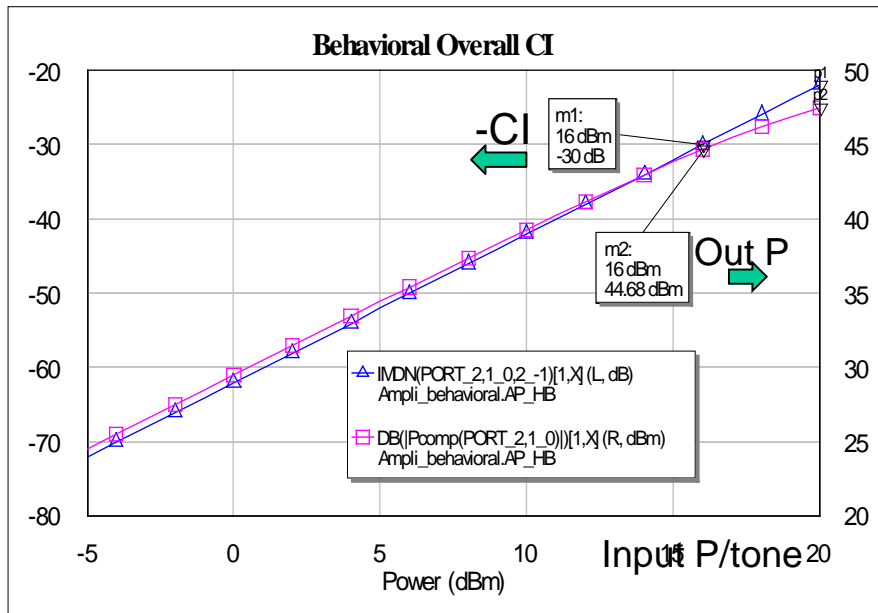

Chosen device for the driver:
MRF6S20010 (IP3=53 dBm)


Spectrum evaluation for CI=30 dBm

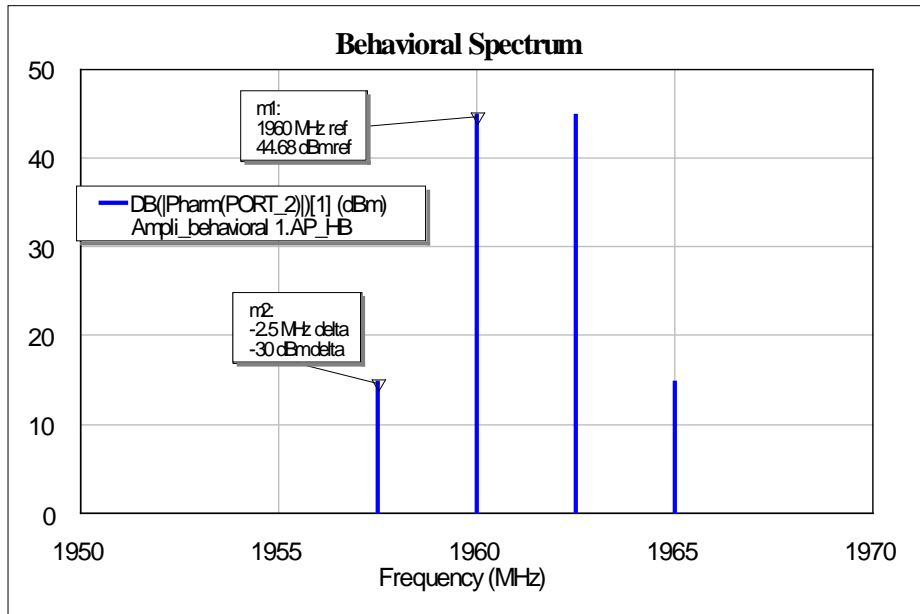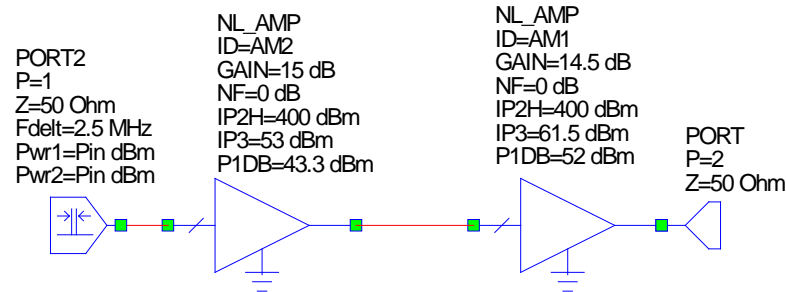

Potenza out: 116.95 W (PEP)
C/I: 30 dBc
Gt=28.68 dB (Pin/tone=16 dBm)

Evaluation of the optimum loads

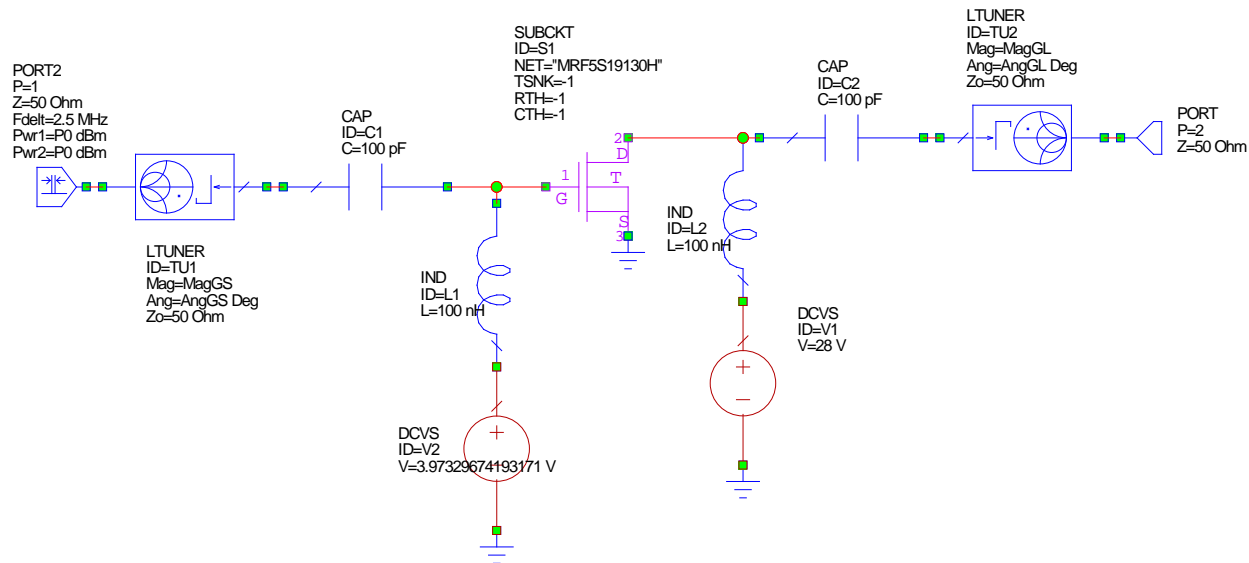- Starting points: optimum impedances reported on datasheets).
- Topology of the networks suggested by the manufacturer
- Biasing point reported on datasheets for optimum performances
- Tuning of the networks for maximize P_{out} e C/I





Result of the simulations (Harmonic balance)

Driver: MRF6S20010

Final: MRF5S19130

Bias: $V_{dd}=28$, $I_d=130$ mA
 $Z_s=9.52+j2.14$ $Z_L=2.75+j3.67$

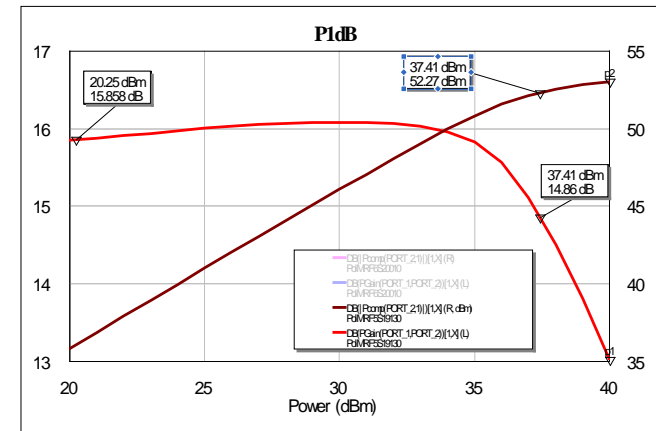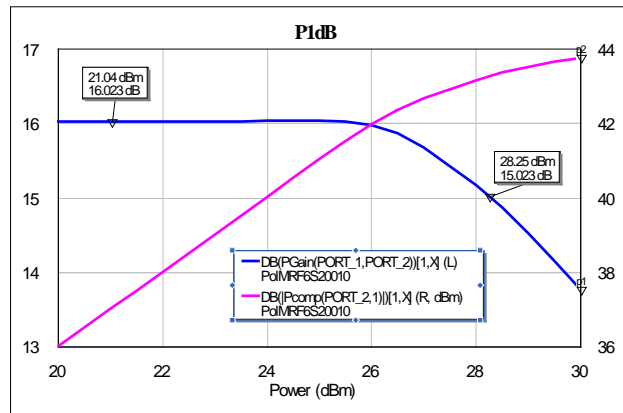
Bias: $V_{dd}=28$, $I_d=1200$ mA
 $Z_s=2.35 - j7.6$ $Z_L=1.28 - j1.5$



P1dB,driver=43.3 dBm
 IP3,driver=50.5 dBm
 CI=34.4 (PEP=39.44 dBm)
 G=17.44 dB


P1dB,final=52.3 dBm
 IP3,final=60.4 dBm
 CI=32. (PEP=50.33 dBm)
 G=12.33 dB

Overall line-up: Spectrum for Pout max

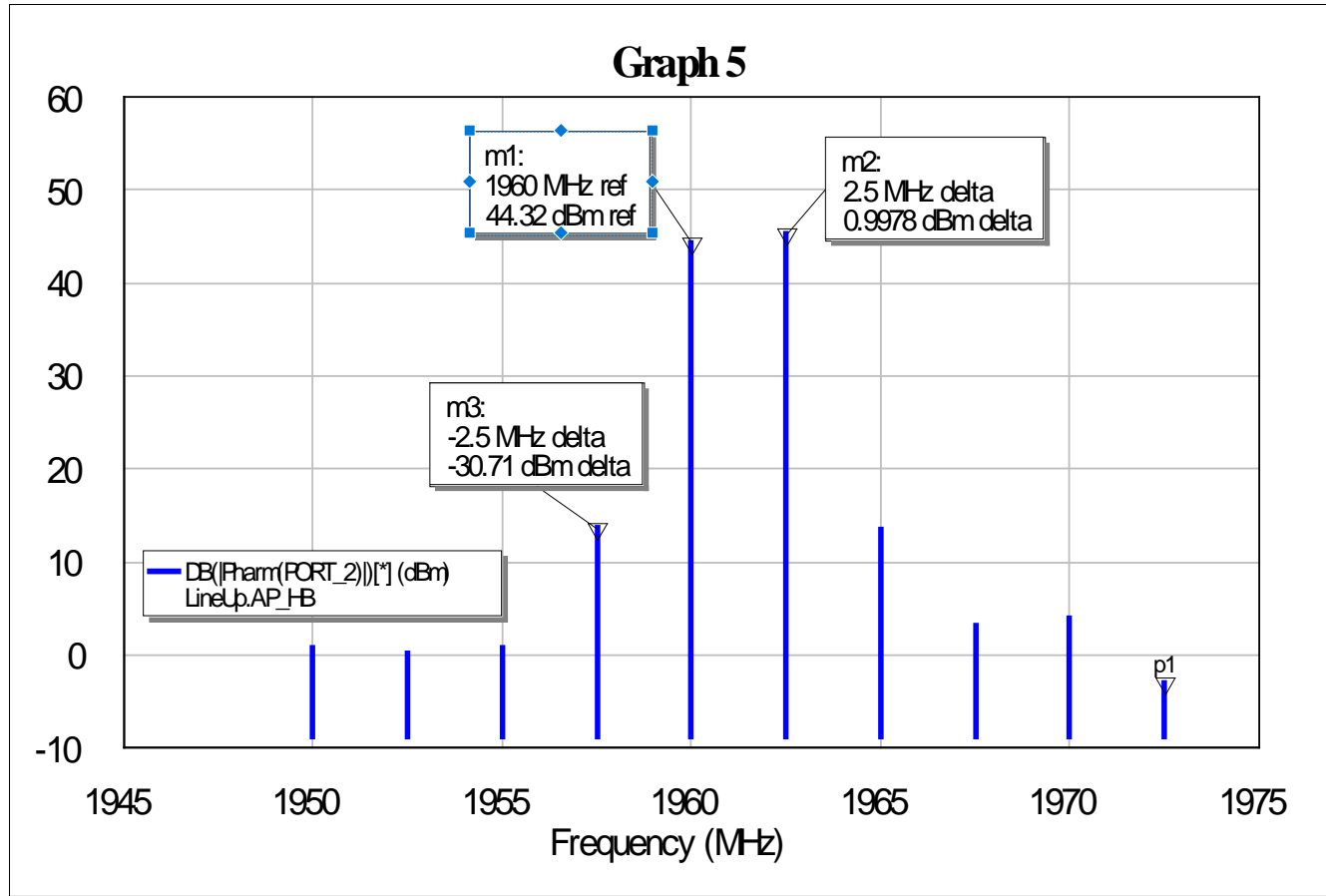


Pout: 107.9 W (PEP), C/I: 30.7 dBc Gt=27.6 dB (Pin=187 mW PEP)

Overall line-up : CI3 e PAE vs Pin

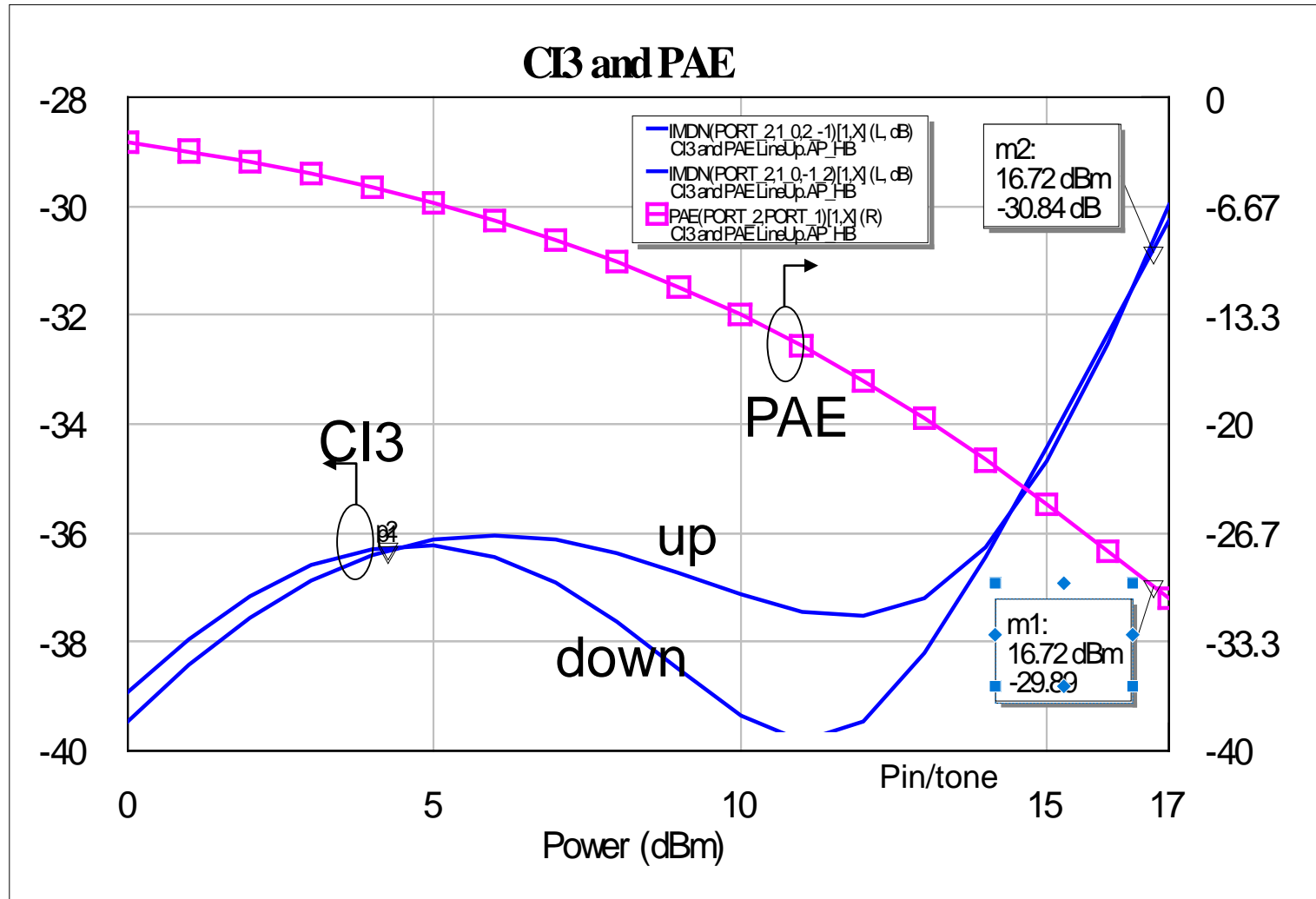


Asymmetry CI3 → Memory effects

Actual (possible) layout of final PA

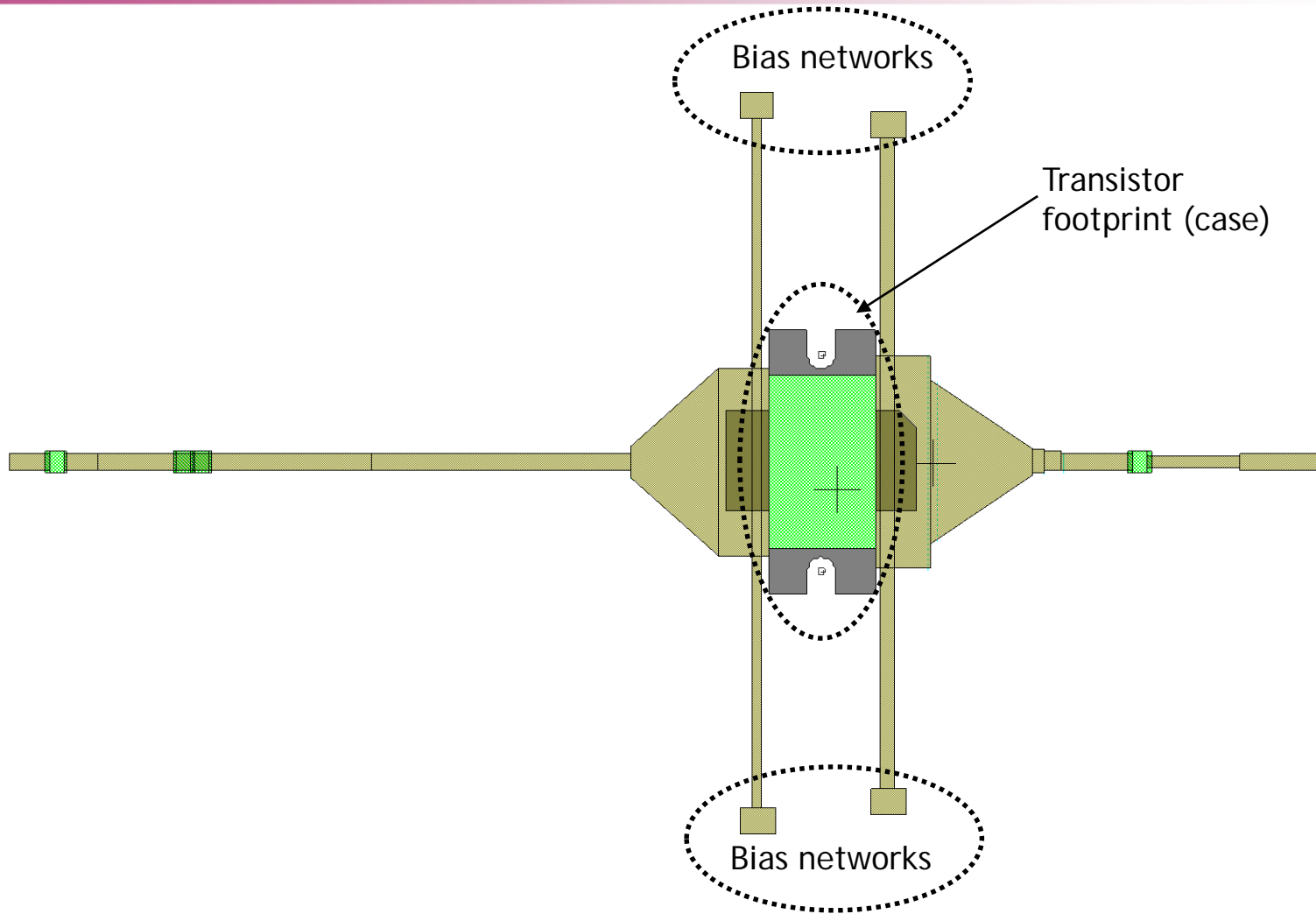


Co-simulation with VSS

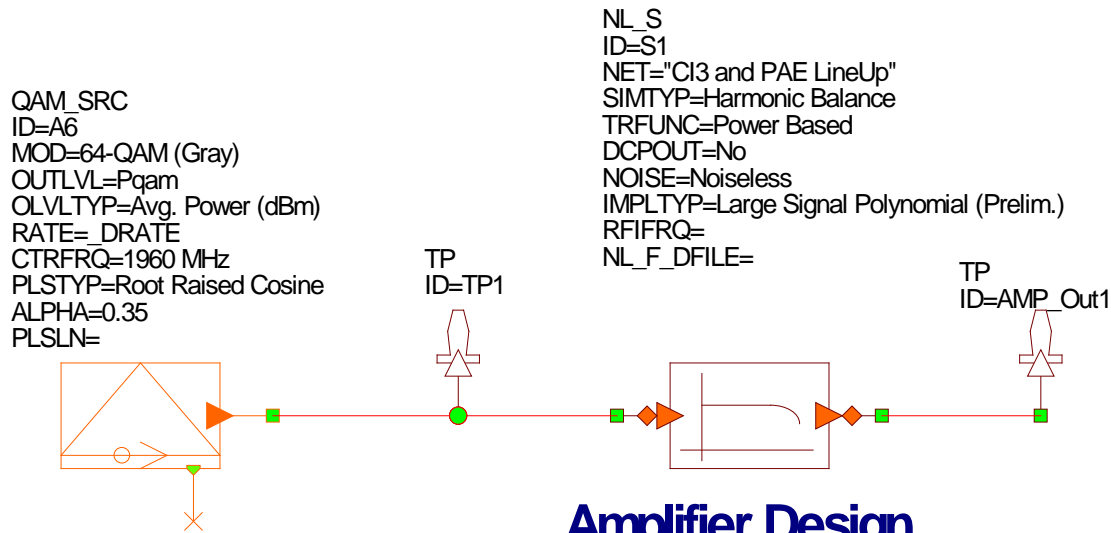- To obtain the estimated response with a RF signal (e.g. 64-QAM) we can use VSS with the block relating to circuit simulation:




**Amplifier Design
From Microwave Office**

Input-output spectra (64-QAM)

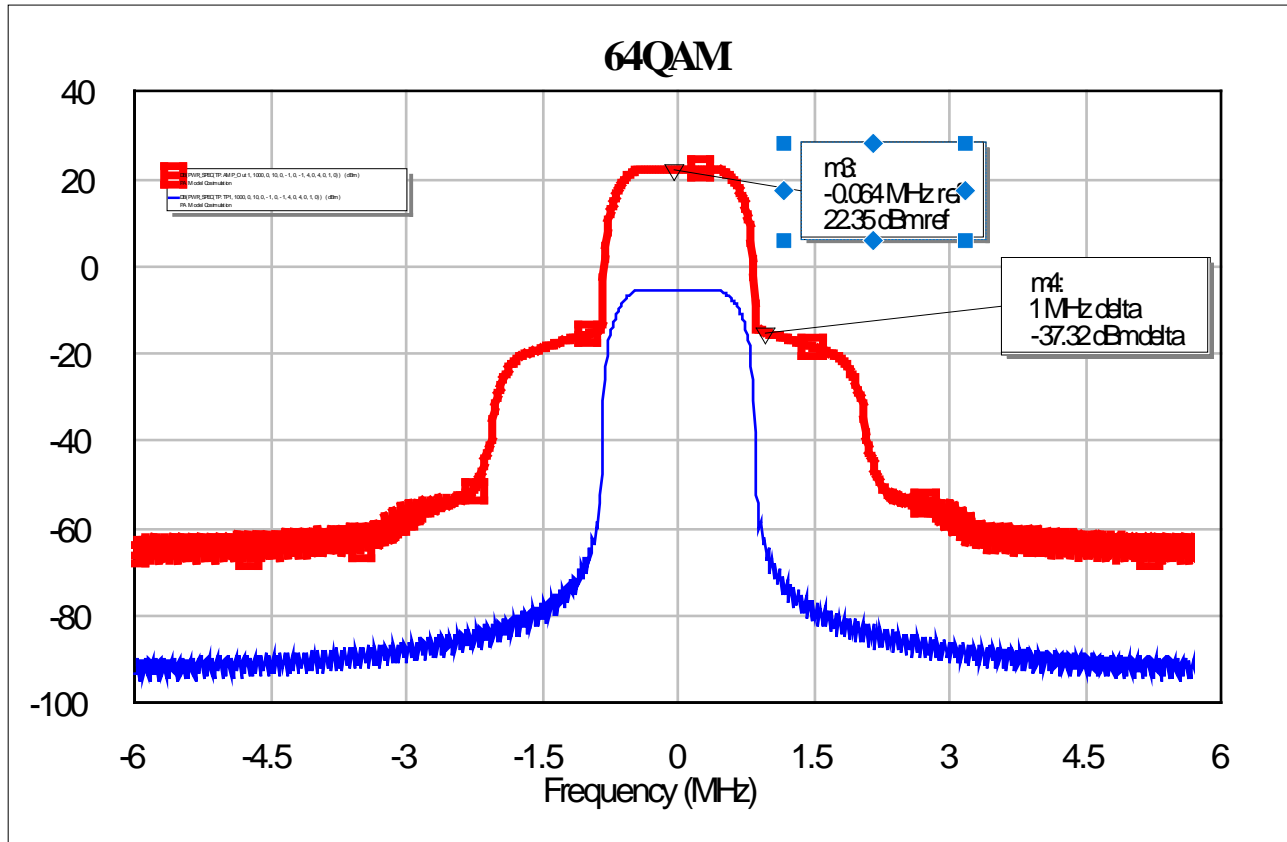


Output power: 40 dBm (average)

Two Modulated carriers (64-QAM)

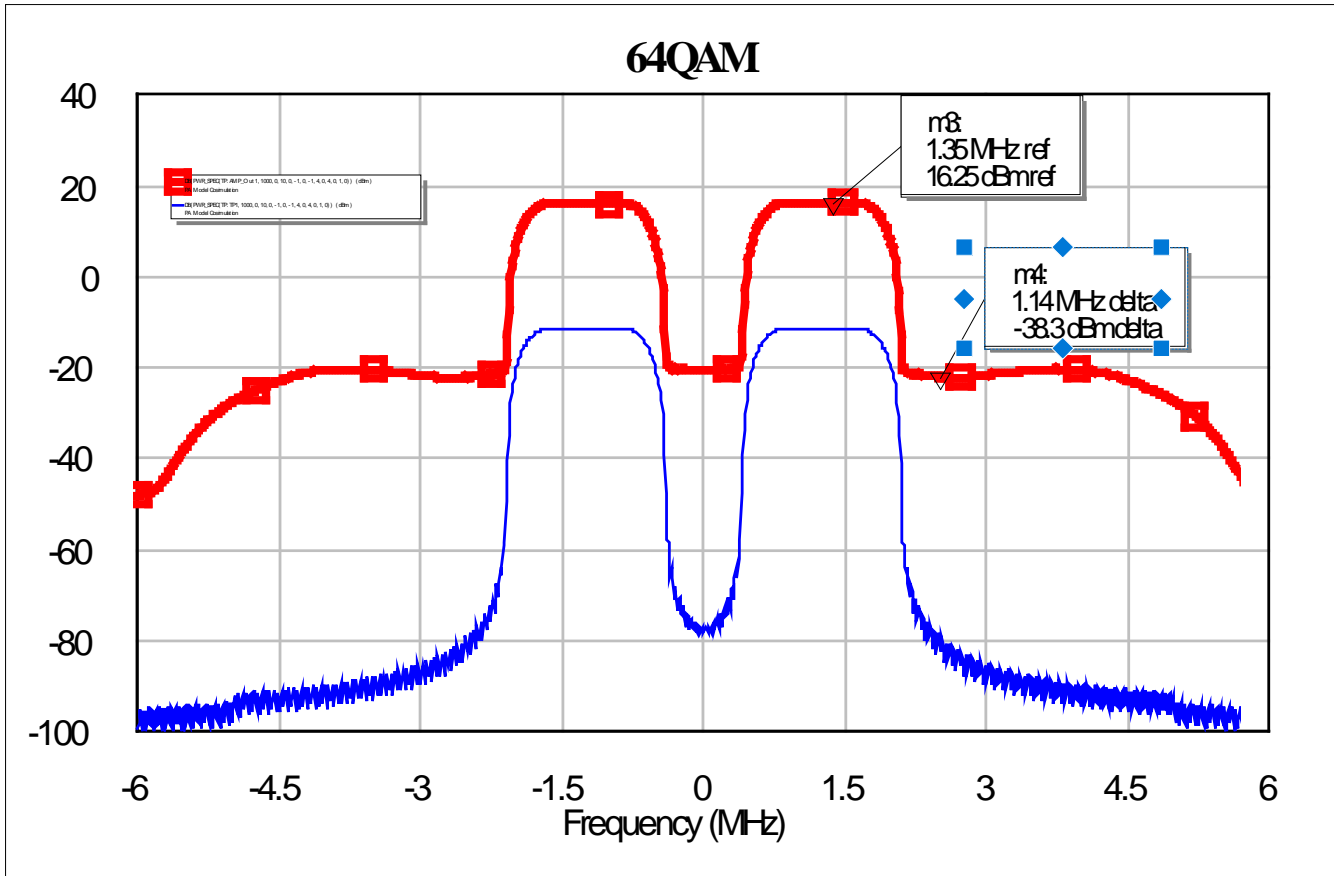

Pout av. : 37 dBm (C/I=38 dB)

Balanced Amplifier

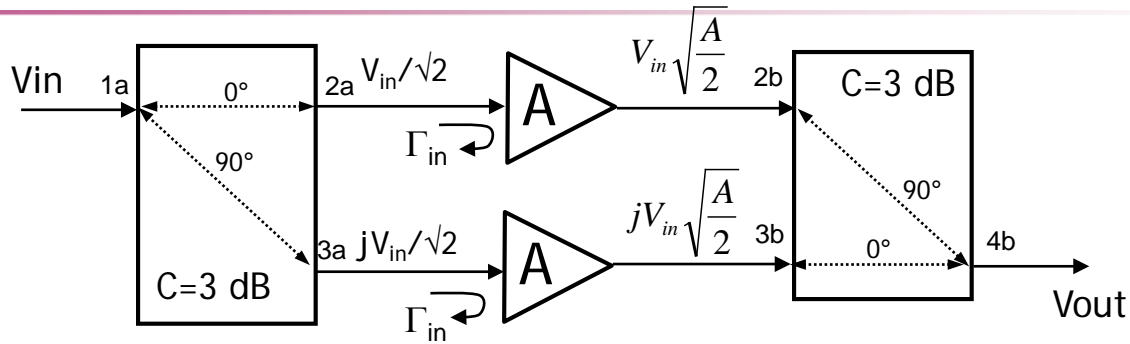

Gain:

$$V_{2b} = \sqrt{A} \cdot V_{in} / \sqrt{2}, \quad V_{3b} = j\sqrt{A} \cdot V_{in} / \sqrt{2}$$

$$V_{out} = V_{4b} = j \frac{V_{2b}}{\sqrt{2}} + \frac{V_{3b}}{\sqrt{2}} = j\sqrt{A} \cdot V_{in} \Rightarrow \frac{P_{out}}{P_{in}} = A$$


Reflection:

$$V_{1a}^+ = V_{in}, \quad V_{2a}^- = \sqrt{A} \cdot V_{in} / \sqrt{2}, \quad V_{2a}^+ = \Gamma_{in} \sqrt{A} \cdot V_{in} / \sqrt{2}, \quad V_{3a}^- = j\sqrt{A} \cdot V_{in} / \sqrt{2},$$

$$V_{3a}^+ = j\Gamma_{in} \sqrt{A} \cdot V_{in} / \sqrt{2}, \quad V_{1a}^- = \frac{1}{\sqrt{2}} (jV_{3a}^+ + V_{2a}^+) = -\Gamma_{in} \sqrt{A} \cdot V_{in} / 2 + \Gamma_{in} \sqrt{A} \cdot V_{in} / 2$$

$$\Gamma_{in} = \frac{V_{1a}^-}{V_{1a}^+} = 0$$

IP3 in balanced amplifiers

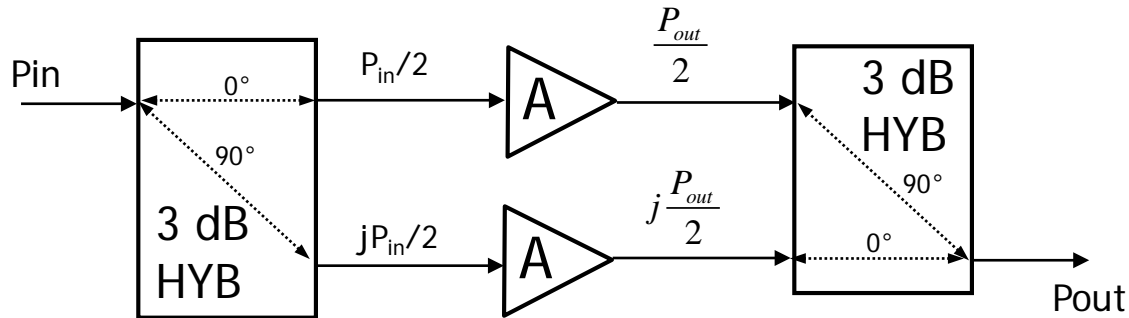



$$P_{\text{int},1} = 3(P_{\text{out}} - 3) - 2IP_3, \quad P_{\text{int},2} = [3(P_{\text{out}} - 3) - 2IP_3]$$

$$P_{\text{int}} = 3(P_{\text{out}} - 3) - 2IP_3 + 3 = 3P_{\text{out}} - 2IP_3 - 6 = 3P_{\text{out}} - 2IP'_3$$

$$IP'_3 = IP_3 + 3$$


Result: the equivalent IP3 of the overall amplifier is doubled with respect to the one of the single amplifiers. This means that for the same overall output power the power of the intermodulation products is 6 dB lower.

Balanced PA with two MRF5S19130

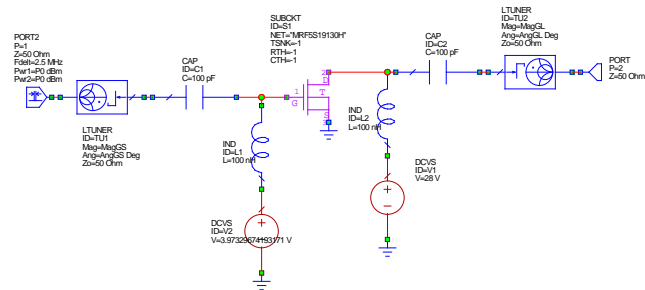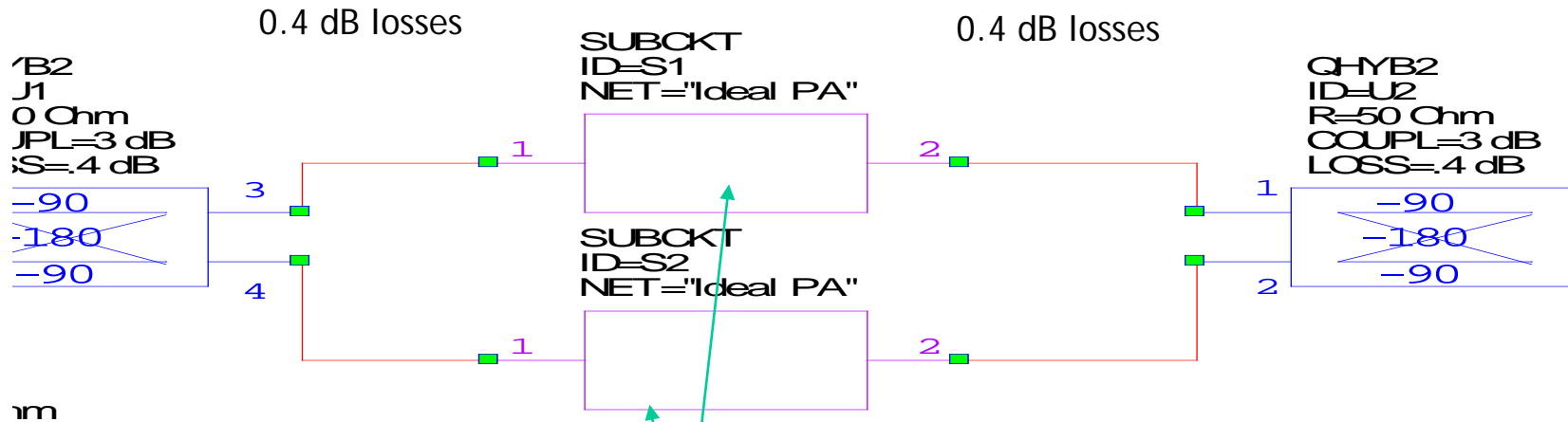


Comparisons with cascade topology

Same output power

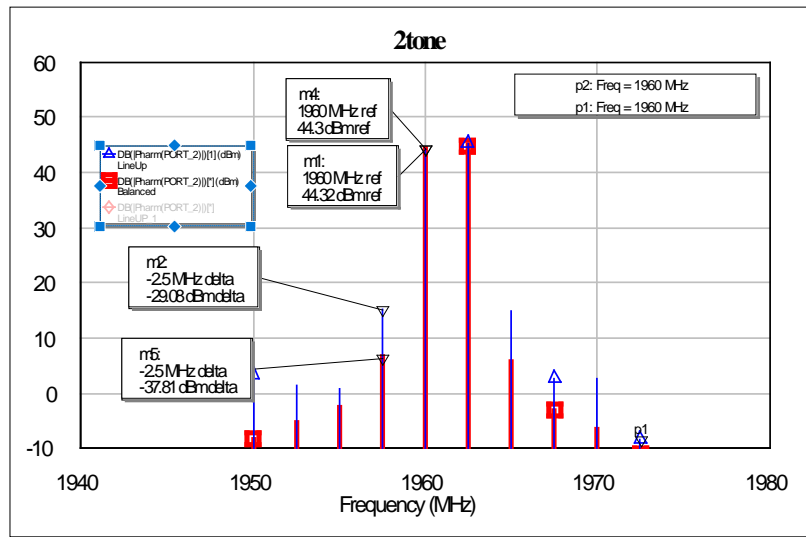

IM3 reduces by 8.8 dB
PAE: from 30% to 18%

Same IM3

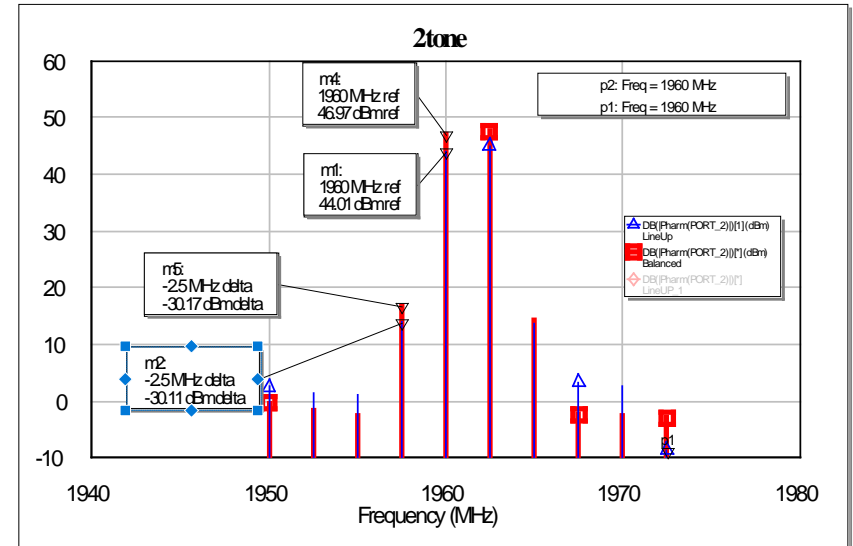

Output power increases
by 3 dB
PAE: from 30% to 27%

Gain reduces by 15 dB