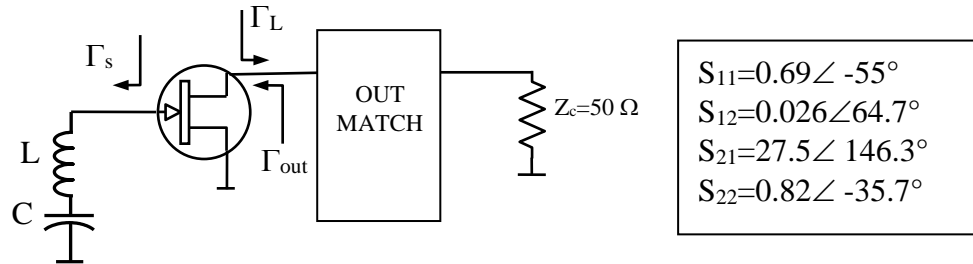


Exercise 010217

The following scheme refers to an oscillator working at $f_{osc}=425$ MHz. The S parameters of the transistor are also reported on the figure.



The resonant circuit resonates at $f_{res}=400$ MHz, where it can be replaced with a short circuit.

- 1) Imposing $|\Gamma_{out}|=1.3$ compute the values of Γ_s and Γ_L determining the start of oscillation
- 2) Verify that for $Z_s=0$ (short circuit) the start of oscillation is not possible. This happens at the resonance frequency f_{res} of the resonator.
- 3) Evaluate the values of L and C determining the requested value of Γ_s at $f_{osc}=425$ MHz and the resonance at $f_{res}=400$ MHz (Hint: the reactance of the series resonator is given by

$$X_s = \omega L - 1/\omega C \text{ with } \omega = 2\pi f. \text{ The resonance frequency is given by } f_{res} = \frac{1}{2\pi\sqrt{LC}}$$

- 4) Chose a topology and design the output network

Soluzione

Inserting the scattering parameter into the S.C. we discover the device potentially instable and the suitable for an oscillator.

1) Draw the mapping circle for $|\Gamma_{out}|=1.3$ and select one of the intersection with the unit circle: $\Gamma_s = 1 \angle 132.31^\circ$. The corresponding reactance results $X_s = 0.442 \cdot 50 = 22.1 \Omega$. Evaluate $\Gamma_{out} = 1.3 \angle -10.4^\circ \rightarrow Z_{out} = -5.21 - j3.53$. The assign $Z_L = 1.7 + j3.52$. Using the S.C. we enter this value as current point and compute $|\Gamma_{in}| = 1.79$, so the oscillation start up is guaranteed.

2) Assigning $\Gamma_s = -1$ (short circuit) as current point we compute $|\Gamma_{out}| = 0.957$ so the oscillation cannot start.


3) We have at $f_{osc} = 425$ MHz: $X_s = \omega_{osc} L - \frac{1}{\omega_{osc} C} = \omega_{osc} L - \frac{\omega_{res}^2 L}{\omega_{osc}} = 22.1$. Replacing $\omega_{osc} = 2\pi \cdot 425$

MHz and $\omega_{res} = 2\pi \cdot 400$ MHz we get $L = 72.48$ nH. Then $C = \frac{1}{\omega_{res}^2 L} = 2.18$ pF.

4) Using a single stub network: $\Phi = 58.75^\circ$, $b = -2.73$.

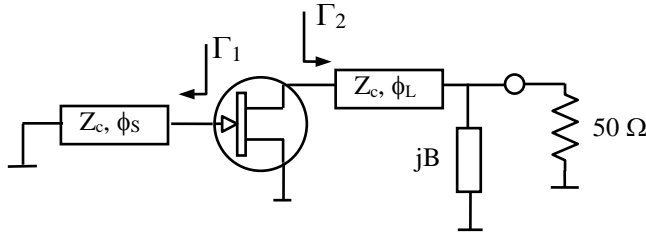Exercise 260916

The following figure represents a microwave oscillator operating at $f_0=10$ GHz. Using the reported scattering parameters of the active device and the components values, evaluate the reflection coefficients Γ_1 and Γ_2 and verify that the start condition of oscillations is satisfied.



$S_{11}=0.521\angle-52.6^\circ$
$S_{12}=0.069\angle42.7^\circ$
$S_{21}=14.44\angle 121.7^\circ$
$S_{22}=0.844\angle -62.3^\circ$
$Z_c=50 \Omega$
$\phi_L=22.27^\circ, \phi_S=78.5^\circ$
$B \cdot Z_c=4.273$

Solution:

With the electronic Smith Chart (and using the circuit parameters) we obtain the values of Γ_1 and Γ_2 :


$$\Gamma_1=1\angle23^\circ, \Gamma_2=0.906\angle160.54^\circ$$

In order the starting oscillations condition is verified we must obtain $|\Gamma_{in}| > 1$ and $|\Gamma_{out}| > 1$. In fact, using the Smith chart, we get:

$$\Gamma_{out}=1.202\angle-168.31^\circ, \Gamma_{in}=1.075\angle-23.16^\circ$$

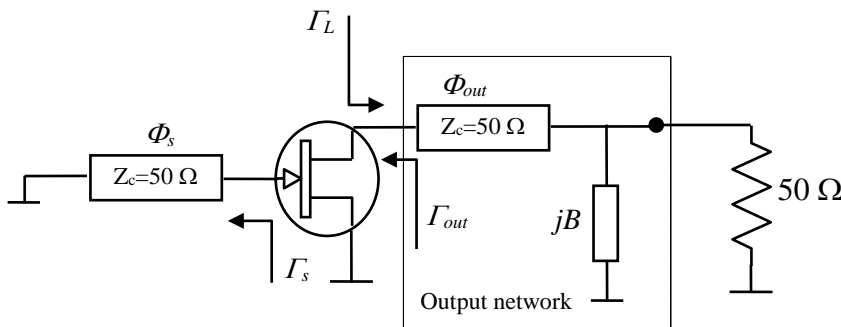Exercise 060716

We want design the oscillator in the following figure, operating at 5 GHz:




The scattering parameters of the transistor are given by:

$$S_{11}=0.844\angle-62.3^\circ, S_{21}=5.273\angle121.7^\circ, S_{12}=0.069\angle42.7^\circ, S_{22}=0.521\angle-52.6^\circ$$

- Select a value for Γ_s and evaluate the electrical length ϕ_s of the first line. (Hint: set $|\Gamma_{out}|=1.2$ and select the Γ_s which determines the minimum value of ϕ_s)
- Design the output network, once the required value of Γ_L has been computed

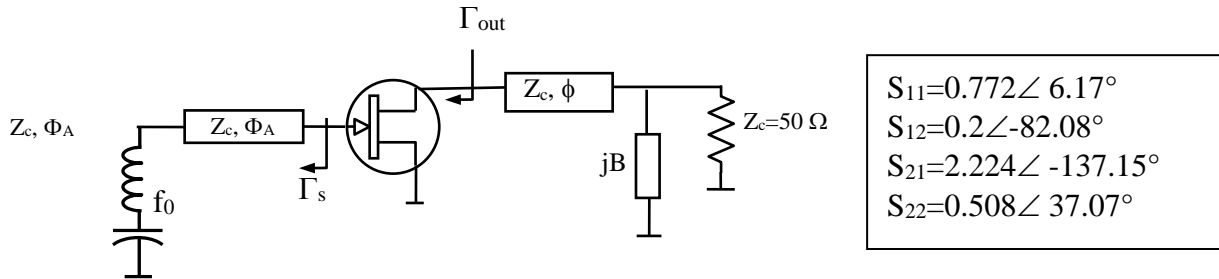Exercise 220914

The following scheme refers to an oscillator working at 24 GHz. The S parameters of the transistor are also reported on the figure.



The resonant circuit resonates at the oscillation frequency, where can be replaced with a short circuit. At all the other frequencies it can be approximated with an open circuit.

- 1) Select a suitable value for ϕ_A (use the mapping circles of Γ_s for obtaining $|\Gamma_{out}| \geq 1.5$)
- 2) Evaluate the parameters of the output network (ϕ, jB) to ensure the start of oscillation and the transfer of the output power to the external load (50Ω).
- 3) Is it possible to get oscillation at 24.1 GHz with the designed circuit? (assume the S parameters unchanged and the resonator replaced with an open circuit)

Solution

Draw on the electronic S.C. the source mapping circle with $|\Gamma_{out}|=1.5$. We must select a point inside this circle on the boundary of the chart ($|\Gamma_s|=1$). A suitable point is the open circuit ($\Gamma_s=1$), for which: $\Gamma_{out}=1.569 \angle 144.53^\circ$, $y_{out}=-1.613-2.01i$. In order to get $\Gamma_s=1$ with a short circuited stub (the resonator is assumed shorted), we need a length $\Phi_A=90^\circ$.

The load to be presented at the transistor output is represented by an admittance y_L given by:

$$y_L = -\frac{1}{3} \operatorname{Re}(y_{out}) - \operatorname{Im}(y_{out}) = 0.54 + j2.01$$


This load determine $|\Gamma_{in}|=1.091$ so the start of oscillation is guaranteed also at input side.

The single stub matching network at output is designed starting from y_L and moving toward load on the circle at constant $|\Gamma|$ until the circle $g=1$ is crossed (first intersection at $\phi=137.08^\circ$). The imaginary part of the normalized admittance at this point represents the susceptance $b=-2.806$ (then $B=-2.806 \cdot 0.02=0.05612$).

At $f=24.1$ GHz, considering the resonator an open circuit, the normalized impedance z_S determined by the stub with length $\Phi' = \Phi \cdot (24.1/24) = 90.375^\circ$ is given by $z_S = 1/j \tan(\Phi') = j0.006545$. Inserting this value into the S.C. the output reflection coefficient can be obtained: $\Gamma_{out}=0.607 \angle 13.046^\circ$. Being $|\Gamma_{out}| < 1$ the oscillation cannot start.

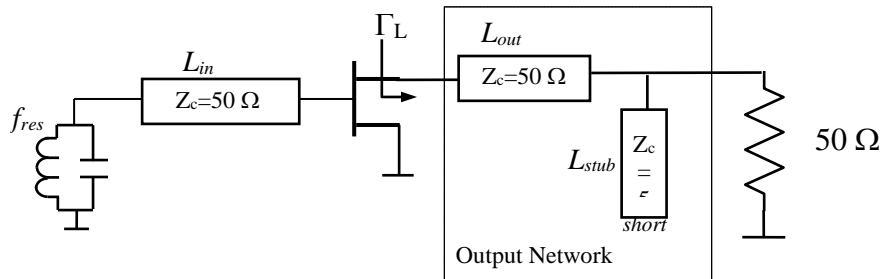Exercise 230215

We want to design the oscillator in the figure operating at 2 GHz:



The S parameters of the active device at 2 GHz are given in the following table as function of the bias current:

Ibias	S11	S12	S21	S22
10 mA	0.745 \angle -162.9°	0.063 \angle -7.1°	1.875 \angle 25.1°	0.602 \angle -119.6°
20 mA	0.76 \angle -145°	0.06 \angle -1.2°	1.92 \angle 43.6°	0.603 \angle -105.3°
30 mA	0.864 \angle -93.4°	0.064 \angle 27.4°	2.545 \angle 93.8°	0.627 \angle -64.2°

- 1) Select the bias current (imposing the necessary oscillation condition)
- 2) Assign a suitable value to the resonant frequency f_{res}
- 3) Assuming the relative dielectric constant of the lines $\epsilon_r=2.2$, evaluate the length L_{in} of the input line
- 4) Evaluate the reflection coefficient Γ_L to be presented at the transistor output and design the output network (i.e. evaluate the lengths L_{out} and L_{stub})

Solution

Using the electronic Smith Chart it can be observed that the active device is potentially instable ($k < 1$) only with $I_{bias}=30$ mA.

The resonant frequency of the resonator is assigned equal to the oscillation frequency. The input line is then an open stub with $b_s = \tan(\beta \cdot L_{in})$. For choosing b_s the mapping circle of the source is drawn with $|\Gamma_{out}|=1.2$. The chosen point must be also on the outer circle (two choices); we have selected $b_s = -1.39$. The electrical length of the input stub is then given by:

$$(\beta \cdot L_{in}) = \tan^{-1}(-1.2) = 129.8^\circ$$

It has:

$$Z_{out} = -0.27 - j1.386 \rightarrow Z_L = 0.09 + j1.386$$

The single-stub matching network transforms Z_L into 50 Ohm. We get:

$$(\beta \cdot L_{out}) = 44.4^\circ, \quad b_{stub} = -5.55 \rightarrow (\beta \cdot L_{stub}) = \tan^{-1}(1/5.55) = 10.21^\circ$$

Lengths computations:


$$\lambda = \frac{300}{f_0 \sqrt{\epsilon_r}} = 101.13 \text{ mm}, \quad \beta = \frac{360}{\lambda} = 3.56 \text{ }^\circ/\text{mm}$$

$$L_{in} = 129.8/\beta = 36.46 \text{ mm}, \quad L_{out} = 44.4/\beta = 12.47 \text{ mm}, \quad L_{stub} = 10.21/\beta = 2.87 \text{ mm}$$


Exercise 3

The following figure represents the general configuration of a microwave oscillator. Using the reported scattering parameters of the active device, evaluate the reflection coefficients Γ_1 and Γ_2 which ensure the start of oscillation (the magnitude of Γ_1 must be imposed equal to 1).

Hint: draw the mapping circle of the source with $|\Gamma_{out}|=1.2$ for determining Γ_1 . For evaluating Γ_2 determine the value of Z_{out} corresponding to the selected Γ_1 and assign $Z_2=|R_{out}/3|-jX_{out}$.

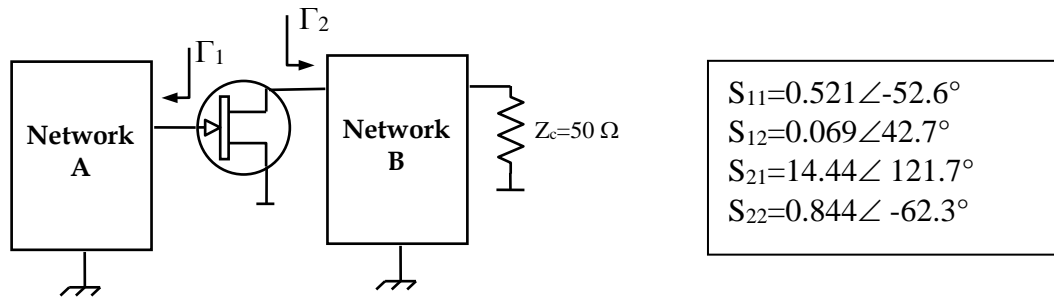

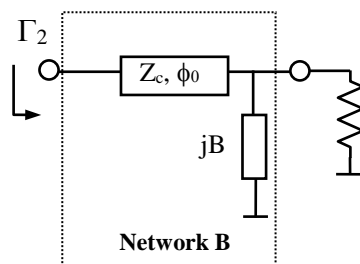Then design the network B, using the scheme in the following figure (assume $Z_c=50$ Ohm and evaluate the electrical length ϕ_0 and the susceptance B):




Solution


The assigned transistor is potentially unstable ($k=0.53$), so it can be used for realizing an oscillator. Using the electronic Smith Chart, the mapping circle with $|\Gamma_{out}|=1.2$ is drawn. The two intersections with the outer circle are: $\Gamma_{1a}=1 \angle 23^\circ$ and $\Gamma_{1b}=1 \angle -161.5^\circ$

Selecting "S Param." \rightarrow "Gamma OUT" the reflection coefficient at port 2 is obtained: $\Gamma_{out,a}=1.2 \angle -168^\circ$ ($\Gamma_{out,a}=1.2 \angle -28.7^\circ$) The S. chart reports also the normalized impedance $Z_{out,a}=-0.092-j0.103$ ($Z_{out,b}=-1.31-j3.44$).


Imposing the condition suggested in the text, the values of Z_2 and Γ_2 are then obtained: $Z_{2a} = 0.03+j0.103 \rightarrow \Gamma_{2a} = 0.94 \angle 168.2^\circ$ ($Z_{2b} = 0.44+j3.44 \rightarrow \Gamma_{2b} = 0.935 \angle 32^\circ$)

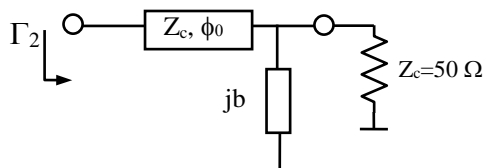The matching network is designed according the well-known procedure:



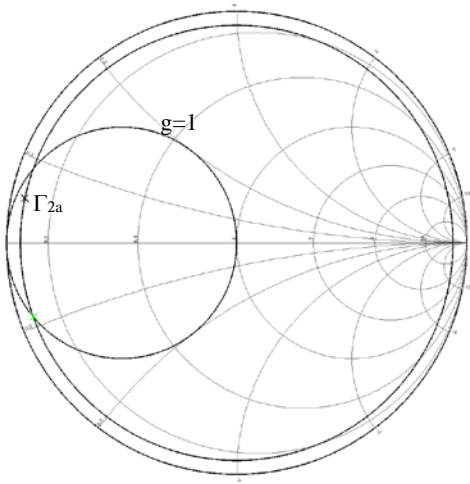

$\phi_0=15.85^\circ, b=5.5$

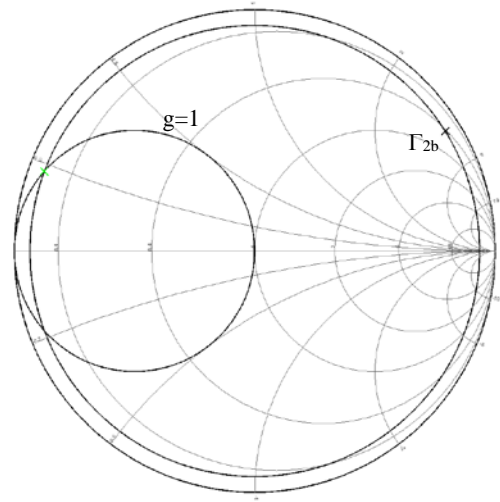

$\phi_0=63.7^\circ, b=-5$