
MICROWAVE MIXERS

Mixer Goal

Translate the carrier frequency of a RF signal.


Conceptually this implies a multiplication:

$$V_{RF} = V_M(t) \cos(\omega_{RF}t + \Phi(t))$$

$$V_{OL} = V_o \cos(\omega_{OL}t)$$


$$V_U = V_{RF} \cdot V_{OL} = V_M(t) V_o \cos(\omega_{RF}t + \phi(t)) \cos(\omega_{OL}t) =$$
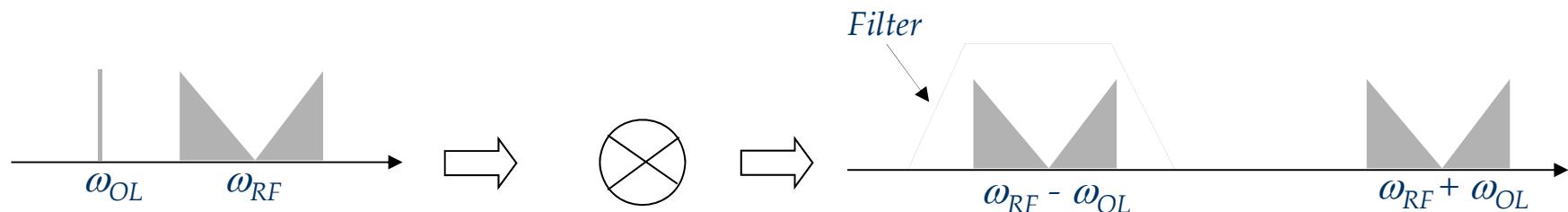
$$\frac{V_0}{2} \left[V_M(t) \cos((\omega_{RF} - \omega_{OL})t + \phi(t)) + V_M(t) \cos((\omega_{RF} + \omega_{OL})t + \phi(t)) \right]$$




Mixer in communication systems

Frequency conversion receiver:

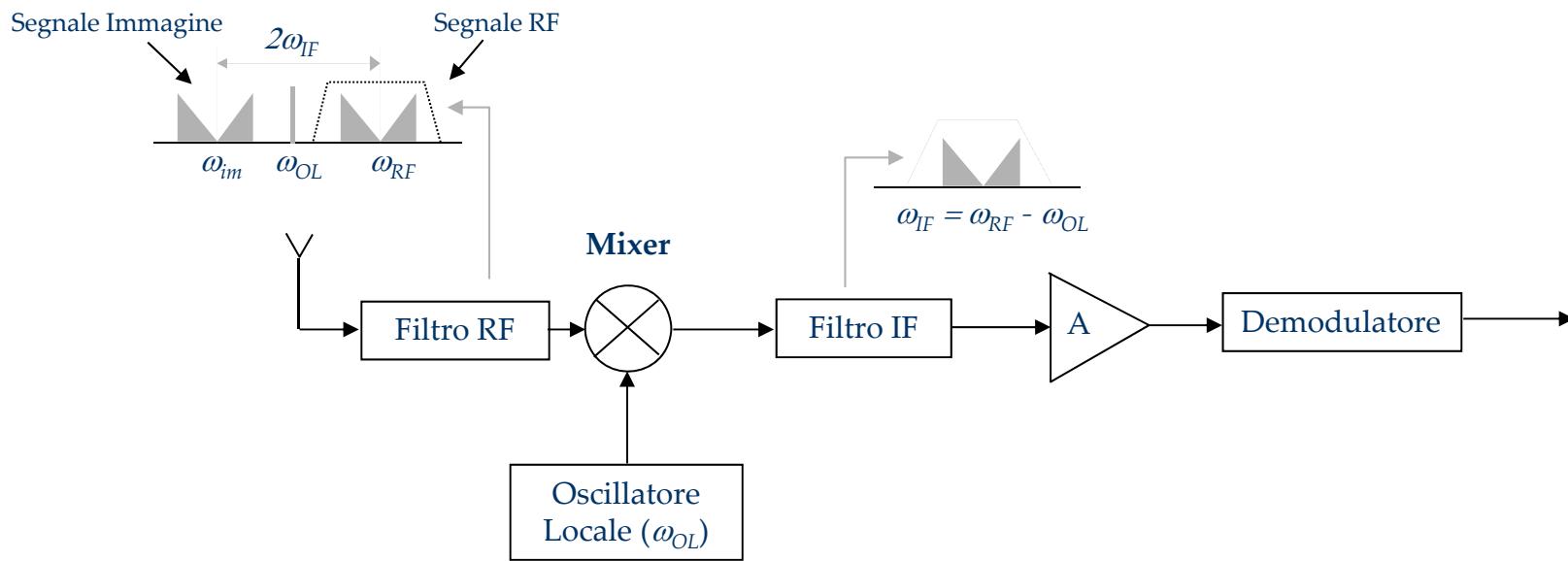

Practical implementation of a microwave mixer

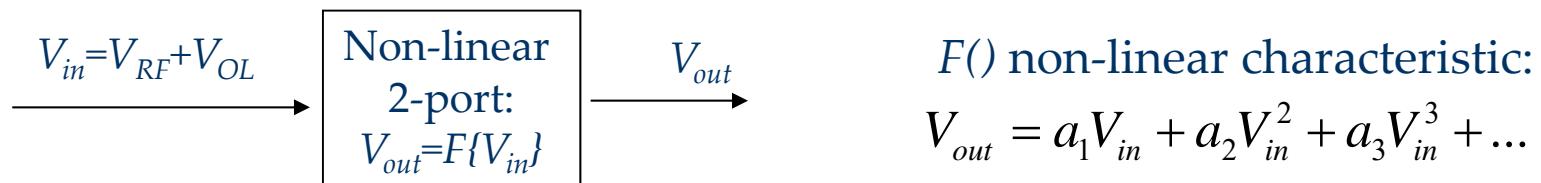At microwave frequency is more easy to realize the frequency conversion exploiting 2-port the non-linear devices:



Substituting V_{RF} and V_{OL} and using the first 2 non-linear terms of the expansion:

$$V_{out} = \frac{a_2}{2} (V_0 + V_M) + a_1 (V_0 \cos(\omega_0 t) + V_M \cos(\omega_{RF} t)) + \\ + \frac{a_2}{2} (V_0^2 \cos(2\omega_0 t) + V_M^2 \cos(2\omega_{RF} t)) + a_2 (2V_0 V_M \cos(\omega_0 t) \cdot \cos(\omega_{RF} t)) + \dots$$

Classes of microwave mixers

The most used non-linear device is a **Schotcky diode**.


There are two main classes of microwave mixers:

- **Mixers with a single diode (single-ended)**
- **Balanced Mixers (with 2 o 4 diodes)**


Parameters of a microwave mixer:

- Conversion Loss(dB) (5-15 dB)
 - Linearity (referred to the translated RF signal)
 - Noise
 - Suppression of spurious products
 - Input-output match
 - Isolation (RF-OL, IF-OL)
-

Analysis of single-ended mixers

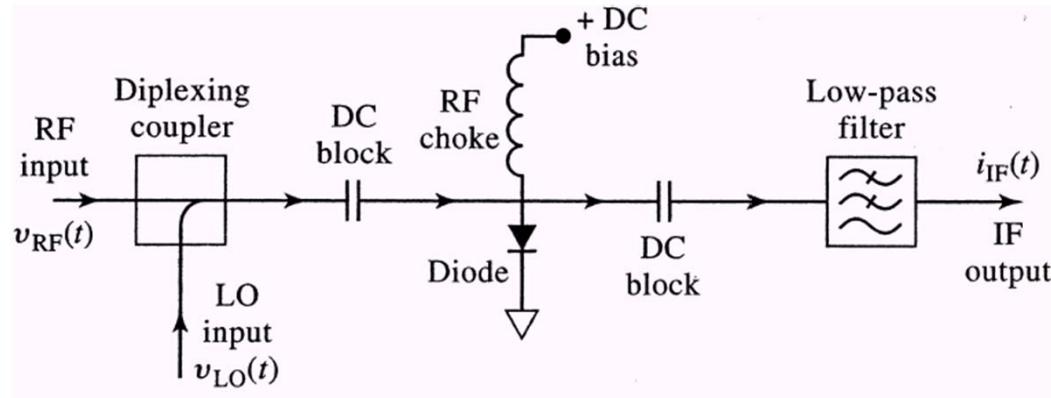

Equivalent circuit:

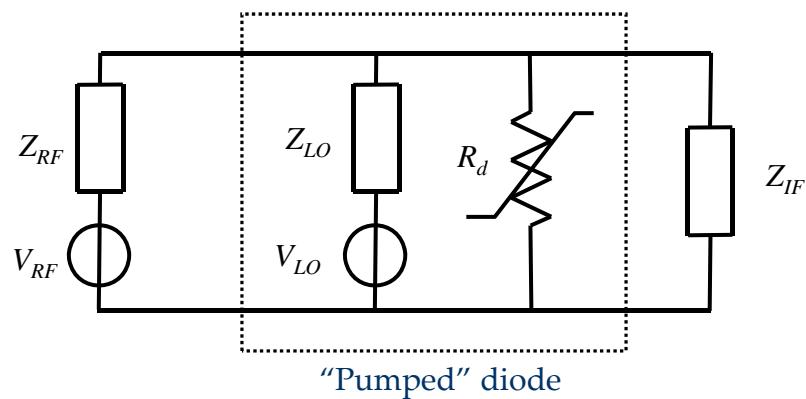

The diode (R_d) is represented by the exponential curve:

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

It can be assumed memoryless (in a first as approximation)

Distortion in a mixer


Effects of distortion:

- The spectrum of the frequency-translated signal around the new carrier frequency is different from the original one
- New replicas of the original RF signal, LO and combination of them are generated at different carrier frequencies


The local linearity is described by the same parameters used for amplifiers ($P_{1\text{dB}}$, IP); in the mixers case the input-output frequencies are different. Moreover the mentioned parameters depend also on the power level of the local oscillator

Single-balanced mixers

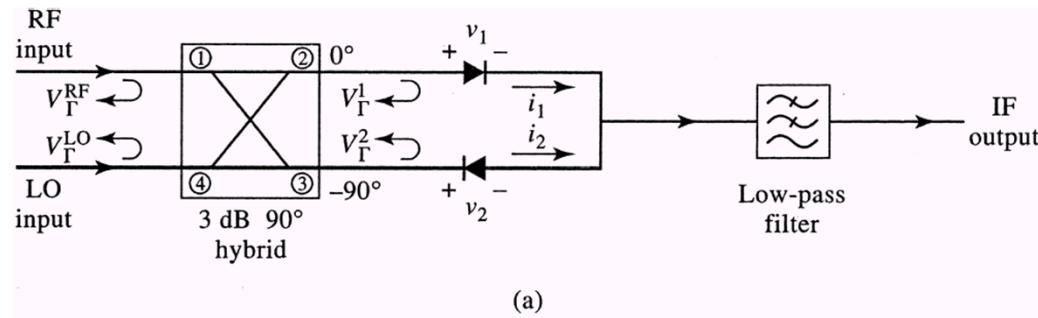They allow an intrinsic suppression of some spurious products.
An higher power from the LO is requested. A better linearity is obtained, together with higher losses (compared to single-ended mixers)



(a)

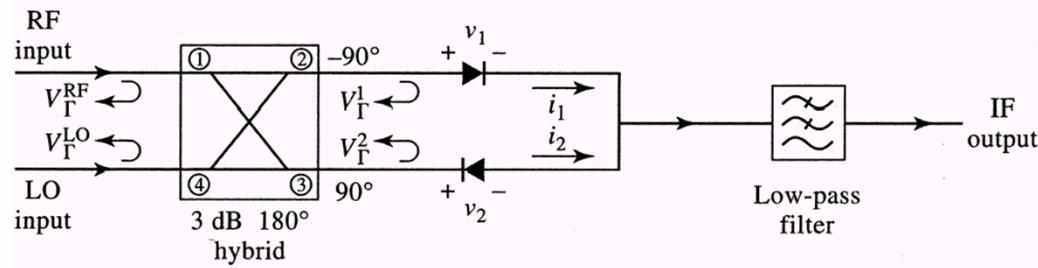


Balance mixer with a 180°hybrid

$$V_{RF} = V_r \cos(\omega_{RF} t)$$

$$V_{OL} = V_p \cos(\omega_P t)$$

$$V_1 \doteq V_{RF} + V_{OL}$$

$$V_2 \doteq V_{RF} - V_{OL}$$

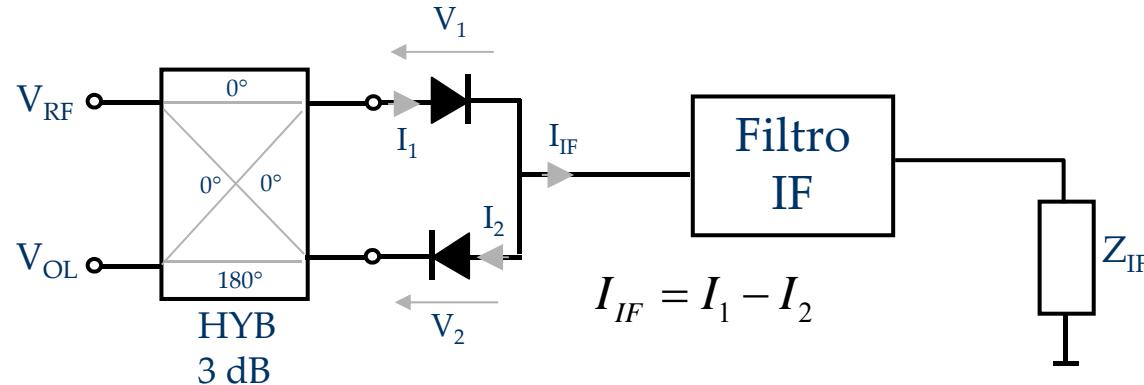

I/V characteristic of diodes: $I_D = a_1 V_D + a_2 V_D^2 + a_3 V_D^3 + \dots$


$$\text{Then: } I_1 = a_1 V_1 + a_2 V_1^2 + a_3 V_1^3 + \dots \quad I_2 = -a_1 V_2 + a_2 V_2^2 - a_3 V_2^3 + \dots$$

The overall current is given by:

$$\begin{aligned} I_{IF} &= a_1(V_1 + V_2) + a_2(V_1^2 - V_2^2) + a_3(V_1^3 + V_2^3) + \dots = 2a_1 V_{RF} + 4a_2 V_{RF} V_{OL} + 2a_3 (V_{RF}^3 + 3V_{RF} V_{OL}^2) + \dots \\ &= 2a_1 V_r \cos(\omega_{RF} t) + 2a_2 V_r V_p \left[\cos((\omega_{RF} - \omega_p)t) + \cos((\omega_{RF} + \omega_p)t) \right] + \\ &\quad + 2a_3 \left[V_r \cos^3(\omega_{RF} t) + 3V_r V_p^2 \cos^2(\omega_p t) \cos(\omega_{RF} t) \right] + \dots \end{aligned}$$

Characteristics of 180° hybrid mixer

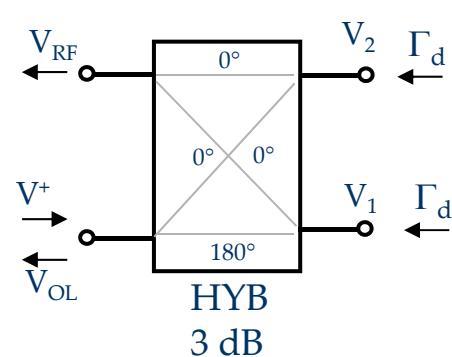- All harmonics of LO are suppressed at IF
- Also the even harmonics of RF are suppressed
- AM Noise of LO is eliminated (NOT the phase noise)
- RF-LO ports are intrinsically isolated




$$V_2 = \frac{V^+}{\sqrt{2}}, \quad V_1 = -\frac{V^+}{\sqrt{2}}$$

$$V_{OL} = -\frac{\Gamma_d V_1}{\sqrt{2}} + \frac{\Gamma_d V_2}{\sqrt{2}} = \frac{\Gamma_d V^+}{2} + \frac{\Gamma_d V^+}{2} = \Gamma_d V^+ \Rightarrow \Gamma_{OL} = \Gamma_d$$

$$V_{RF} = \frac{\Gamma_d V_1}{\sqrt{2}} + \frac{\Gamma_d V_2}{\sqrt{2}} = -\frac{\Gamma_d V^+}{2} + \frac{\Gamma_d V^+}{2} = 0 \Rightarrow S_{OL-RF} = 0$$

Double-balanced Mixer

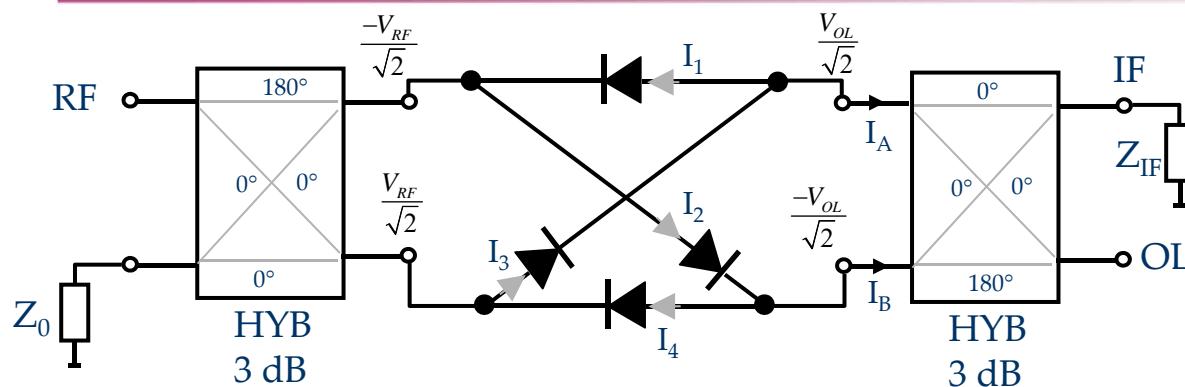

$$I_D = a_1 V_D + a_2 V_D^2$$

$$V_2 = \frac{-V_{RF} + V_{OL}}{\sqrt{2}}, \quad V_1 = \frac{V_{RF} + V_{OL}}{\sqrt{2}}$$

$$V_3 = \frac{V_{RF} - V_{OL}}{\sqrt{2}}, \quad V_4 = \frac{-V_{RF} - V_{OL}}{\sqrt{2}}$$

$$V_A = kI_A = k(I_3 - I_1) = k(a_1 V_3 + a_2 V_3^2 - a_1 V_1 - a_2 V_1^2) = k[a_1(V_3 - V_1) + a_2(V_3^2 - V_1^2)] = \\ = \frac{k}{\sqrt{2}}[-2a_1 V_{OL} - 4a_2 V_{OL} V_{RF}]$$


$$V_B = kI_B = k(I_2 - I_4) = k(a_1 V_2 + a_2 V_2^2 - a_1 V_4 - a_2 V_4^2) = k[a_1(V_2 - V_4) + a_2(V_2^2 - V_4^2)] = \\ = \frac{k}{\sqrt{2}}[2a_1 V_{OL} - 4a_2 V_{OL} V_{RF}]$$

$$V_{IF} = \frac{V_A + V_B}{\sqrt{2}} = -\frac{k}{2}[8a_2 V_{OL} V_{RF}]$$


Characteristics of double-balanced mixers

- ALL harmonics of LO and RF are suppressed
 - ALL even intermodulation products are suppressed
 - Perfect isolation LO-RF
 - High LO power required
 - Worsens conversion loss
 - Linearity improvement
-

Image-suppression mixers

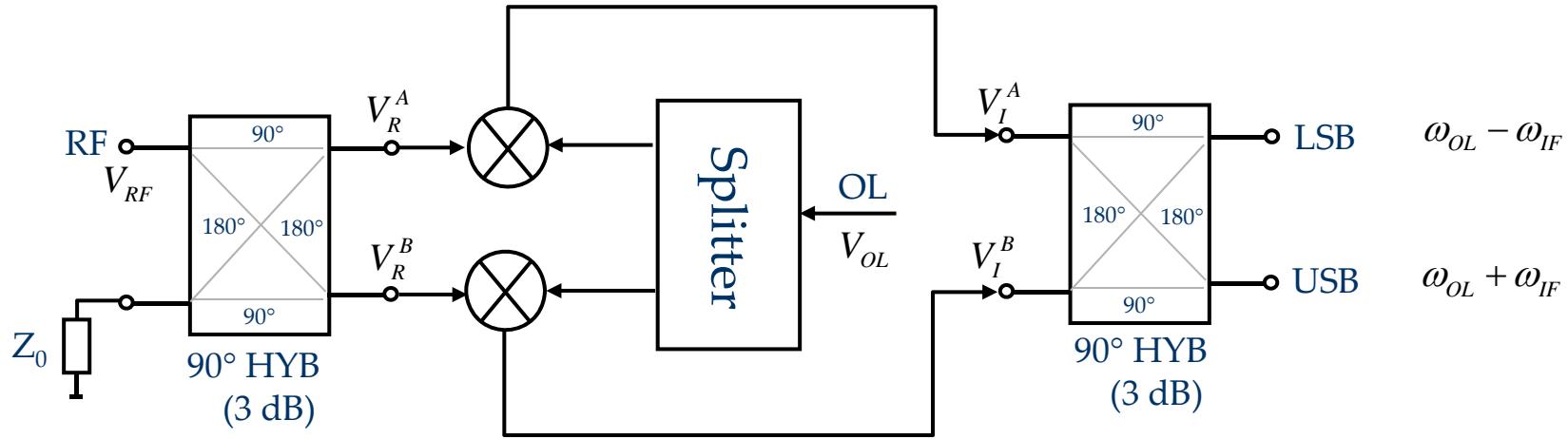

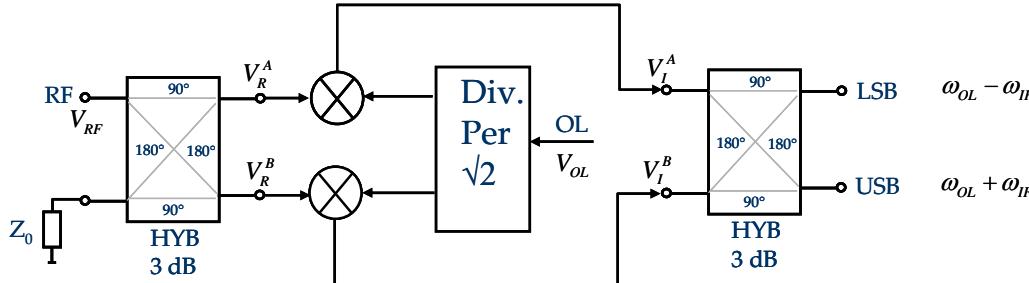This configuration separates the translated and image signals. The image filter is then no more necessary (or its requirements are strongly reduced)



$$V_{OL} = V_0 \cos(\omega_0 t), \quad V_{RF} = V_U \cos((\omega_0 + \omega_{IF})t) + V_L \cos((\omega_0 - \omega_{IF})t)$$

$$V_R^A = \frac{V_U}{\sqrt{2}} \sin((\omega_0 + \omega_{IF})t) + \frac{V_L}{\sqrt{2}} \sin((\omega_0 - \omega_{IF})t), \quad V_R^B = -\frac{V_U}{\sqrt{2}} \cos((\omega_0 + \omega_{IF})t) - \frac{V_L}{\sqrt{2}} \cos((\omega_0 - \omega_{IF})t)$$

$$V_I^A = k \frac{V_U V_0}{2} [\sin((\omega_0 + \omega_{IF})t) \cos(\omega_0 t)] + k \frac{V_L V_0}{2} [\sin((\omega_0 - \omega_{IF})t) \cos(\omega_0 t)] =$$

$$= k \frac{V_U V_0}{4} [\sin((2\omega_0 + \omega_{IF})t) + \sin(\omega_{IF} t)] + k \frac{V_L V_0}{4} [\sin((2\omega_0 - \omega_{IF})t) - \sin(\omega_{IF} t)]$$

$$V_I^B = k \frac{V_U V_0}{2} [-\cos((\omega_0 + \omega_{IF})t) \cos(\omega_0 t)] + k \frac{V_L V_0}{2} [-\cos((\omega_0 - \omega_{IF})t) \cos(\omega_0 t)] =$$

$$= k \frac{V_U V_0}{4} [-\cos((2\omega_0 + \omega_{IF})t) - \cos(\omega_{IF} t)] - k \frac{V_L V_0}{4} [\cos((2\omega_0 - \omega_{IF})t) + \cos(\omega_{IF} t)]$$

$$V_{USB} = j \left(\frac{V_I^B}{\sqrt{2}} \right) - \frac{V_I^A}{\sqrt{2}} = -k \frac{V_U V_0}{2\sqrt{2}} [\sin((2\omega_0 + \cancel{\omega_{IF}})t) + \sin(\omega_{IF} t)] - k \frac{V_L V_0}{2\sqrt{2}} [\sin((2\omega_0 - \cancel{\omega_{IF}})t)]$$

$$V_{LSB} = j \left(\frac{V_I^A}{\sqrt{2}} \right) - \frac{V_I^B}{\sqrt{2}} = k \frac{V_L V_0}{2\sqrt{2}} [\cos(\omega_{IF} t)]$$