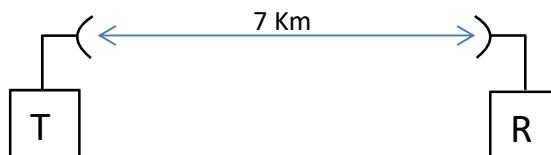


## RF SYSTEMS

Written Test of September 1, 2016

Surname & Name
Identification Number
Signature

### Exercise 1



The figure shows a terrestrial link operating at 4 GHz with bandwidth  $B=2$  MHz. The two stations are located 7 Km away and the antennas are identical with the following features:


Efficiency  $\eta=0.9$ . Directivity function  $f(\theta)=1$  for  $0 < \theta < 35^\circ$ ,  $=0$  elsewhere.

- 1) Evaluate the gain  $G$  of the antennas
- 2) It is known the system noise temperature  $T_{\text{sys}}=900$  °K of the station R. What is the power to be transmitted from T in order to get the system SNR equal to 30 dB? Assume the antennas pointed for the maximum gain.
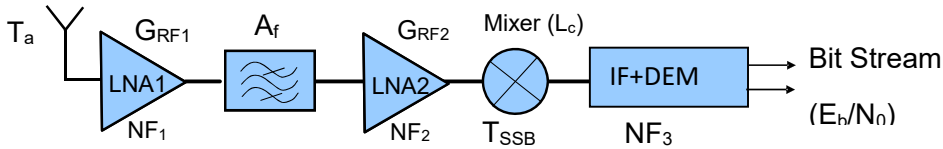
## Exercise 2

The scheme in the figure represents the RF front-end of a receiver for a satellite earth station operating at 4 GHz with signal bandwidth 100 MHz.

The goal is to get the system SNR equal to 27 dB with the power of the received signal equal to -100 dBW



$NF_1 = ?$ $G_{RF1} = 10 \text{ dB}$ $T_a = 60 \text{ °K}$ $A_f = 0.1 \text{ dB}$ $G_{RF2} = 20 \text{ dB}$ $NF_2 = 2 \text{ dB}$ $L_c = 4 \text{ dB}$ $T_{SSB} = 200 \text{ °K}$ $NF_3 = 2 \text{ dB}$
---


- Evaluate the Noise Figure  $NF_{RF1}$  of LNA1 in order to meet the goal
- What is the maximum data rate  $R$  of the demodulated bit stream with  $(E_b/N_0) = 18 \text{ dB}$ ?

Hint: Use the expression relating the system SNR to  $E_b/N_0$

Use  $K = -228.6 \text{ dBW}/(\text{Hz} \cdot \text{°K})$  (Boltzmann Constant)
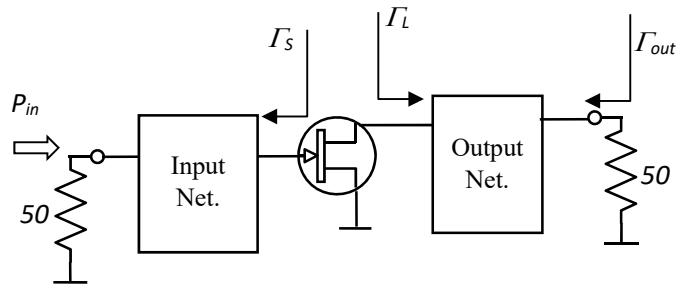
### Exercise 3

We want design a single stage amplifier at 5 GHz using the scheme in the following figure (input and output networks are lossless):



The transistor to be used has the following parameters:

$$S_{11}=0.52\angle 143.8^\circ \quad S_{21}=4.255\angle 28.7^\circ \quad S_{12}=0.081\angle 4.9^\circ \quad S_{22}=0.287\angle -87.7^\circ$$

$$\Gamma_{\text{opt}}=0.19\angle -170.4^\circ \quad F_{\text{min}}=0.85 \text{ dB} \quad R_n=0.06 \text{ (Noise parameters)}$$

3<sup>th</sup> order Intercept point (IP3): 20 dBm

The amplifier must exhibit the transducer gain as high as possible compatibly with the stability requirement and the noise figure not larger than 1 dB.

- 1) Select a proper value for  $\Gamma_S$  and  $\Gamma_L$  in order to satisfy the above requirements
- 2) Assuming at input a 2-tone signal (4.95 and 5.05 GHz) with available mean power ( $P_{in}$ ) equal to -10 dBm, evaluate the output mean power  $P_{out}$ . Compute also the power at each intermodulation frequency (specify the value of these frequencies)

## Solution

### Exercise 1

The antenna gain is obtained from the formula:

$$G = \eta 4\pi \left[ \int_0^{2\pi} d\varphi \int_0^{\pi} g(\theta) \sin \theta d\theta \right]^{-1} = 2\eta \int_0^{20^\circ} \sin \theta d\theta = \frac{2\eta}{1 - \cos(35^\circ)} = 9.95 \text{ (10 dB)}$$

The system SNR is defined as:

$$SNR_{\text{sys}} = \frac{P_{\text{rec}}}{KT_{\text{sys}} B} = 30 \text{ dB}$$

Then the received power must be  $P_r = 30 + KT_{\text{sys}}|_{\text{dBm}} + 10\log(B) = 30 - 169 + 63 = -76 \text{ dBm}$

The Friis equation for the given link is:

$$P_{\text{rec}} = P_{\text{tr}} + 2G - L_f$$


$$\text{with: } L_f = 20 \cdot \log\left(\frac{4\pi R}{\lambda}\right) = 121.38 \text{ dB, } (\lambda = 3\text{e}8/4\text{e}9 = 0.075\text{m})$$

Then the transmitted power results:

$$P_{\text{tr}} = P_{\text{rec}} - 2G + L_f = -76 - 20 + 121.38 = 25.4 \text{ dBm}$$

## Exercise 2

Equivalent noise scheme :

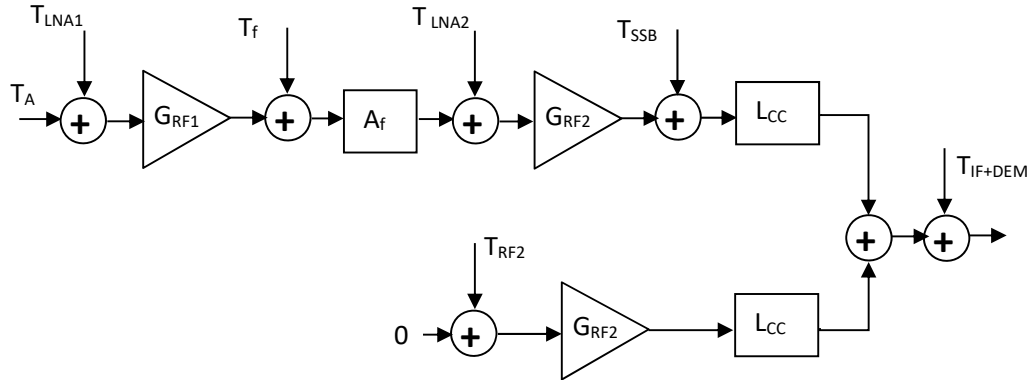

Where:

$$T_{LNA2} = 290 \left( 10^{\frac{NF_2}{10}} - 1 \right) = 169.62 \text{ °K}, \quad T_f = 290 \left( 10^{\frac{A_f}{10}} - 1 \right) T_0 = 6.755 \text{ °K}$$

$$T_{IF+DEM} = 290 \left( 10^{\frac{NF_3}{10}} - 1 \right) = 169.62 \text{ °K}$$

The equivalent noise temperature at the input of the receiver is then given by:

$$T_{sys} = T_A + T_{LNA1} + \frac{T_f}{G_{RF1}} + 2 \frac{T_{LNA2} A_f}{G_{RF1}} + \frac{T_{SSB} A_f}{G_{RF1} G_{RF2}} + \frac{T_{IF+DEM} L_c A_f}{G_{RF1} G_{RF2}}$$

$$= T_{LNA1} + 36.03$$

Imposing the SNR it results:  $N=KT_{sys}B=P_{rec}-SNR=-127 \text{ dBW}$ . The equivalent temperature is then given by:

$$10 \log(T_{sys}) = -127 - (KB)_{dB} = 21.6 \rightarrow T_{sys} = 144.5 \text{ °K}$$

Finally the  $NF_1$  is obtained:

$$T_{LNA1} = T_{sys} - 36.03 = 48.51 \text{ °K}$$

$$NF_1 = 10 \log \left( 1 + \frac{T_{LNA1}}{290} \right) = 0.67 \text{ dB}$$

The system SNR is equal to 27 dB and is expressed as:

$$SNR = \frac{P}{N_0 \cdot B} = \frac{E_B}{N_0} \left( \frac{R}{B} \right) = 27 \text{ dB}$$

then:  $(R/B)_{dB} = 27 - 18 = 9 \text{ dB} \rightarrow R = 7.94 B = 794 \text{ Mbit/sec}$

### Exercise 3

The transistor is unconditionally stable with  $G_{max}=16.8$  dB and  $NF_{min}=0.85$ .

We draw first the circle  $NF=1$  dB on the S.C. Then we look for the circle with constant Available power gain that is tangent to NF circle. We get  $G_{av}=15.11$  dB. Selecting the tangent point on the S.C and imposing conjugate matching at output we get:

$\Gamma_s=.464\angle-144.6$ ,  $\Gamma_L=.488\angle97.6$ ,  $NF=1$  dB,  $G_T=15.11$  dB.

The power in each tone at output is  $P_0=-10-3+G_T=2.11$  dBm. The power in each interm. line is given by:

$P_{int}=3*P_0-2*IP_3=3*2.11-40=-33.67$  dBm