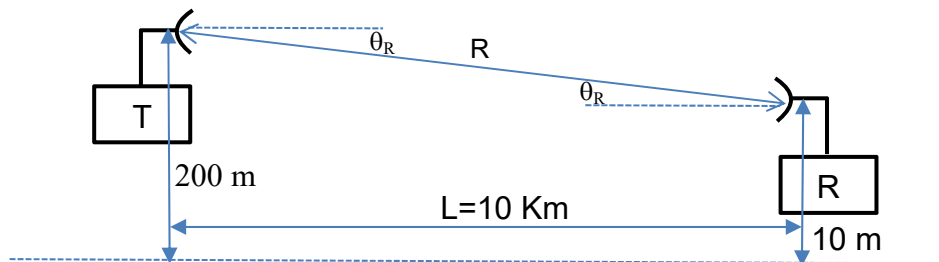


**RF SYSTEMS -  
Written Test of February 3<sup>th</sup>, 2016**

|                              |
|------------------------------|
| <b>Surname &amp; Name</b>    |
| <b>Identification Number</b> |
| <b>Signature</b>             |

Exercise 1



A terrestrial link operating at 6 GHz is illustrated in the above figure. The antennas of the receiver and transmitter are identical and are characterized by the following directivity function:


$$f(\theta) = \begin{cases} 1 - \frac{\sin(\theta)}{\sin(\theta_0)} & 0 < \theta < \theta_0 \\ 0 & \theta_0 < \theta < \pi \end{cases} \quad \theta_0 = \pi/18$$

The radiation impedance  $Z_R$  and the loss resistance  $R_p$  of the antennas are also given:  $Z_R = 50\Omega$ ,  $R_p = 12.64\Omega$ .

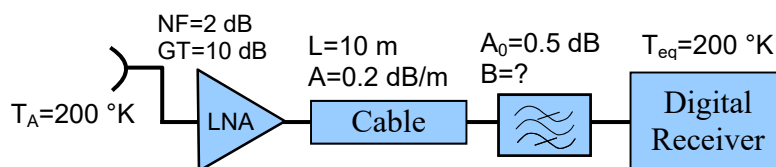1) Evaluate the gain of the antennas [Hint:  $\int \sin^2(x) dx = \frac{1}{2}(x - \sin(x)\cos(x))$ ]

The transmitted signal is a 64-QAM modulated carrier with the following parameters: roll-off factor  $\alpha = 0.3$ , data rate  $R = 155$  Mbit/sec, transmitted power  $P_T = 10$  dBm.


The RF front-end of R is schematized in the following figure:



- 1) Evaluate the filter bandwidth
- 2) Evaluate the system  $SNR_{sys}$  and the  $(E_b/N_0)$  ratio requested by the digital receiver
- 3) Assume the  $P_{1dB}$  of the transmitter equal to 20 dBm. Evaluate the transmitted mean power (2-tone signal) determining the intermodulation mean power equal to the system noise power at the input of R

### Exercise 2

Consider the following 2-port circuit:

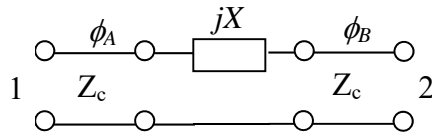

$$Z_c = 50 \Omega$$

$$\phi_1 = 45^\circ$$


$$\phi_2 = 100^\circ$$

$$X = 100 \Omega$$

Evaluate the scattering parameters  $S_{11}$ ,  $S_{22}$ ,  $S_{12}$ . Hint: use the eigenvalues method for the inner part (reactance  $X$ ) and then move the reference sections of the two ports.
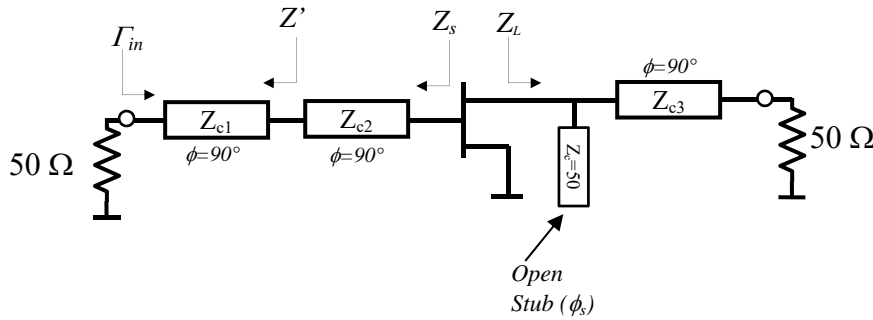
### Exercise 3

The low noise amplifier at 2 GHz with the scheme in the figure must be designed.



$$\begin{aligned}
 S_{11} &= 0.519 \angle -133.27^\circ \\
 S_{12} &= 0.095 \angle 17.7^\circ \\
 S_{21} &= 4.071 \angle 41.2^\circ \\
 S_{22} &= 0.392 \angle -90.39^\circ \\
 NF_{\min} &= 0.35 \text{ dB} \\
 \Gamma_{s,\text{opt}} &= 0.52 \angle 94.6^\circ \\
 r_n &= 0.081
 \end{aligned}$$

The goal of the design is to obtain the transducer gain  $G_T > 14$  dB and the noise figure  $NF = 1$  dB.

- Evaluate  $Z_S$  and  $Z_L$  in order to fit this requirements.
- Evaluate  $Z_{c1}$ ,  $Z_{c2}$ ,  $Z_{c3}$  and  $\phi_s$ .
- Evaluate the input reflection coefficient  $\Gamma_{in}$

The input network is constituted by two sections of transmission lines  $\lambda/4$  long. The chosen value of  $Z_s$  must be compatible with this network topology (for computing  $Z_{c1}$  and  $Z_{c2}$  select a suitable value for  $Z'$ ).

The stub length  $\phi_s$  and the characteristic impedance  $Z_{c3}$  of the line must be evaluated for the output network (note that the line reports a real admittance in parallel to the stub).

## Solution

### Exercise 1

$$\text{Efficiency: } \eta = \frac{Z_R}{Z_R + R_p} = 0.7982$$

Antenna Gain:

$$G = \frac{4\pi\eta}{\int_0^{2\pi} d\varphi \int_0^{\theta_0} (1 - \sin(\theta)/\sin(\theta_0)) \sin(\theta) d\theta} = \frac{2\eta}{1 - \cos(\theta_0) - \left[ \frac{\theta_0 - \sin(\theta_0)\cos(\theta_0)}{2\sin(\theta_0)} \right]} = 316.23 \text{ (25 dB)}$$

Link Equation:

$$P_r = P_t - 20 \cdot \log\left(\frac{4\pi R}{\lambda}\right) + 2G_A + 20 \cdot \log(f(\theta_R))$$

$$R = \sqrt{L^2 + 0.19^2} = 10.002 \text{ Km}, \quad \theta_R = \tan^{-1}\left(\frac{0.19}{10}\right) = 1.0885^\circ$$

$$f(\theta_R) = 1 - \frac{\sin(1.0885^\circ)}{\sin(10^\circ)} = 0.8906$$

Substituting:

$$P_r = 10 - 20 \cdot \log\left(\frac{4\pi 10^4}{5 \cdot 10^{-2}}\right) + 2 \cdot 25 + 20 \cdot \log(0.8906) \cong -69 \text{ dBm}$$

Expression of  $\text{SNR}_{\text{sys}}$ :

$$\text{SNR}_{\text{sys}} = \frac{P_r}{KT_{\text{sys}}B}, \quad B = \frac{R(1+\alpha)}{\log_2 64} = 33.58 \text{ MHz}, \quad K = 1.38 \cdot 10^{-23}.$$

Evaluation of  $T_{\text{sys}}$ :

$$T_{\text{sys}} = T_A + T_{LNA} + \frac{T_1}{G_T} + T_{eq} \frac{A_1}{G_T}$$

$$T_{LNA} = 290(10^{0.2} - 1) = 169.62, \quad G_T = 10$$

$$A_1 = A \cdot 10 + A_0 = 2.5 \text{ dB}, \quad T_1 = 290(10^{0.25} - 1) = 225.7$$

$$T_{\text{sys}} = 427.75 \text{ °K}$$

Evaluation of  $\text{SNR}_{\text{sys}}$ :

$$\text{SNR}_{\text{sys}} = \frac{P_r}{KT_{\text{sys}}B} = \frac{1.259 \cdot 10^{-10}}{1.98 \cdot 10^{-13}} = 635.82 \text{ (28 dB)}$$

$$\frac{E_b}{N_0} = \frac{\text{SNR}_{\text{sys}}}{(R/B)} = \frac{635.82}{4.61} = 138 \text{ (21.4 dB)}$$

Received intermodulation power ( $P_{\text{int,rec}}$ ):



$$P_{\text{int,rec}} = P_{\text{int}} - 20 \cdot \log\left(\frac{4\pi R}{\lambda}\right) + 2G_A + 20 \cdot \log(f(\theta_R)) = P_{\text{int}} - 79 = P_{\text{noise}} = -97 \text{ dBm}$$

$$P_{\text{int}} = 79 - 97 = -18 \text{ dBm} = 3(P_m - 3) - 2IP_3 + 3 = 3P_m - 2P_{1dB} - 26$$

$$P_m = \frac{P_{\text{int}} + 2P_{1dB} + 26}{3} = 16 \text{ dBm}$$
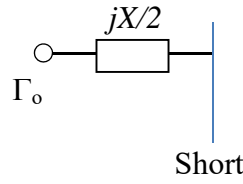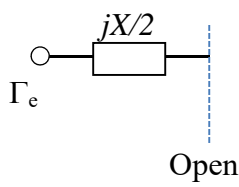
### Exercise 2

Let consider the inner part. The eigen-networks and the corresponding eigenvalues result:



$$\Gamma_e = 1, \Gamma_o = \frac{jX/2 - 50}{jX/2 + 50}$$

Then:

$$S'_{11} = \frac{1}{2}(\Gamma_e + \Gamma_o) = \frac{j100}{100 + j100} = \frac{j}{1+j} = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}}$$

$$S'_{12} = \frac{1}{2}(\Gamma_e - \Gamma_o) = \frac{100}{100 + j100} = \frac{1}{1+j} = \frac{1}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

Now, moving outwards the reference sections, we get the scattering parameters of the complete 2-port:

$$S_{11} = S'_{11} e^{-2j\phi_A} = \frac{1}{\sqrt{2}} e^{j\left(-\frac{\pi}{2} + \frac{\pi}{4}\right)} = \frac{1}{\sqrt{2}} e^{-j\frac{\pi}{4}}$$

$$S_{22} = S'_{11} e^{-2j\phi_B} = \frac{1}{\sqrt{2}} e^{j\left(-\frac{10\pi}{9} + \frac{\pi}{4}\right)} = \frac{1}{\sqrt{2}} e^{-j\frac{31\pi}{36}}$$

$$S_{12} = S'_{12} e^{-j(\phi_A + \phi_B)} = \frac{1}{\sqrt{2}} e^{j\left(-\frac{29\pi}{36} - \frac{\pi}{4}\right)} = \frac{1}{\sqrt{2}} e^{-j\frac{19\pi}{18}}$$

### Exercise 3

The value of  $Z_s$  must be on the circle with  $NF=1$  dB and inner to the circle  $Gav=14$  dB. Moreover, due to the topology of the input network  $Z_s$  must be real. Using the electronic Smith chart we find that there is only one point on the  $\Gamma_s$  plane satisfying the above conditions:

$$\Gamma_s = 0.501 \angle 180^\circ \Rightarrow z_s = 0.332 \Rightarrow Z_s = 50 \cdot z_s = 16.6 \Omega$$

The two  $\lambda/4$  transformers operate as impedance inverters with  $K=Z_c$ . Imposing  $Z'=30 \Omega$  (about in the middle of the range  $Z_s \rightarrow 50$ ) we get:

$$Z_{c1} = \sqrt{50 \cdot Z'} = 38.73 \, \Omega, \quad Z_{c2} = \sqrt{Z_s \cdot Z'} = 22.32 \, \Omega$$

Using the Smith chart, selecting “optimum gamma, load” we get:

$$\Gamma_L = 0.615 \angle 96.92^\circ, \quad G_T = 14.482 \, \text{dB}, \quad NF = 1 \, \text{dB}$$

For designing the output network we observe that the impedance presented by this network at the transistor output is constituted by the parallel of the susceptance of the open circuited stub with the resistance obtained from the  $\lambda/4$  transformer. The obtaining YL from the Smith chart:

$$y_L = 0.506 - j0.993 \Rightarrow Y_L = \frac{y_L}{50} = 0.01012 - j0.01986$$

Then:

$$b_s = \tan(\phi_s) = -0.993 \Rightarrow \phi_s = 135.2^\circ$$

$$\frac{Z_{c3}^2}{50} = \frac{1}{0.01012} \Rightarrow Z_{c3} = 70.29 \, \Omega$$

For computing  $G_{in}$  we must evaluate first gamma at the input of the transistor ( $\Gamma_{in,t}$ ) from the Smith chart (“S Param., Gamma IN”):

$$\Gamma_{in,t} = 0.696 \angle -158.035^\circ \quad (Z_{in,t} = 9.3 - j9.4)$$

Then we evaluate the impedance  $Z_1$  at the input of the second  $\lambda/4$  transformer (see the figure):

$$Z_1 = \frac{Z_{c2}^2}{Z_{in,t}} = 26.5 + j26.8$$

The input impedance is obtained from the first  $\lambda/4$  transformer:

$$Z_{in} = \frac{Z_{c1}^2}{Z_1} = 28 - j28.3 \quad (z_{in} = 0.56 - j0.57)$$

$$\Gamma_{in} = 0.432 \angle -107.91^\circ \quad (\text{from the Smith chart})$$

