

RF SYSTEMS
Written Test of July 6th, 2016

Surname & Name
Identification Number
Signature

Exercise 1


Consider a spacecraft for deep-space exploration in orbit around Jupiter. It is equipped with a digital transmitter operating at 12 GHz (transmitted power $P_T=20$ W). The antenna of the vehicle is a 5m dish with aperture efficiency $\epsilon_a=0.6$ and efficiency $\eta=0.8$. The receiving station on the Earth has a 70m dish antenna with $\epsilon_a=0.65$ and $\eta=0.9$; the receiver exhibits a overall system noise temperature of $T_{sys}=25$ °K.

Imposing the maximum BER at the receiver output equal to 10^{-3} , the required E_b/N_0 ration must be 4.75 (6.77 dB).

- 1) Evaluate the gain of both antennas and the half-power beamwidth θ_{3dB} of the Earth station antenna
- 2) Evaluate the maximum data rate R of the link assuming the path length $r=0.78 \cdot 10^9$ Km and the additional link attenuation $L_a=5$ dB (due to atmospheric losses).
- 3) If there is an error in the antenna pointing equal to $\theta_{3dB}/2$, what is the resulting degraded BER for the same data rate previously evaluated? Assume:

$$BER = \frac{1}{2} \operatorname{erfc}(\sqrt{x}) \cong -0.0012541x^3 + 0.016458x^2 - 0.073553x + 0.11351 \quad (x=E_b/N_0)$$

Exercise 2

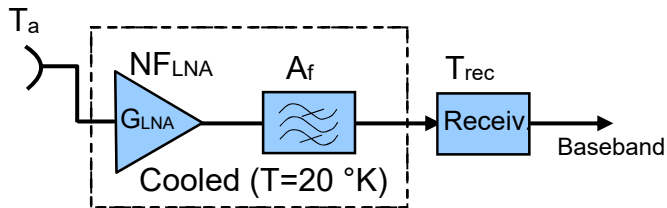


$T_a=10^\circ\text{K}$
 $NF_{LNA}= ?$
 $G_{LNA}=20 \text{ dB}$
 $A_f=0.5 \text{ dB}$
 $T_{rec}= 100^\circ\text{K}$

The scheme in the above figure represents the front-end of the Earth Station receiver of exercise 1 (note that the low noise amplifier and the filter are cooled at 20°K). Assuming the parameters above reported and the imposed system temperature $T_{sys}=25^\circ\text{K}$, evaluate the required value of the LNA noise figure. If the system SNR must be 10 dB, what is the maximum system bandwidth?

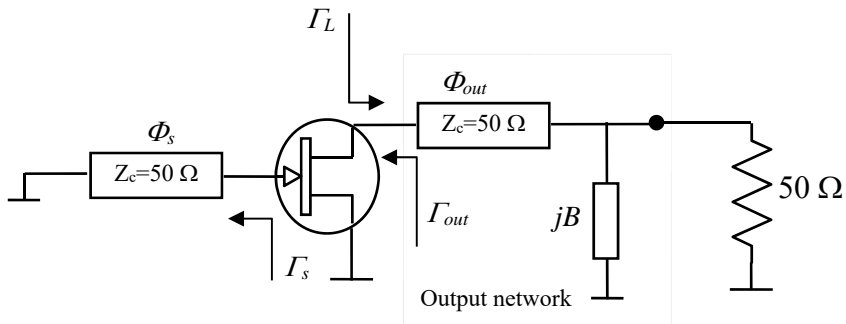Exercise 3

We want design the oscillator in the following figure, operating at 5 GHz:



The scattering parameters of the transistor are given by:

$$S_{11}=0.844\angle-62.3^\circ, S_{21}=5.273\angle121.7^\circ, S_{12}=0.069\angle42.7^\circ, S_{22}=0.521\angle-52.6^\circ$$

- Select a value for Γ_s and evaluate the electrical length Φ_s of the first line. (Hint: set $|\Gamma_{out}|=1.2$ and select the Γ_s which determines the minimum value of Φ_s)
- Design the output network, once the required value of Γ_L has been computed